



Analog IC Design : 2022-23


Lecture 3

MOSFET Single Stage Amplifiers Part-2


By Dr. Sanjay Vidhyadharan

sanjayvidhyadharan.in


CS Amplifier

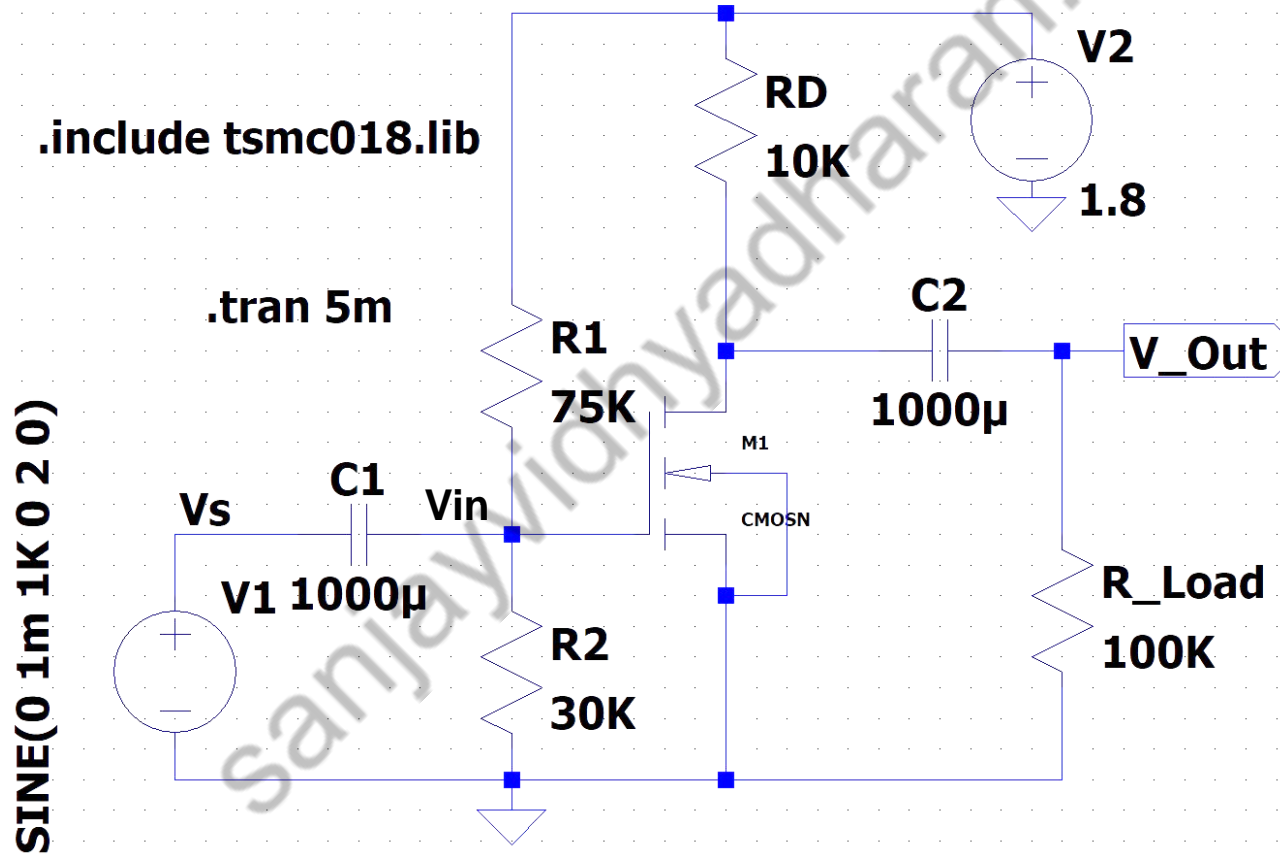

CS Amplifier

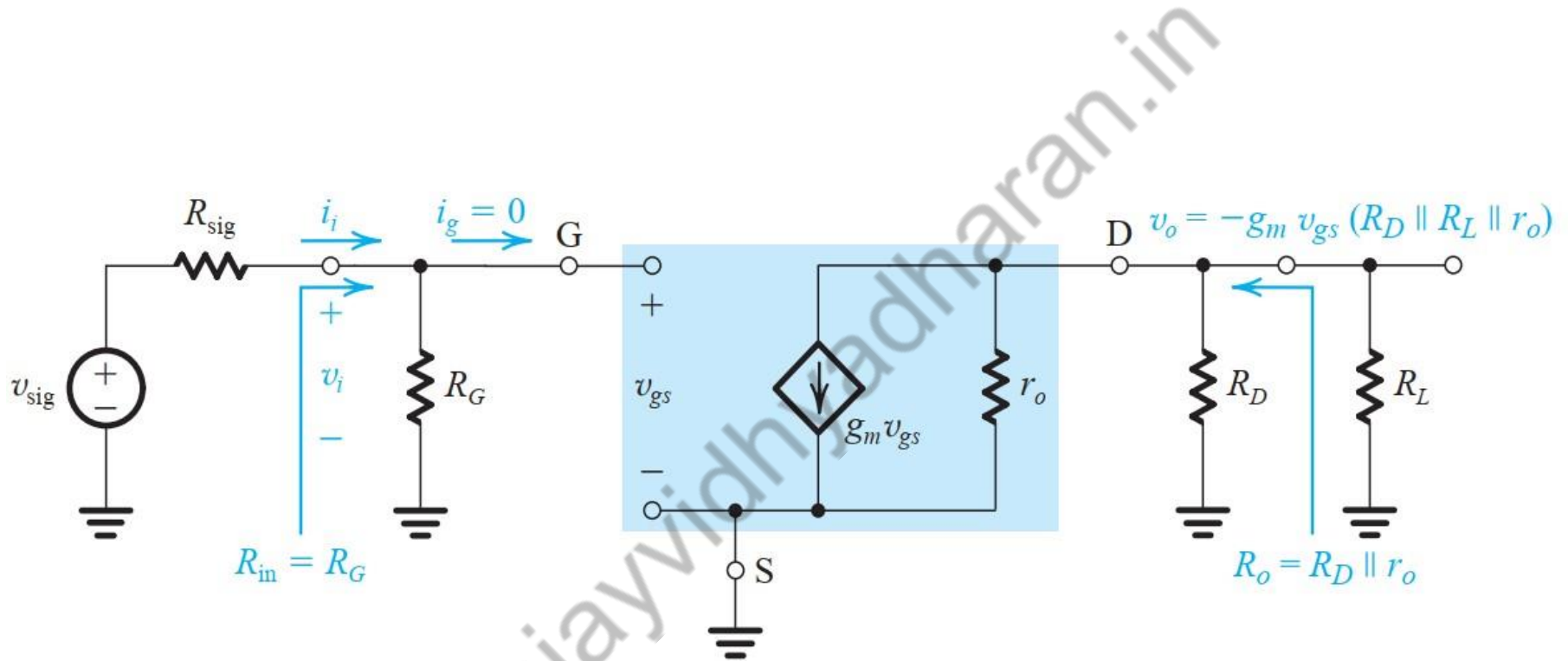

CS Amplifier

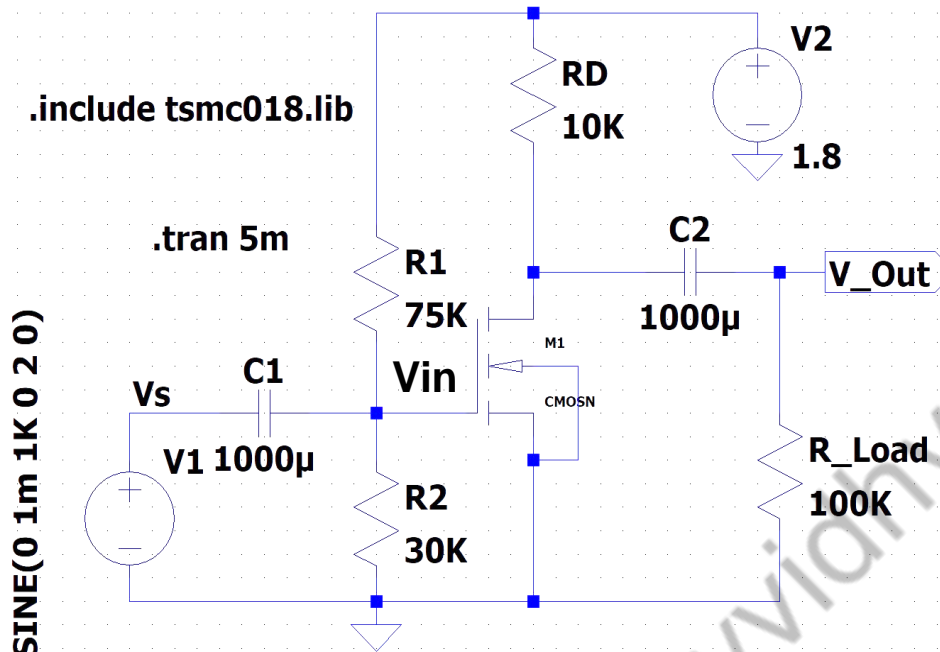

Design Steps


- Fix I_{DQ} Meeting following conditions
 - $I_{DQ} * V_{DD} < \text{Max Power Constraint}$
 - $SR = dV_o / dt$ maximum $V/\mu s$
 $SR = I_D / C_{Load}$
- Fix R_D for Max Symmetrical Output swing
 $R_D = (V_{DD} - V_{ov}) / 2I_{DQ}$
- Fix (W/L) for required gain

$$\text{Gain} = -g_m * (R_D || r_o || RL)$$

$$g_m = 2I_D / V_{ov}$$

$$g_m = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right) I_D}$$

CS Amplifier

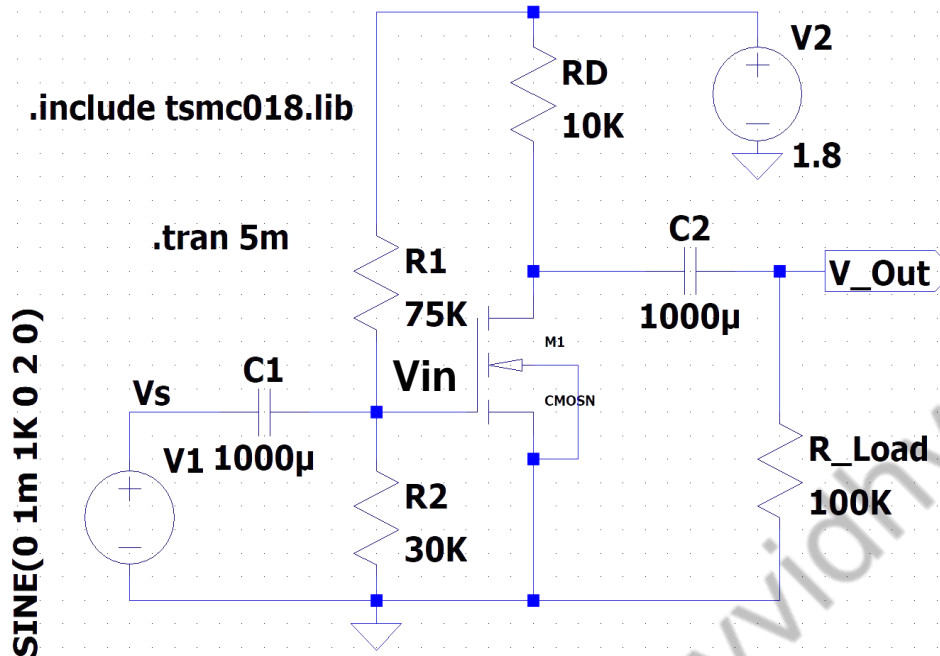

Design Steps

4. Design issues with R1 and R2
Set for V-overdrive (V_{GS})

$$g_m = \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_{Tn}) (1 + \lambda_n V_{DS})$$



5. Values of C1 and C2

Gain is a function of Load Resistance
High Input Impedence
High Miller Capacitance
Current, Voltage and Power Gain

$$\text{Gain} = -g_m * (R_D || r_o || RL)$$

CS Amplifier

CS stage with source degeneration.

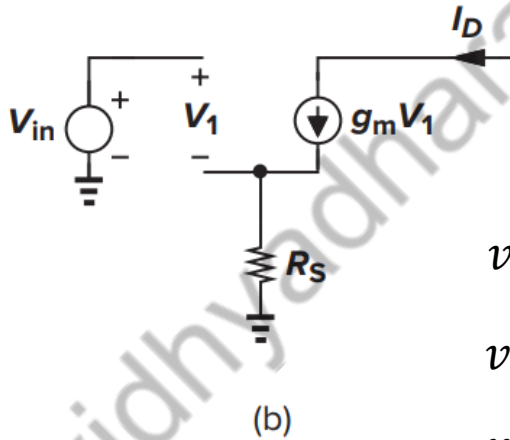 

$$V_{IN} = V_{GS} + I_D R_S$$

$$\Delta I_D = \Delta(V_{IN} - V_{GS})/R_S$$

$$v_{in} = v_{gs} + i_d R_S$$

$$v_{in} = v_{gs} + g_m v_{gs} R_S$$

$$v_{in} = v_{gs} (1 + g_m R_S)$$

$$v_{out} = i_d R_D$$



$$v_{out} = -v_{gs} g_m R_D$$

$$Gain = - \frac{g_m R_D}{(1 + g_m R_S)}$$

$$Gain \sim - \frac{R_D}{R_S}$$

CS Amplifier

CS stage with source degeneration.

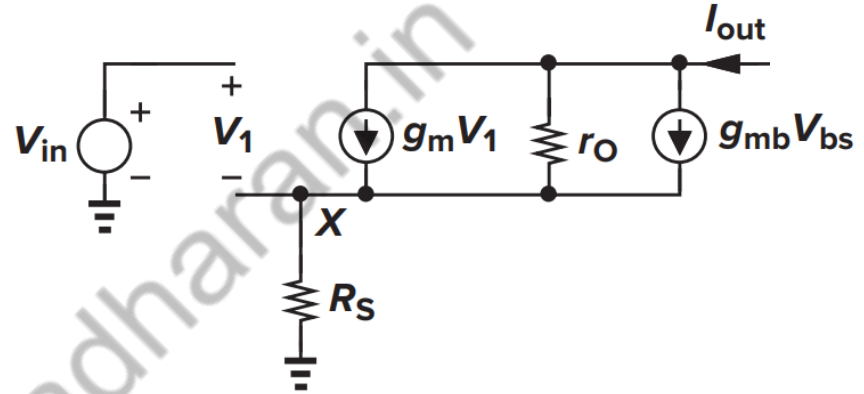 

$$v_{in} = v_{gs} + V_X$$

$$v_{out} = -i_{out} R_D$$

$$v_{in} = v_{gs} + i_{out} R_S$$

$$i_{out} = g_m (v_{in} - i_{out} R_S) - (g_{mb} i_{out} R_S) + \frac{-i_{out} R_D - i_{out} R_S}{r_o}$$

$$i_{out} \left(1 + (g_m + g_{mb}) R_S + \frac{R_D + R_S}{r_o} \right) = g_m v_{in}$$


$$Gain = \frac{-g_m R_D}{1 + (g_m + g_{mb}) R_S + \frac{R_D + R_S}{r_o}}$$

$$Gain = \frac{-g_m R_D r_o}{R_D + R_S + r_o + (g_m + g_{mb}) R_S r_o}$$

$$Gain \sim - \frac{R_D}{R_S} \quad 7$$

CS Amplifier

CS Amplifier Output Resistance

 


$$i_{out} = -g_m i_{out} R_s - g_{mb} i_{out} R_s + \frac{v_{out} - i_{out} R_s}{r_o}$$

$$i_{out} ((g_m + g_{mb}) r_o R_s + r_o + R_s) = v_{out}$$

$$R_{out} \approx r_o + g_m r_o R_s$$

CS Amplifier

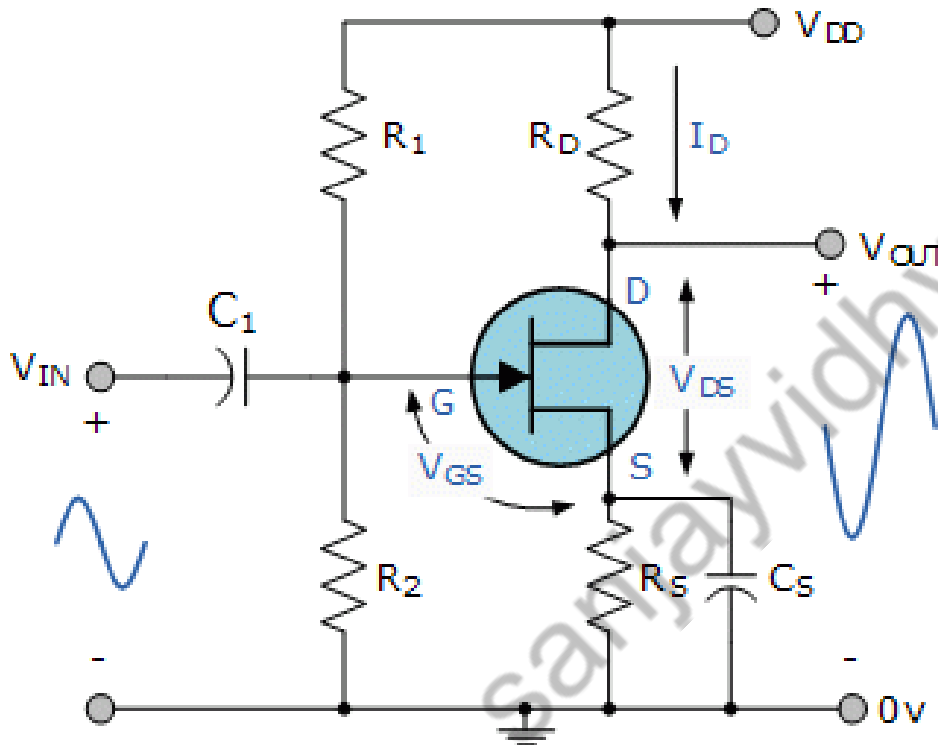CS stage with source degeneration and bypass capacitor.




$$\text{Gain} \sim -g_m R_D$$

Design Steps


1. Fix I_{DQ} Meeting following conditions
 - (a) $I_{DQ} * V_{DD} < \text{Max Power Constraint}$
 - (b) $SR = dV_o / dt$ maximum $V/\mu s$
 $SR = I_{DQ} / C_{Load}$
2. Fix R_D for Max Symmetrical Output swing
 $R_D = (0.9 V_{DD} - V_{ov}) / 2I_{DQ}$
3. $R_S = 0.1 V_{DD} / I_{DQ}$

CS Amp with Current Source Supply

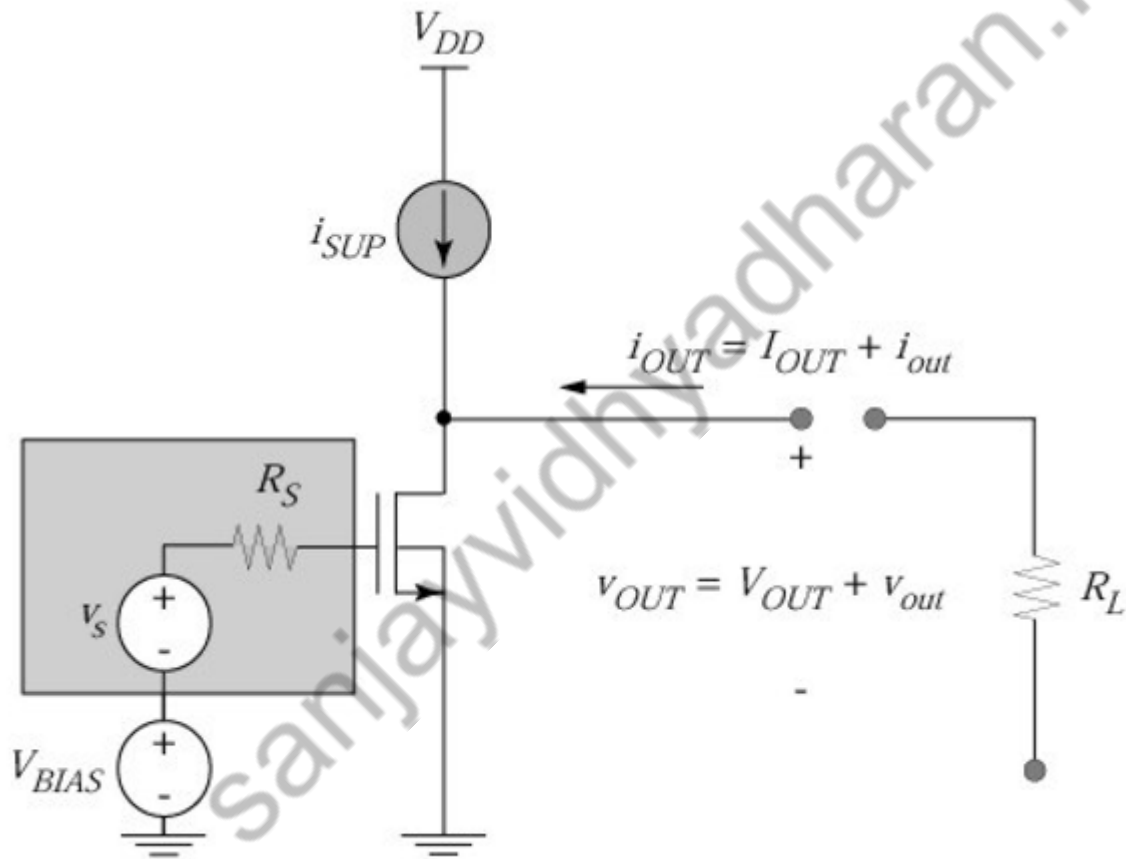

Gain = ?

CS Amp with Current Source Supply

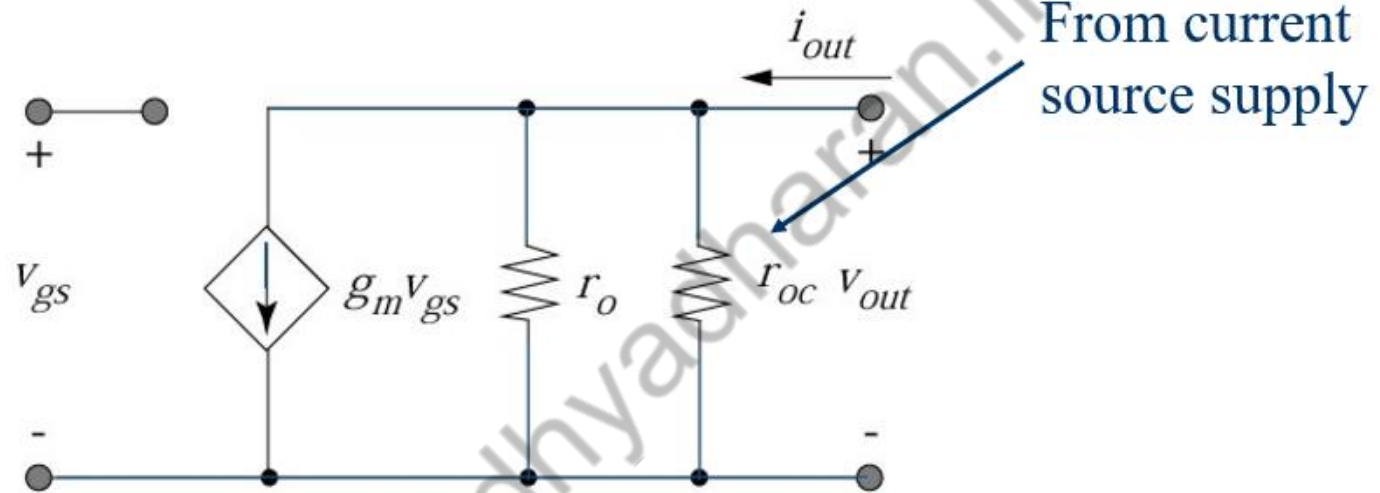


$$R_{in} = \infty$$

$$G_m = g_m$$


$$R_{out} = r_o \parallel r_{oc}$$

P-Channel CS Amplifier

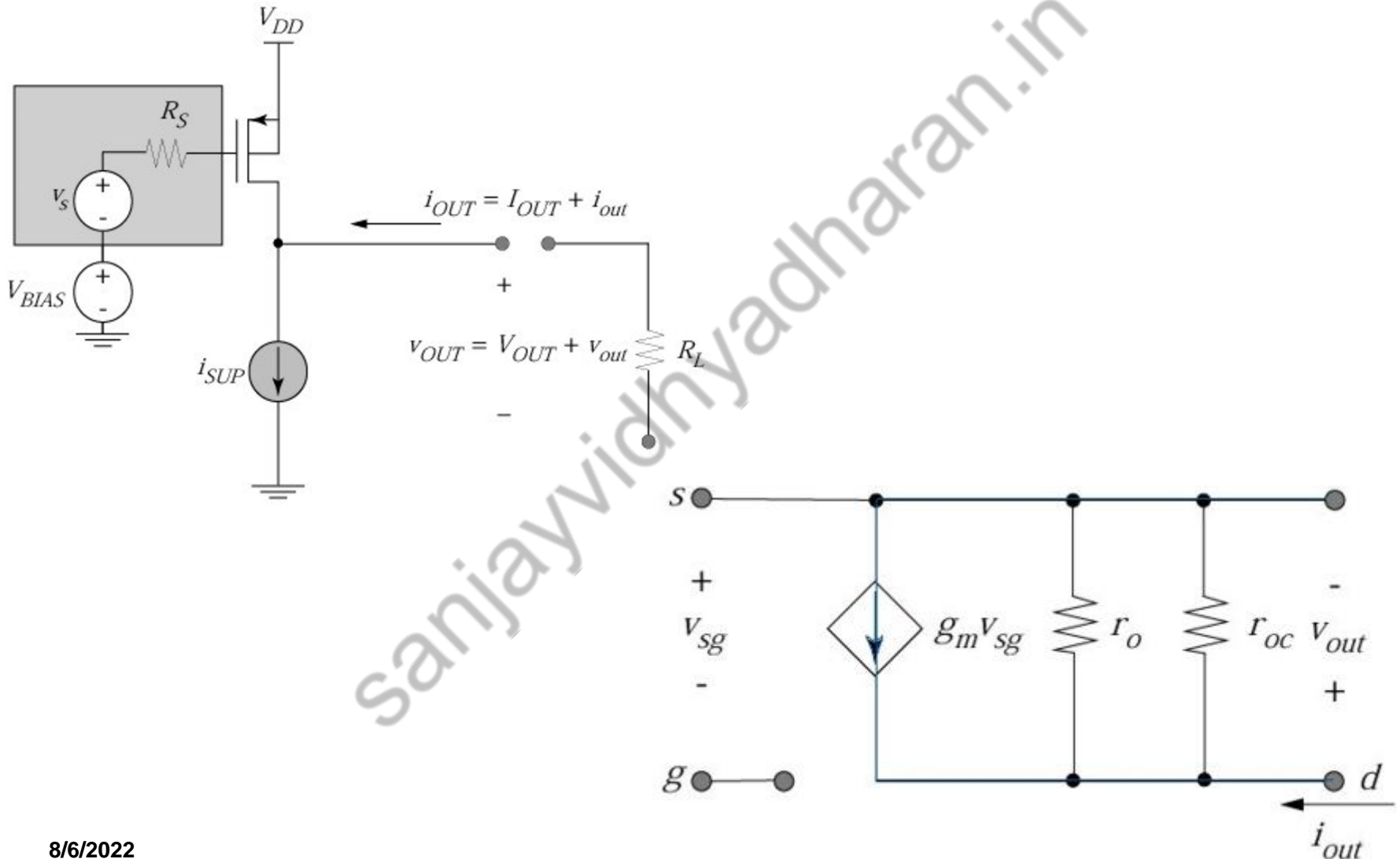

8/6/2022

CS Amplifier with Active Load

 

$$v_{out} = g_{m1} v_{in} * (r_{o1} || r_{o2})$$

CS Amplifier with Active Load

Design Steps

1. Fix I_{DQ} Meeting following conditions

(a) $I_{DQ} * V_{DD} < \text{Max Power Constraint}$


(b) $SR = dV_o / dt$ maximum $V/\mu s$

$$SR = I_{DQ} / C_{load}$$





2. $Gain = g_m (r_{o1} || r_{o2} || R_L)$

$$g_m = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right) I_D}$$

 
$$g_m = \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_{Tn}) (1 + \lambda_n V_{DS})$$



Active Loads

 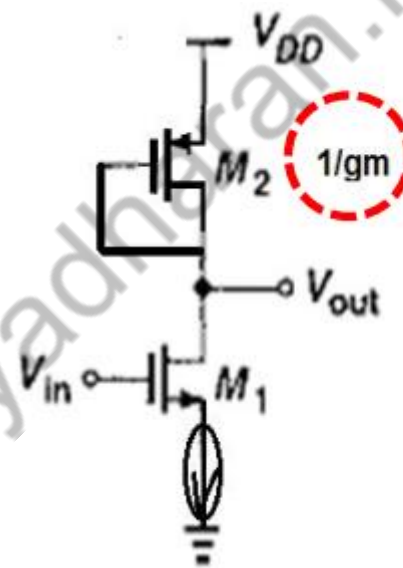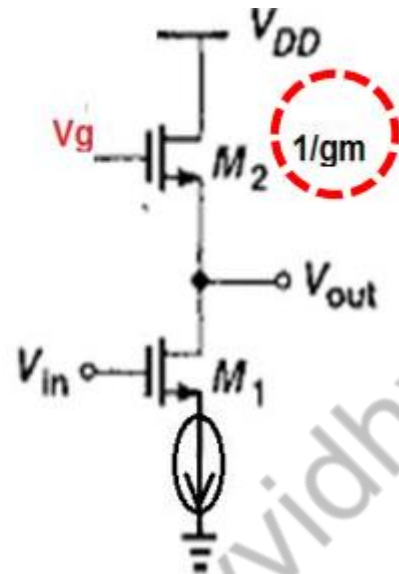 

Active Loads

 

By applying KVL,,


$$\text{We have, } V_{GS} = V_G - V_S = - V_x$$

$$V_{BS} = V_B - V_S = - V_x \text{ [Body is connected to ground]}$$


By applying KCL at Node A, We get,

$$I_x + g_m V_{GS} + g_{mb} V_{BS} - V_x/r_o = 0$$
 
$$\text{i.e. } I_x = g_m V_x + g_{mb} V_x + V_x/r_o$$




Common Gate Amplifier

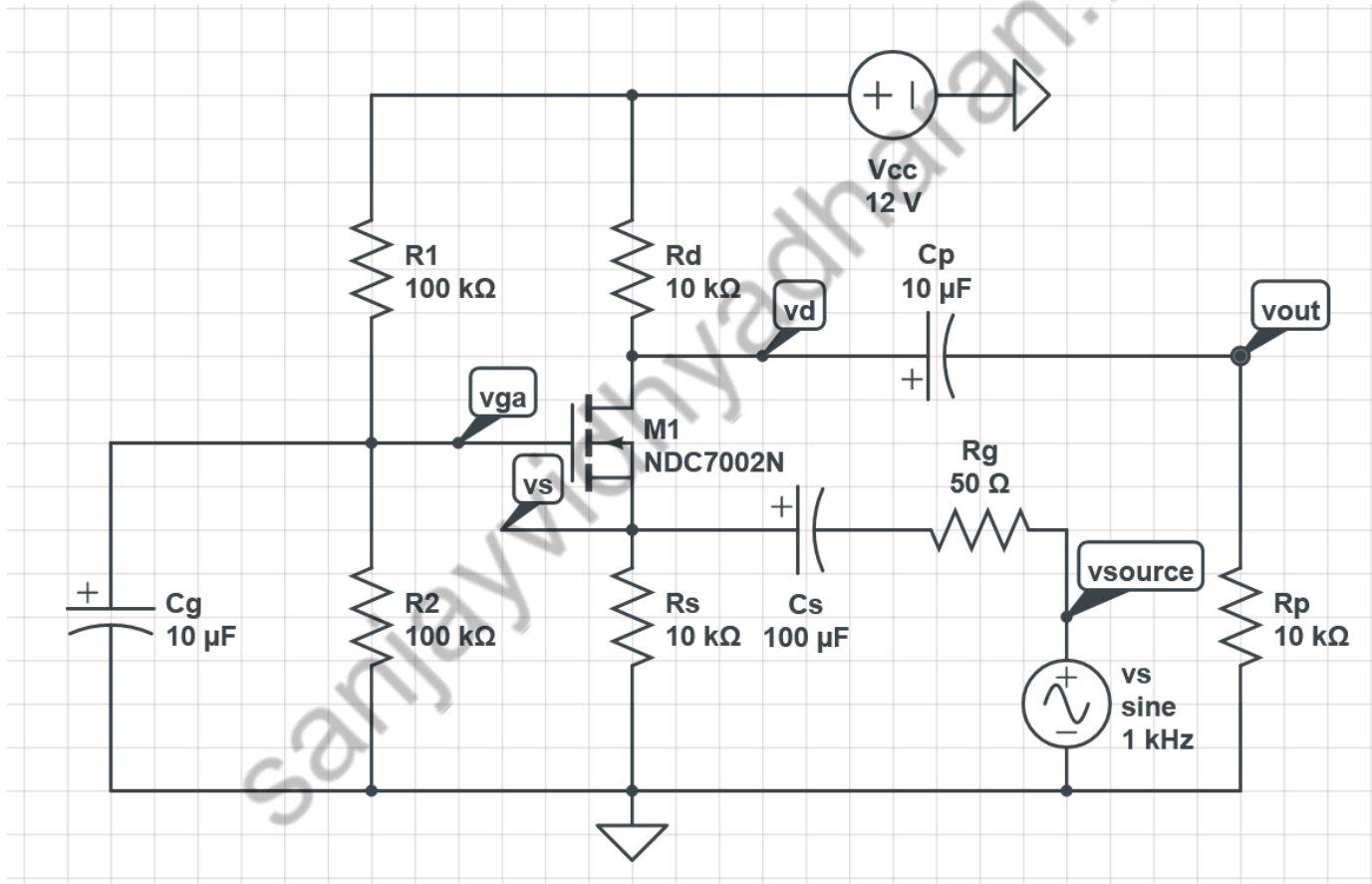

8/6/2022

17

Common Gate Amplifier

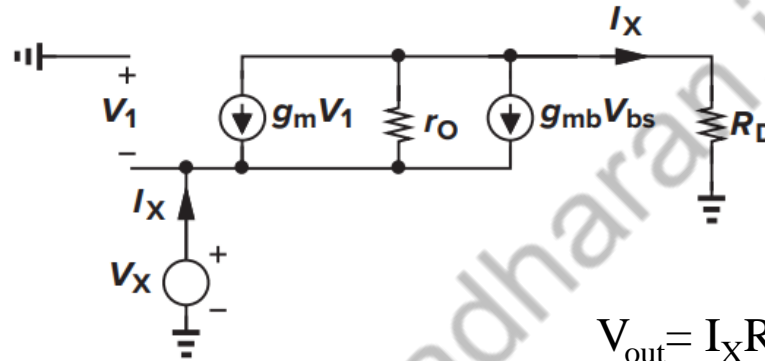

$$V_1 = -V_X$$

$$V_{out} = I_X R_D$$

$$R_D I_X + r_O [I_X - (g_m + g_{mb}) V_X] = V_X$$

$$\text{Gain} = R_D (1/r_o + g_m + g_{mb})$$

$$\begin{aligned} \frac{V_X}{I_X} &= \frac{r_o}{1 + (g_m + g_{mb}) r_o} \\ &= \frac{1}{\frac{1}{r_o} + g_m + g_{mb}} \end{aligned}$$

$$\text{Gain} \approx R_D (g_m + g_{mb})$$

Advantages ??

Low I/P Impedance

High Frequency Applications

Gain is a function of Load Resistance


Low Input Impedance

Low Miller Capacitance

Current, Voltage and Power Gain

Simulation

Common Drain Amplifier

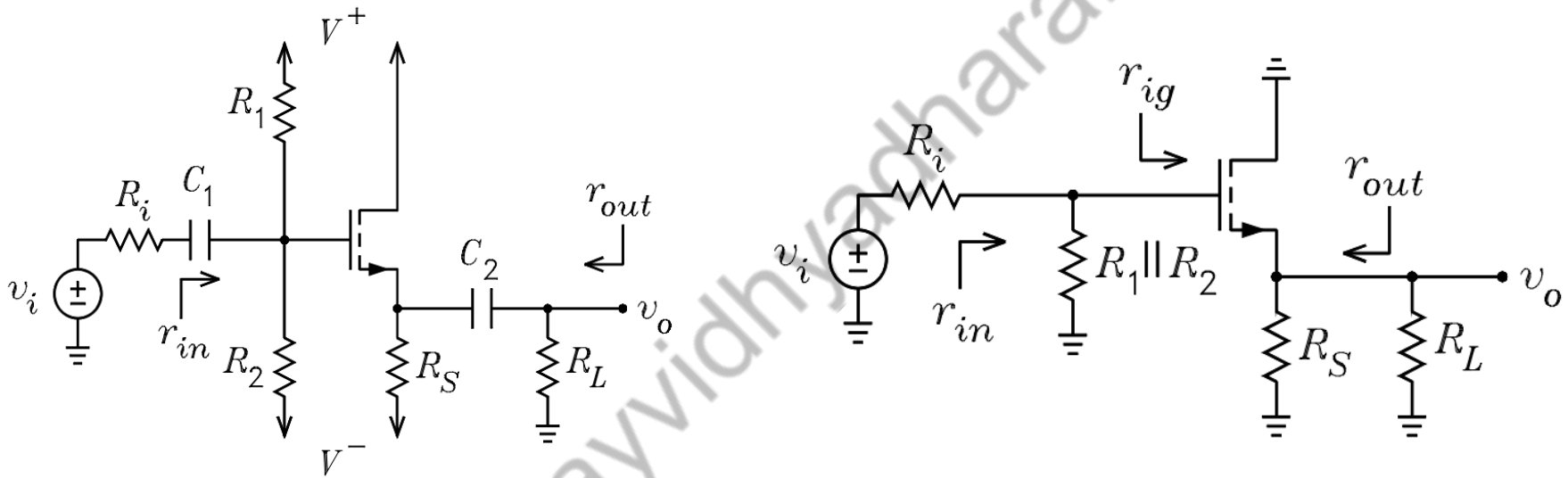

Assuming $R_1 \parallel R_2 \gg r_{in}$

$$V_{in} = V_{gs} + V_{out}$$

Common Drain Amplifier


$$V_{in} = V_{gs} + V_{out}$$

$$\frac{v_{out}}{R'_L || r_o} = g_m v_{gs} - g_{mb} v_{out}$$

$$\frac{v_{out}}{R'_L || r_o} = g_m (v_{in} - v_{out}) - g_{mb} v_{out}$$

$$\frac{v_{out}}{v_{in}} = \frac{g_m}{\frac{1}{R'_L || r_o} + g_{mb} + g_m}$$
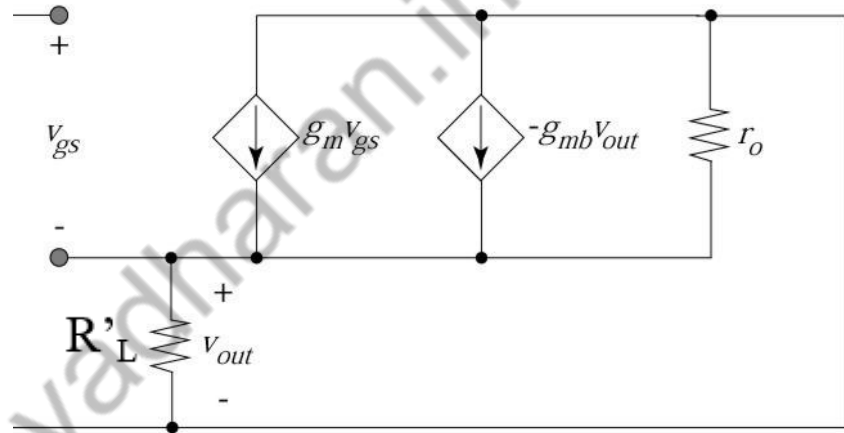
$$\frac{V_{out}}{V_{in}} \approx \frac{g_m}{g_{mb} + g_m} \approx 1$$



Advantages ??


Low O/P Impedance

$$R_{out} \approx \frac{1}{g_m + g_{mb}}$$

*Gain is a **NOT** function of Load Resistance
Current, Voltage and Power Gain*


Summary of CS, CG & CD Amplifiers with Current Source Bias

	Transistor Type	
	NMOS	PMOS
Common Source/ Common Emitter (CS/CE)		
Common Gate/ Common Base (CG/CB)		
Common Drain/ Common Collector (CD/CC)		

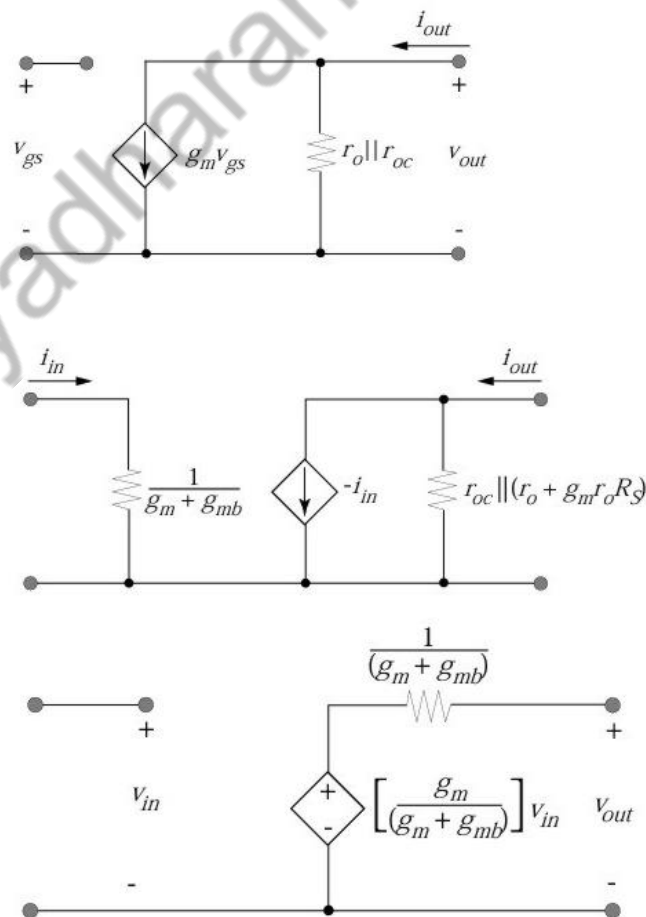

Telescopic Cascode Amplifier
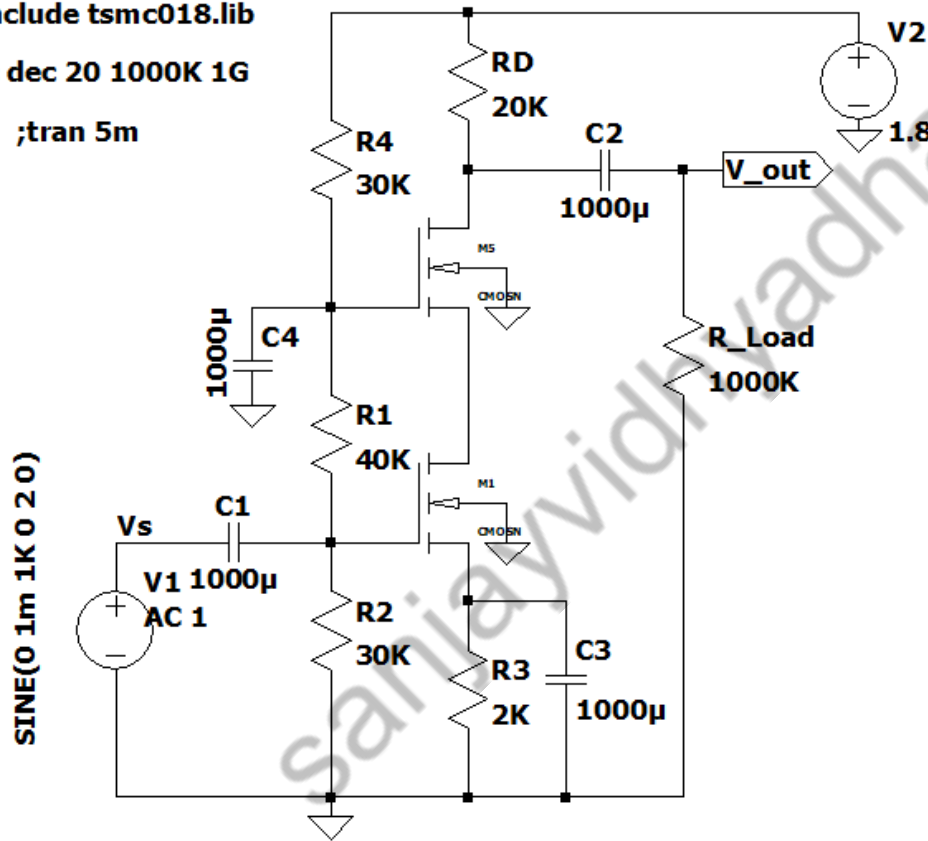
```
.include tsmc018.lib
.ac dec 20 1000K 1G
;tran 5m
```





$$Gain \sim -g_m R_D$$

Advantages ??

Telescopic Cascode Amplifier
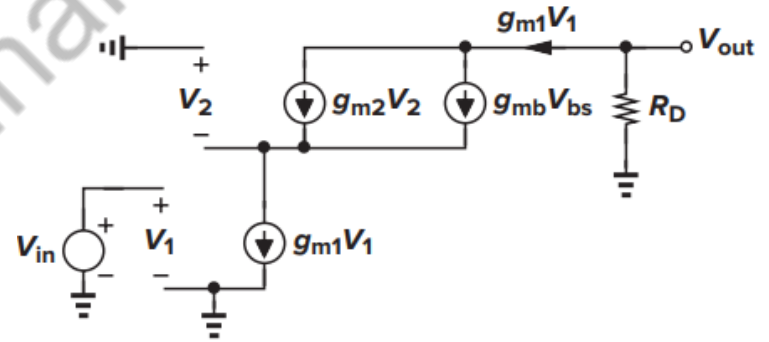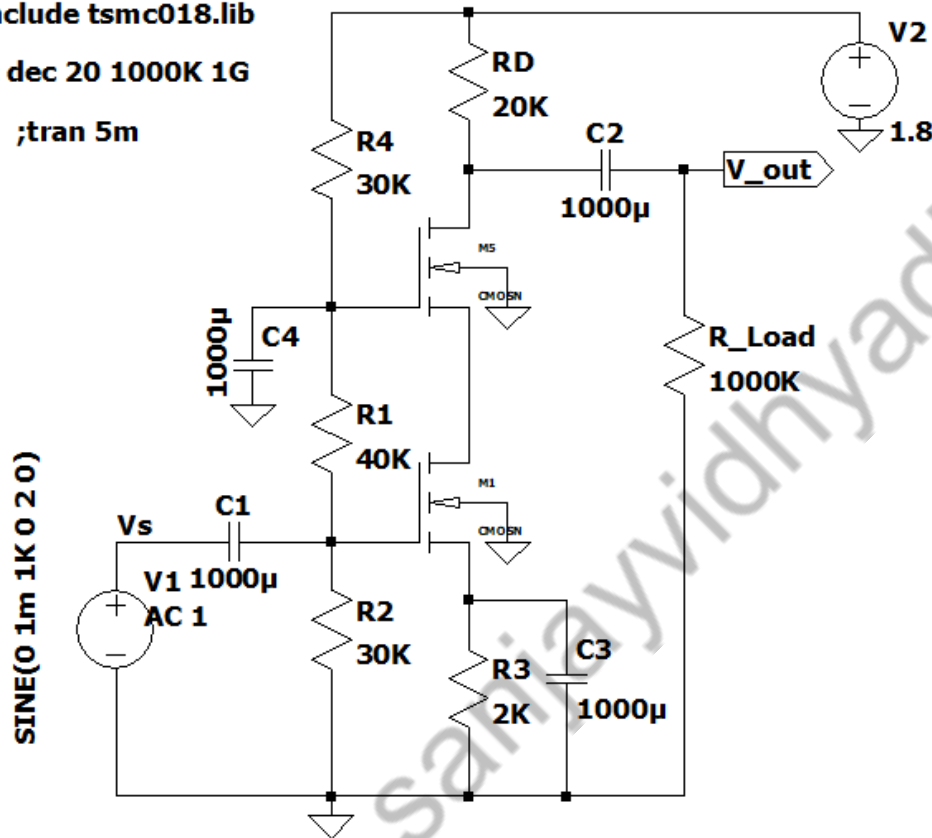
```
.include tsmc018.lib
.ac dec 20 1000K 1G
;tran 5m
```




$Gain \sim -g_m R_D$

Advantages ??

Telescopic Cascode Amplifier

Cascode Amplifier Output Resistance

 



$$i_{out} = -g_{m2} i_{out} r_{o1} - g_{mb2} i_{out} r_{o1} + \frac{v_{out} - i_{out} r_{o1}}{r_{o2}}$$

$$i_{out} ((g_{m2} + g_{mb2}) r_{o1} r_{o2} + r_{o1} + r_{o2}) = v_{out}$$

$$R_{out} \approx (g_{m2} + g_{mb2}) r_{o2} r_{o1}$$

Telescopic Cascode Amplifier

  Cascode Amplifier with Simple Active Load



$$A_v = -g_{m1}(R_o \parallel R_L)$$

$$R_o \approx (g_{m2}r_{o2})r_{o1}$$

$$R_L = r_{o3} \ll R_o$$



$$A_v \approx -g_{m1}r_{o3}$$

Similar gain as CS amplifier.

No gain boosting.

Telescopic Cascode Amplifier

  Cascode Amplifier with Cascode Current-Source Load



$$A_v = -g_{m1}(R_{on} \parallel R_{op})$$

$$R_{on} \approx (g_{m2}r_{o2})r_{o1}$$

$$R_{op} \approx (g_{m3}r_{o3})r_{o4}$$


If all transistors are similar :

$$A_v = -\frac{1}{2}(g_m r_o)^2$$

--> High gain !

Disadvantages ??

Folded Cascode Amplifier

 

"Folding" the CG stage using PMOS.

Q_1 is biased with $I_1 - I_2$

Q_2 is biased with I_2

Folded cascode avoids stacking too many transistors vertically, which will be difficult for low power supply voltage V_{DD}

Folded Cascode Amplifier


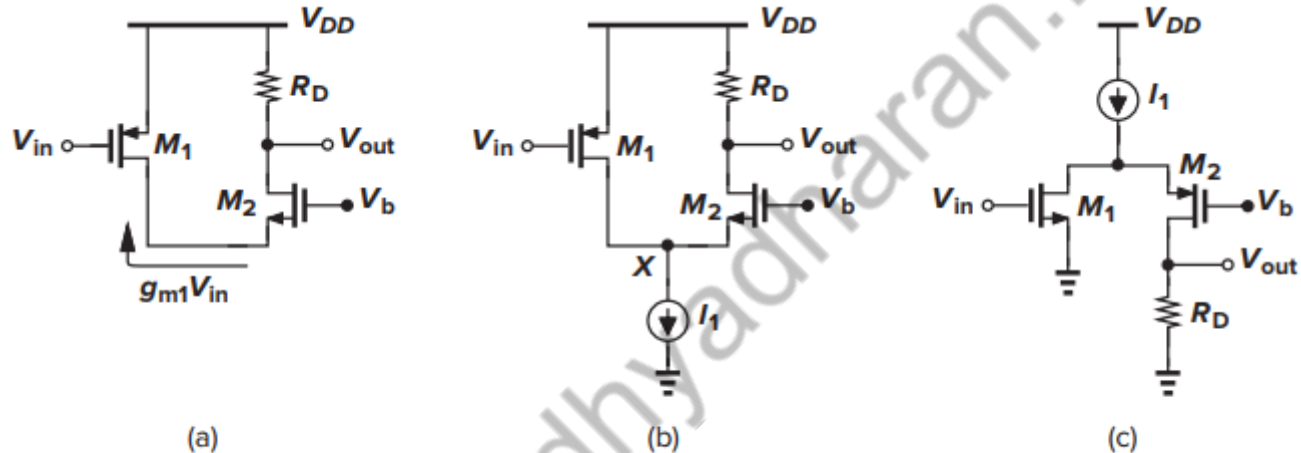


Figure 3.74 (a) Simple folded cascode; (b) folded cascode with proper biasing; (c) folded cascode with NMOS input.

Source: Design of Analog CMOS Integrated Circuits by Behzad Razavi


Folded Cascode Amplifier

Folded cascode with cascode load.

 


Source: Design of Analog CMOS Integrated Circuits by Behzad Razavi

Useful Transistor Pairings

 


CC + CE

 - High input resistance
- Much wider bandwidth than single CE amplifier (To be discussed later)



CD + CS

 - Main benefit is wider bandwidth than single CE amplifier



CD + CE

- in BiCMOS technology (BJT+CMOS)
- Similar to MOS version but use BJT for higher g_m

Thank you