 





**Analog IC Design : 2022-23**  
**Lecture 4**  
**Differential Amplifiers Part-1**  
**By Dr. Sanjay Vidhyadharan**

sanjay vidhyadharan

# Single-Ended and Differential Operation



(a)

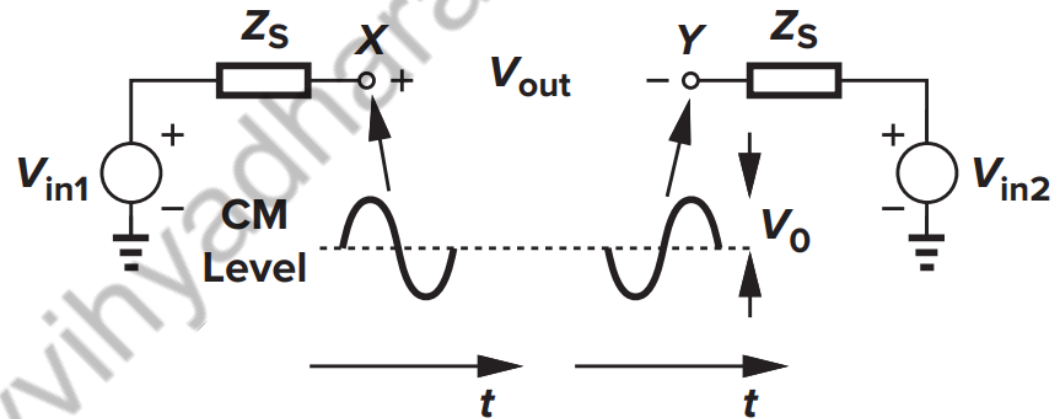


(b)

(a) Single-ended and (b) differential signals.


# Advantages of Differential Signals

## Transmission Line Noise Cancellation

 


# Advantages of Differential Signals


## Power Supply Noise Cancellation

 
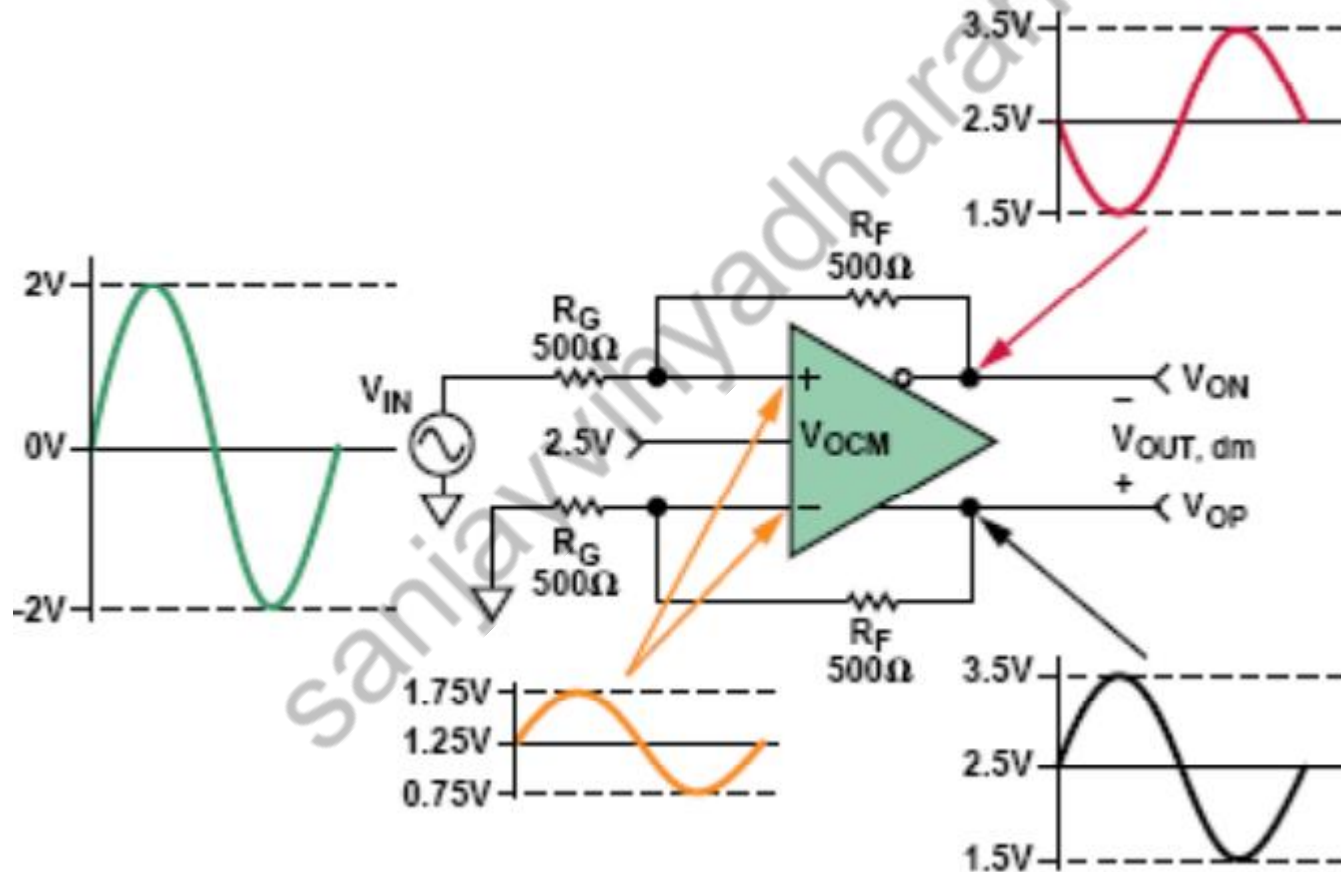
# Converting Single Input to Differential


 
# Converting Single Input to Differential



# Differential Amplifier Definitions

- Common mode rejection ratio (*CMRR*)

$$CMRR = \left| \frac{A_{VD}}{A_{VC}} \right|$$

*CMRR* is a measure of how well the differential amplifier rejects the common-mode input voltage in favor of the differential-input voltage.

- Input common-mode range (*ICMR*)

The input common-mode range is the range of common-mode voltages over which the differential amplifier continues to sense and amplify the difference signal with the same gain.

Typically, the *ICMR* is defined by the common-mode voltage range over which all MOSFETs remain in the saturation region.

- Output offset voltage ( $V_{OS(out)}$ )


The output offset voltage is the voltage which appears at the output of the differential amplifier when the input terminals are connected together.

- Input offset voltage ( $V_{OS(in)} = V_{OS}$ )



The input offset voltage is equal to the output offset voltage divided by the differential voltage gain.

$$V_{OS} = \frac{V_{OS(out)}}{A_{VD}}$$

# Simple Differential Circuit

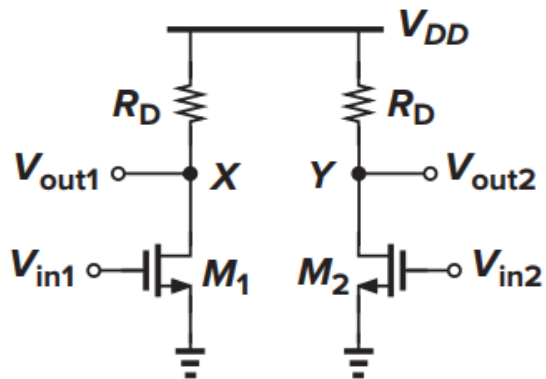




(a)

  

(b)



# Basic MOS Differential Pair

  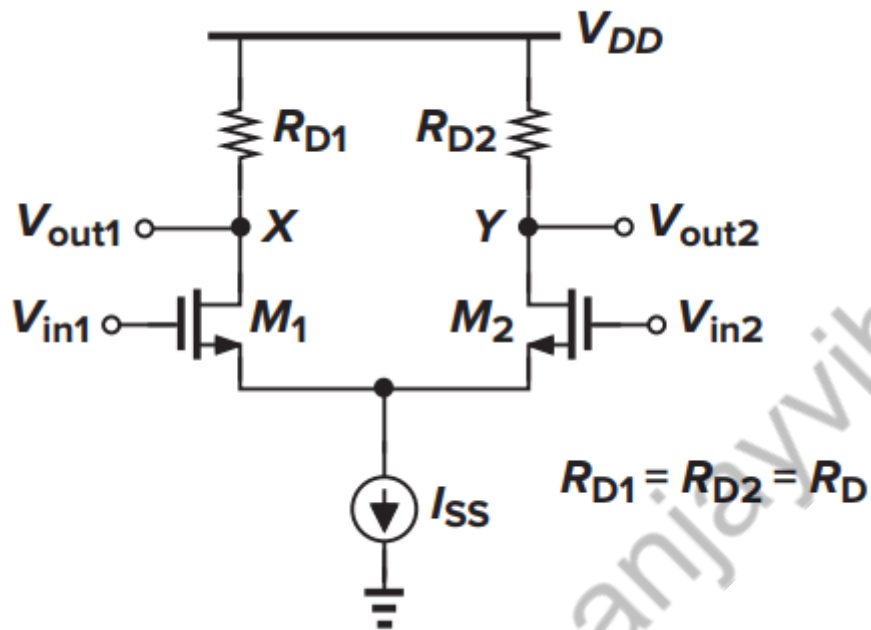

“Current stealing” phenomenon

# MOSFET Current Equation

$$k'_n = \mu_n C_{ox}$$

$$I_D = \frac{k'_n W (V_{GS} - V_T)^2}{2L}$$

$$k_n = k'_n (W/L)$$

$$k_n = (\mu_n C_{ox}) (W/L)$$

$$\beta = \frac{1}{2} \mu \cdot C_{ox} \cdot \frac{W}{L}$$


$$I_D = \beta (V_{GS} - V_T)^2$$

$$I_D = \frac{\mu_n C_{ox}}{2} \left( \frac{W}{L} \right) (V_{GS} - V_{tn})^2$$

$$i_D = \frac{1}{2} k'_n \left( \frac{W}{L} \right) (v_{GS} - V_t)^2$$

$$i_D = \frac{1}{2} k'_n \left( \frac{W}{L} \right) v_{OV}^2$$

# MOS Differential Pair

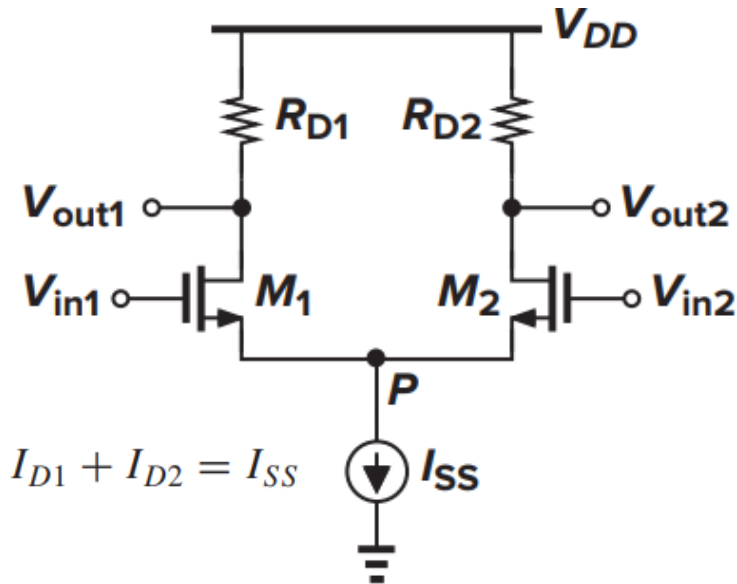

$$(V_{GS} - V_{TH})^2 = \frac{I_D}{\frac{1}{2}\mu_n C_{ox} \frac{W}{L}}$$

$$V_{GS} = \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} + V_{TH}$$

$$V_{in1} - V_{in2} = \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} \frac{W}{L}}} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox} \frac{W}{L}}}$$

$$(V_{in1} - V_{in2})^2 = \frac{2}{\mu_n C_{ox} \frac{W}{L}} (I_{SS} - 2\sqrt{I_{D1}I_{D2}})$$

sgb


$$\left( \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2 \right) - I_{SS} = -2\sqrt{I_{D1}I_{D2}}$$

$$4I_{D1}I_{D2} = (I_{D1} + I_{D2})^2 - (I_{D1} - I_{D2})^2 = I_{SS}^2 + (I_{D1} - I_{D2})^2$$

$$(I_{D1} - I_{D2})^2 = \frac{1}{4} \left( \mu_n C_{ox} \frac{W}{L} \right)^2 (V_{in1} - V_{in2})^4 + I_{SS} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2$$


$$I_{D1} - I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2}) \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2}$$

# MOS Differential Pair

 

 
## Differential Transconductance Gain vs. Input Voltage

$$\frac{\partial I_D}{\partial V_{in}} = G_m = \frac{\mu_n C_{ox}}{2} \frac{W}{L} \frac{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - 2(V_{in1} - V_{in2})^2}{\sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2}}$$



(a)

 


(b)

## Maximum Differential Transconductance Gain Occurs at $\Delta V_{in}=0$

$$g_m = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right) I_D}$$

$$G_{m,max} = \sqrt{\mu_n C_{ox} \left(\frac{W}{L}\right) I_{SS}}$$

# MOS Differential Pair

 

## Differential Voltage Gain

$$V_{out1} - V_{out2} = R_D \Delta I_D = R_D G_m \Delta V_{in}$$



## Differential Voltage Gain near $\Delta V_{in} = 0$

$$|A_v| = \frac{\Delta V_{out}}{\Delta V_{in}} = G_{m,max} R_D = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}} R_D$$

Differential Transconductance Gain Falls to Zero at  $\Delta V_{in} = \Delta V_{in1}$

$$\frac{\partial \Delta I_D}{\partial \Delta V_{in}} = G_m = \frac{\mu_n C_{ox} W}{2L} \frac{4I_{SS} - 2(V_{in1} - V_{in2})^2}{\sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2}}$$
  
$$\rightarrow \Delta V_{in1} = \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$




$\Delta V_{in} = \Delta V_{in1}$  is the maximum differential input that the amplifier can “handle”

# MOS Differential Pair
 
## Two types of Differential Gains

“Single-ended”:  $V_{out1}$   
(or  $V_{out2}$ )  
with respect  
to ground.





$$A_v(diff) = \frac{V_{out1} - V_{out2}}{V_{in1} - V_{in2}} = ?$$

$$A_v(S.E.) = \frac{V_{out1}}{V_{in1} - V_{in2}} = ?$$

# CS Amplifier

CS stage with source degeneration.

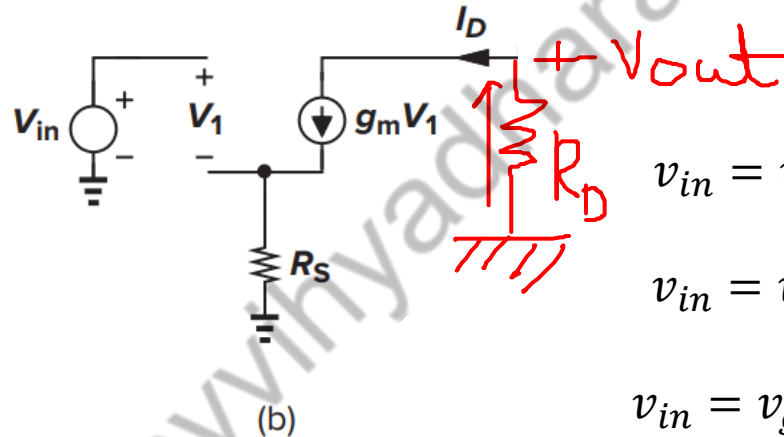 

$$v_{in} = v_{gs} + i_d R_s$$

$$v_{in} = v_{gs} + g_m v_{gs} R_s$$




$$v_{in} = v_{gs} (1 + g_m R_s)$$

$$v_{out} = -i_d R_D$$

$$v_{out} = -v_{gs} g_m R_D$$

$$Gain = \frac{-g_m R_D}{1 + g_m R_s} = \frac{-R_D}{\frac{1}{g_m} + R_s}$$


# Differential Mode Response

   

$$\frac{V_X}{V_{in1}} = \frac{-R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$



# Differential Mode Response

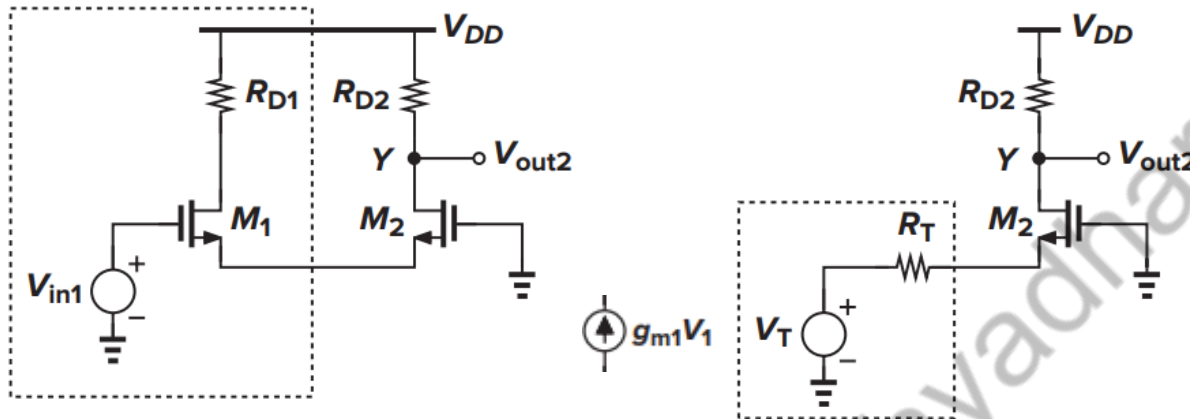

$$-v_{gs2} = \frac{-i_d}{g_{m1}} + v_{gs1}$$

$$\frac{i_d}{g_{m2}} = \frac{-i_d}{g_{m1}} + v_{gs1}$$

$$v_{gs1} = \frac{i_d}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

$$v_{out} = i_d R_{D2}$$


$$(V_X - V_Y)|_{\text{Due to } V_{in1}} = \frac{-2R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} V_{in1}$$

$$(V_X - V_Y)|_{\text{Due to } V_{in1}} = -g_m R_D V_{in1}$$

$$\frac{(V_X - V_Y)_{tot}}{V_{in1} - V_{in2}} = -g_m R_D$$

# Differential Mode Response
 
## Single-ended Differential Voltage Gain



$$A_{V,SE} = \frac{V_X}{V_{in1} - V_{in2}} = -\frac{g_m}{2} R_D$$


$$A_{V,SE} = \frac{V_Y}{V_{in1} - V_{in2}} = \frac{g_m}{2} R_D$$

# Differential Mode Response

Comparison: Differential voltage gain of a differential amplifier vs voltage gain of a CS amplifier

- If the same current source  $I_{SS}$  drives the differential amplifier and the CS, each transistor of the differential amplifier has  $g_m$  which is  $1/\sqrt{2}$  of that of the CS transistor. Differential gain reduces by a factor of  $1/\sqrt{2}$ .
- If both amplifiers have the same  $W/L$  in each transistor and the same load, and we want the gain to be the same, then if we use  $I_{SS}$  at CS, we need to use  $2I_{SS}$  at the differential amplifier.

# The “Virtual Ground” Concept

 

$$V_p = V_{in2} + iR$$


$$V_p = V_{in2} + \frac{V_{in1} - V_{in2}}{2R} R$$

$$V_p = \frac{V_{in1} + V_{in2}}{2}$$



- In a symmetric device (as above), if inputs change anti-symmetrically (one goes up by a certain amount, and the other goes down by the same amount), then  $V_P$  does not change.
- For small-signal analysis point  $P$  becomes “virtual ground”

# The “Virtual Ground” Concept

## The “Half-Circuit” Concept

 

# Differential Mode Response

  


No voltage change  
since Left and Right are  
anti-symmetric (odd)

$$\text{Gain} = -g_m R_D$$
 
# Differential Mode Response

Differential-mode small-signal half-circuit



CS amplifier for input difference!

$$\frac{v_{o1}}{v_{id}/2} = -g_m(R_D \parallel r_o)$$

For the total circuit


$$v_{od} = v_{o1} - v_{o2}$$

$$\text{But } v_{o2} = -v_{o1}$$

$$\therefore v_{od} = 2v_{o1}$$

$$A_d = \frac{v_{od}}{v_{id}} = \frac{2v_{o1}}{v_{id}} = -g_m(R_D \parallel r_o)$$

# MOS Differential Pair

 

What is  $\Delta v_{in,max}$ ?

$$v_{G1} = v_t + \sqrt{\frac{2I_{SS}}{k'_n \frac{W}{L}}}$$


$$v_{G2} = v_t$$

$$\Delta v_{in,max} = \sqrt{\frac{2I_{SS}}{k'_n \frac{W}{L}}}$$



# MOS Differential Pair

MOS Differential Pair

 

$V_{CM}$ : Common Mode

$v_{id}$ : Differential Mode


$$v_{G1} = V_{CM} + \frac{v_{id}}{2}, \quad v_{G2} = V_{CM} - \frac{v_{id}}{2}$$

$$V_{CM} = \frac{v_{G1} + v_{G2}}{2}, \quad v_{id} = v_{G1} - v_{G2}$$

Ideally, no CM response, large DM response

# MOS Differential Pair

## Common-Mode

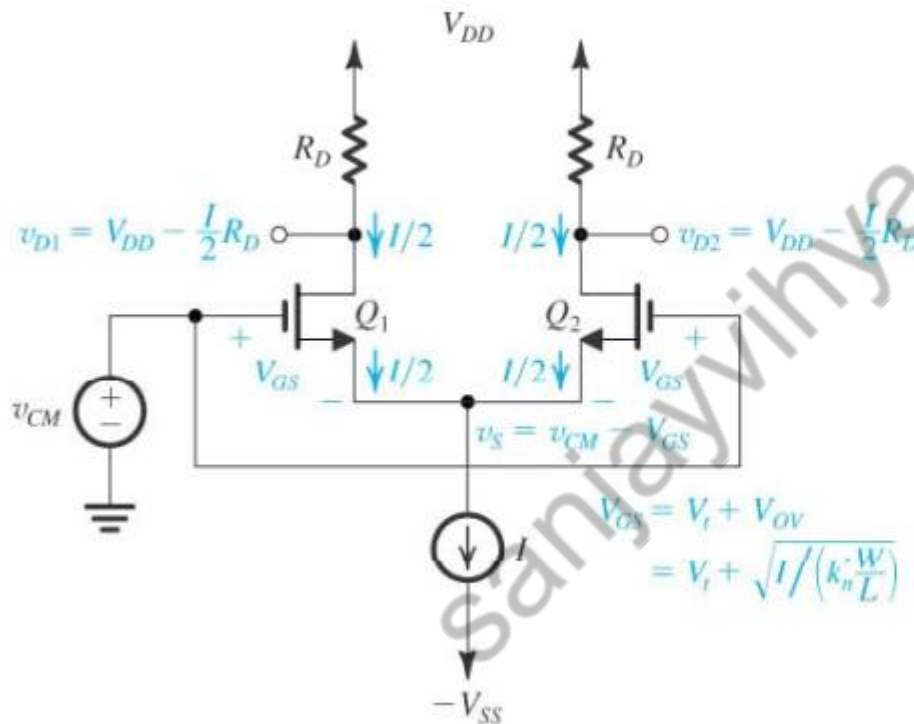


CMMR = ????

# MOS Differential Pair

 
## Common-Mode Input vs. Output Swing Tradeoff

Each drain voltage can go as high as  $V_{DD}$  and as low as  $V_{in,CM} - V_{TH}$ .  
The larger  $V_{in,CM}$  the smaller the swing.



# MOS Differential Pair

## Common-Mode

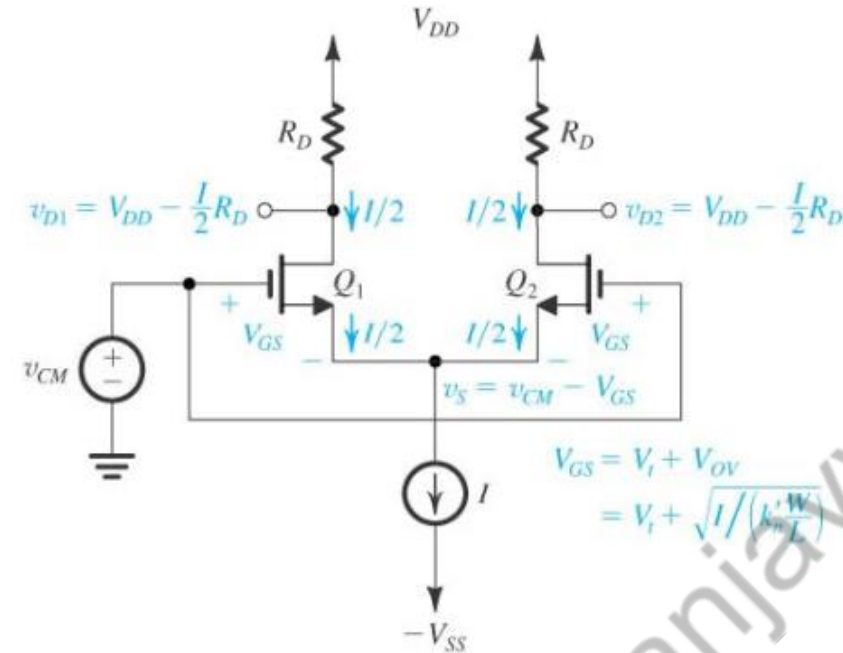

$V_{CM, \max}?$

$$v_{DS} \geq v_{GS} - V_t$$

$$(V_{DD} - \frac{I}{2}R_D) - (V_{CM} - v_{GS}) \geq v_{GS} - V_t$$

$$\therefore V_{DD} - \frac{I}{2}R_D + V_t \geq V_{CM}$$


$$V_{CM, \max} = V_{DD} - \frac{I}{2}R_D + V_t$$

How to  
Maximise ?

If a voltage  $V_{CS}$  is needed across the current source, then

$$V_{CM\min} = -V_{SS} + V_{CS} + V_t + V_{OV}$$

How to  
Minimise ?

 



**Thank you**

sanjayviharadharan