

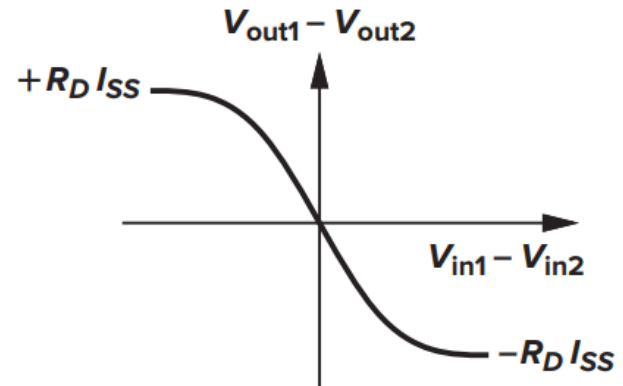


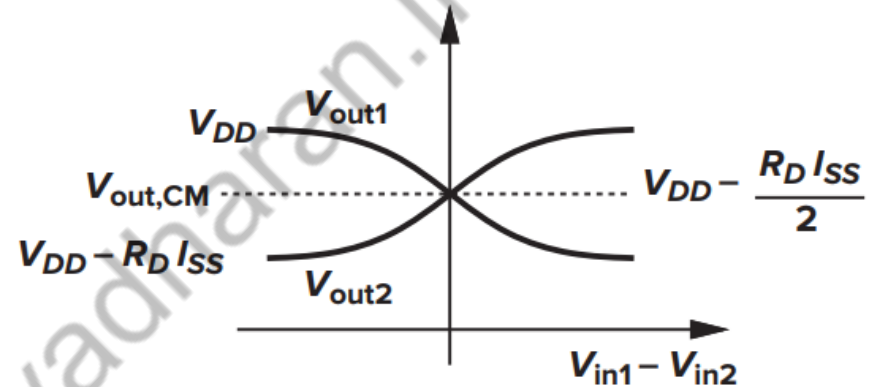

**Analog IC Design : 2022-23**  
**Lecture 5**  
**Differential Amplifiers Part-2**  
**By Dr. Sanjay Vidhyadharan**


sanjayvidhyadharan.in

# Basic MOS Differential Pair

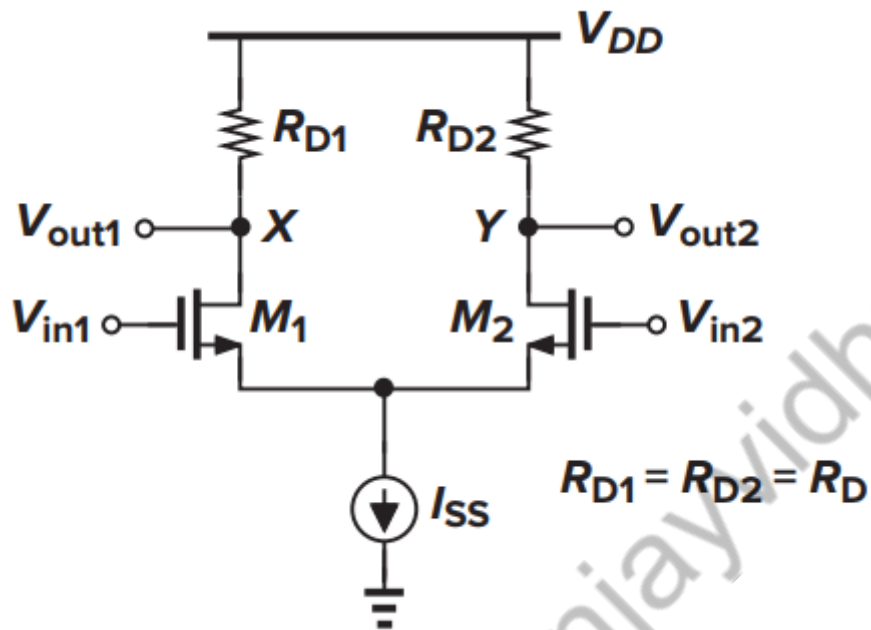



“Current stealing” phenomenon

# MOS Differential Pair

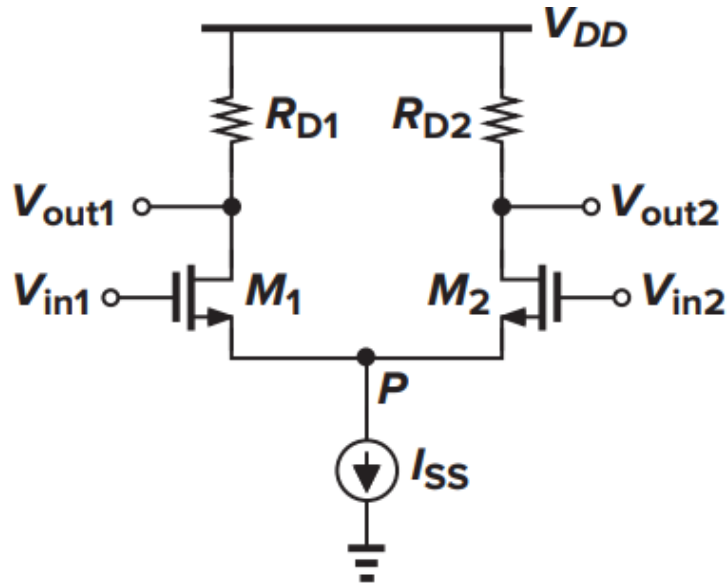
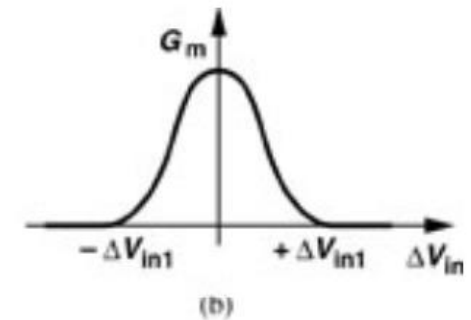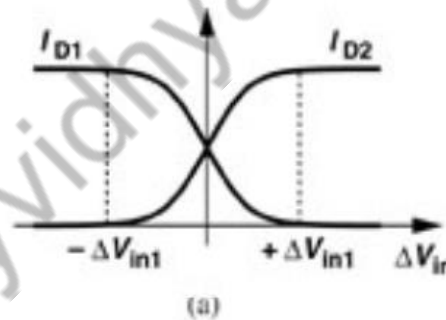
## Differential Transconductance Gain vs. Input Voltage

$$\frac{\partial I_D}{\partial V_{in}} = G_m = \frac{\mu_n C_{ox}}{2} \frac{W}{L} \frac{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - 2(V_{in1} - V_{in2})^2}{\sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2}}$$




**Maximum Differential Transconductance Gain Occurs at  $\Delta V_{in}=0$**

$$g_m = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right) I_D}$$

$$G_{m,max} = \sqrt{\mu_n C_{ox} \left(\frac{W}{L}\right) I_{SS}}$$

# MOS Differential Pair

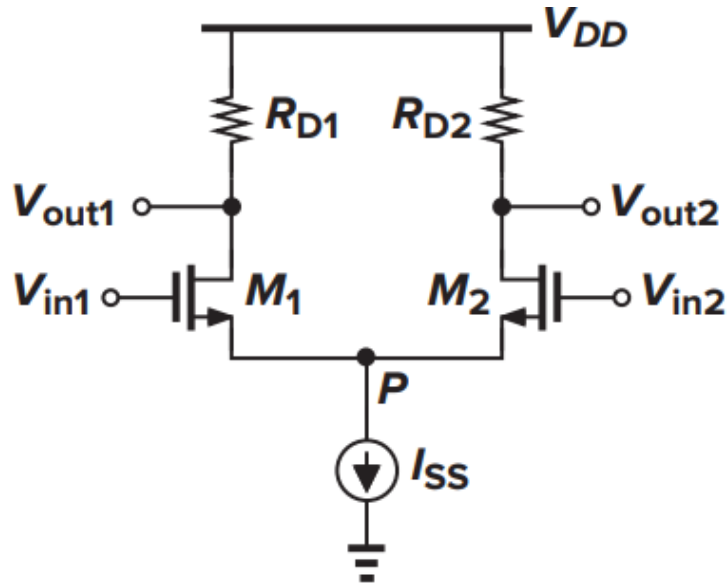

## Differential Voltage Gain

$$V_{out1} - V_{out2} = R_D \Delta I_D = R_D G_m \Delta V_{in}$$



## Differential Voltage Gain near $\Delta V_{in} = 0$

$$|A_v| = \frac{\Delta V_{out}}{\Delta V_{in}} = G_{m,max} R_D = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}} R_D$$

Differential Transconductance Gain Falls to Zero at  $\Delta V_{in} = \Delta V_{in1}$

$$\frac{\partial \Delta I_D}{\partial \Delta V_{in}} = G_m = \frac{\mu_n C_{ox}}{2} \frac{W}{L} \frac{\frac{4I_{SS}}{\mu_n C_{ox} W/L} - 2(V_{in1} - V_{in2})^2}{\sqrt{\frac{4I_{SS}}{\mu_n C_{ox} W/L} - (V_{in1} - V_{in2})^2}}$$

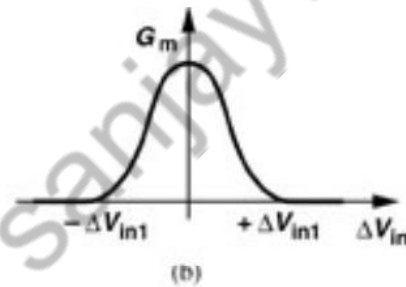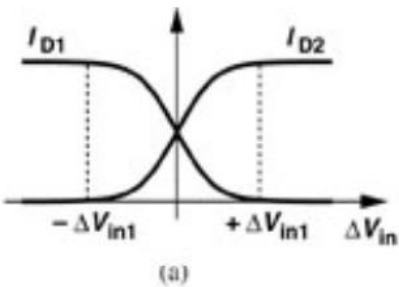
$$\Delta V_{in1} = \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$



$\Delta V_{in} = \Delta V_{in1}$  is the maximum differential input that the amplifier can “handle”


# The “Virtual Ground” Concept

## The “Half-Circuit” Concept

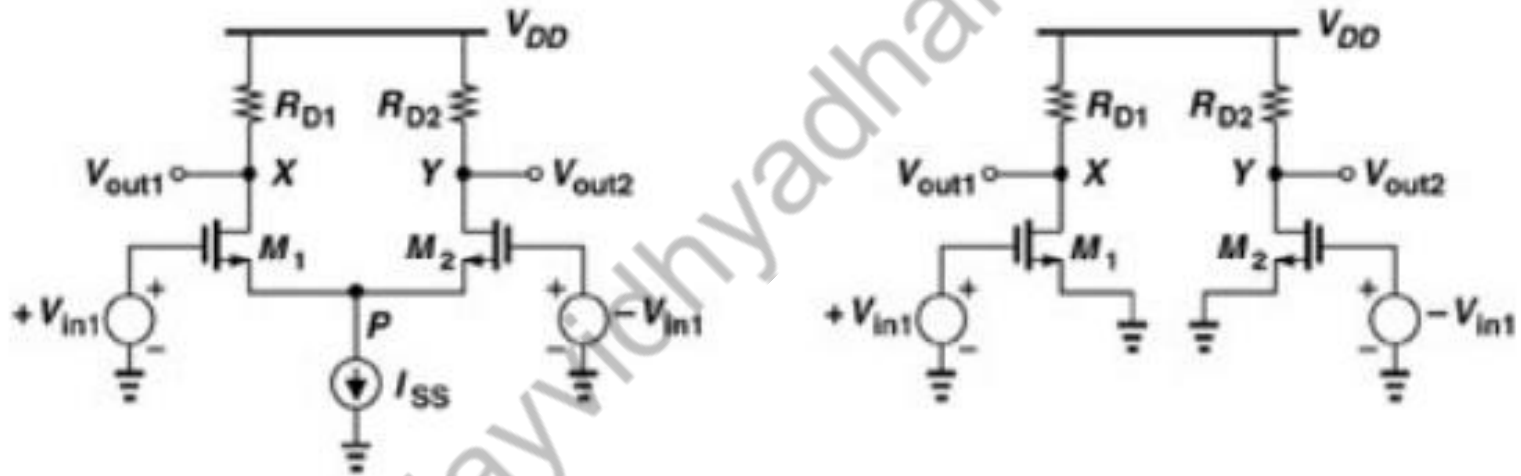
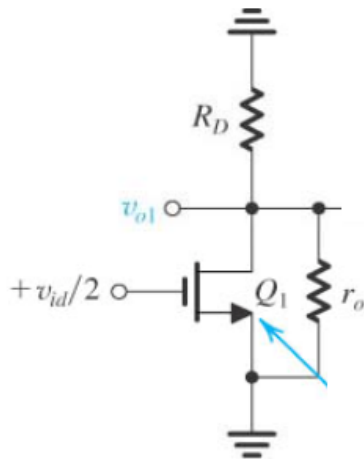
# Differential Mode Response

Differential-mode small-signal half-circuit



$$\frac{v_{o1}}{v_{id}/2} = -g_m(R_D \parallel r_o)$$

For the total circuit

$$v_{od} = v_{o1} - v_{o2}$$

$$\text{But } v_{o2} = -v_{o1}$$


$$\therefore v_{od} = 2v_{o1}$$

**CS amplifier for input difference!**

$$A_d = \frac{v_{od}}{v_{id}} = \frac{2v_{o1}}{v_{id}} = -g_m(R_D \parallel r_o)$$

# MOS Differential Pair


## Common-Mode

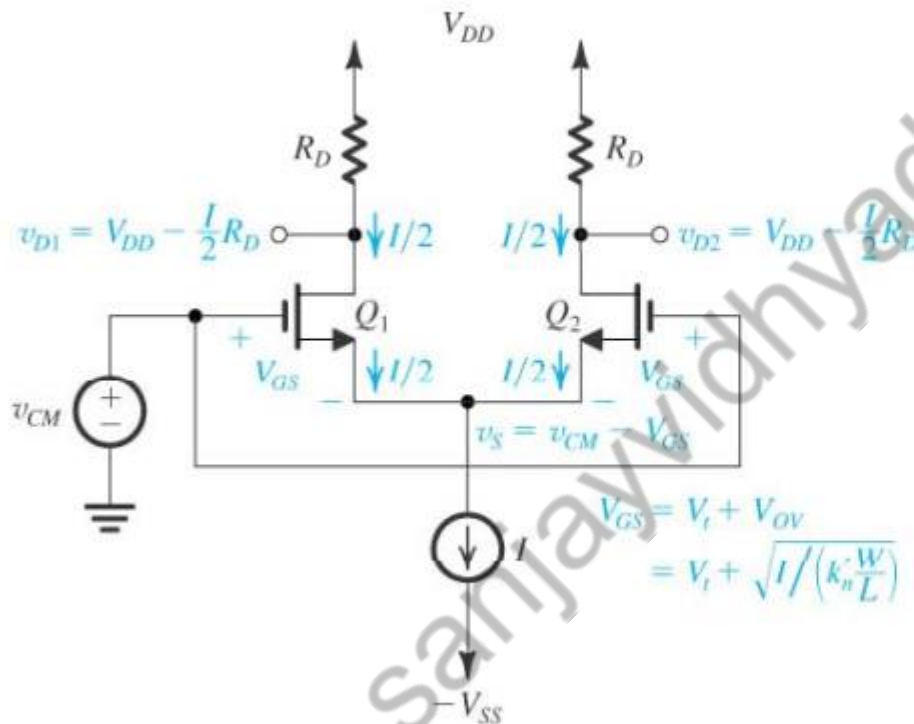

$$\text{CMRR} = \text{????}$$

# MOS Differential Pair

## Common-Mode

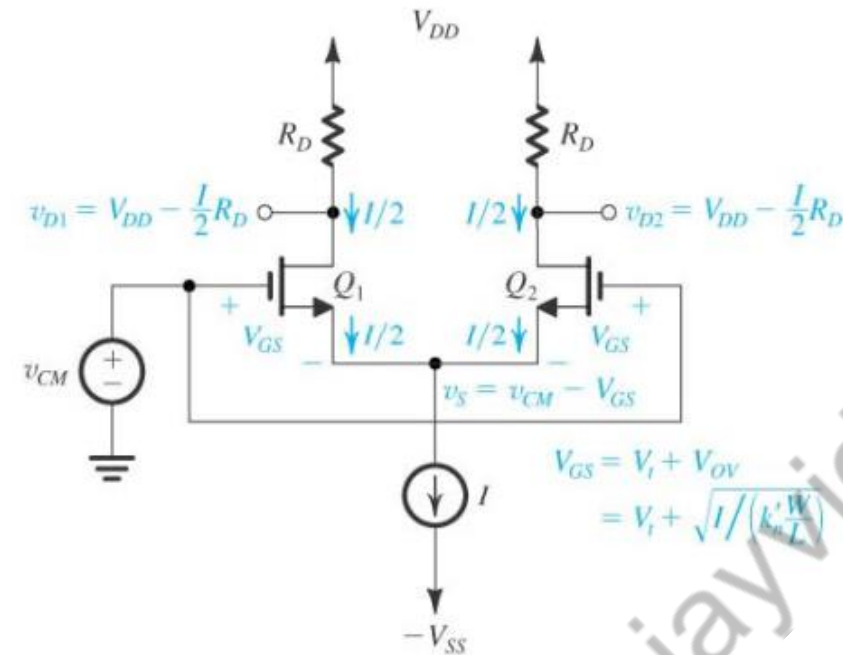

$V_{CM, \max}$ ?

$$v_{DS} \geq v_{GS} - V_t$$

$$(V_{DD} - \frac{I}{2}R_D) - (V_{CM} - v_{GS}) \geq v_{GS} - V_t$$

$$\therefore V_{DD} - \frac{I}{2}R_D + V_t \geq V_{CM}$$

$$V_{CM, \max} = V_{DD} - \frac{I}{2}R_D + V_t$$

How to  
Maximise ?






If a voltage  $V_{CS}$  is needed across the current source, then

$$V_{CM, \min} = -V_{SS} + V_{CS} + V_t + V_{OV}$$



How to  
Minimise ?



# Common-Mode Response

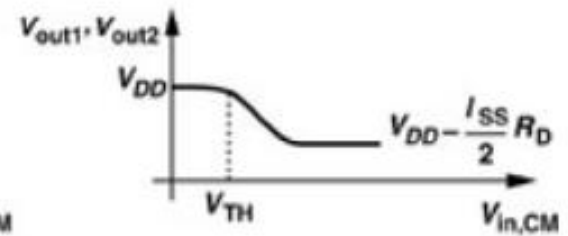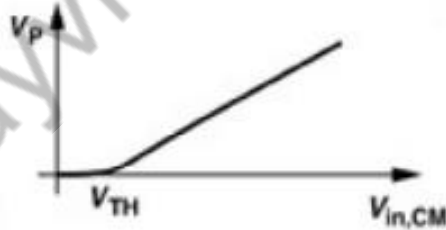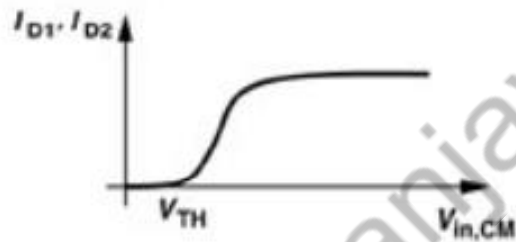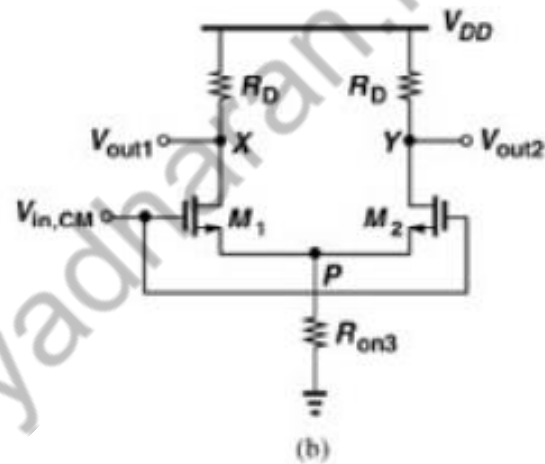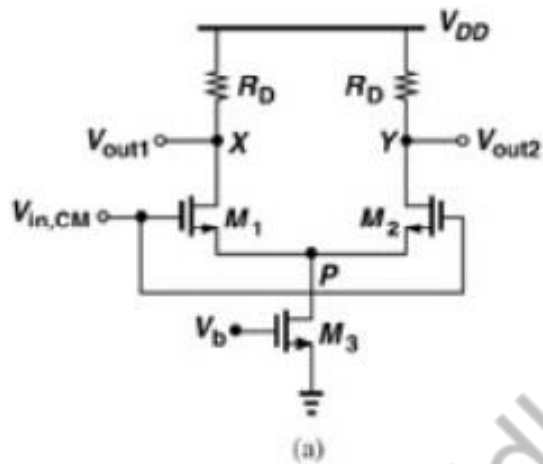

# Common-Mode Response

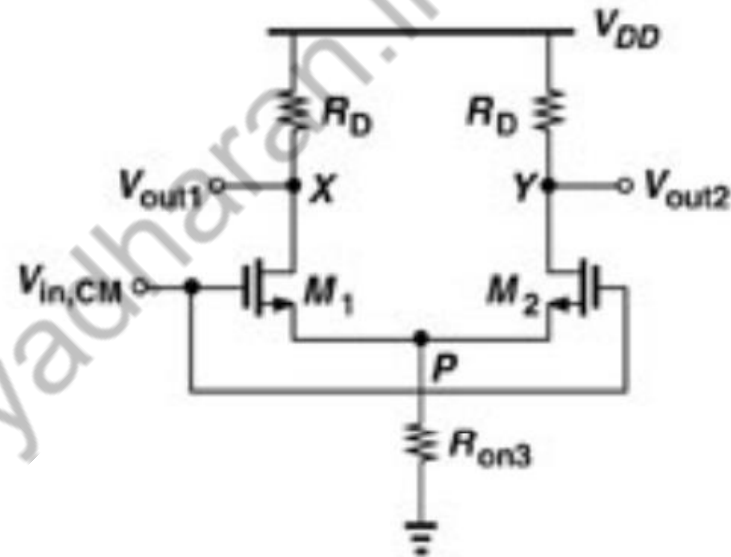
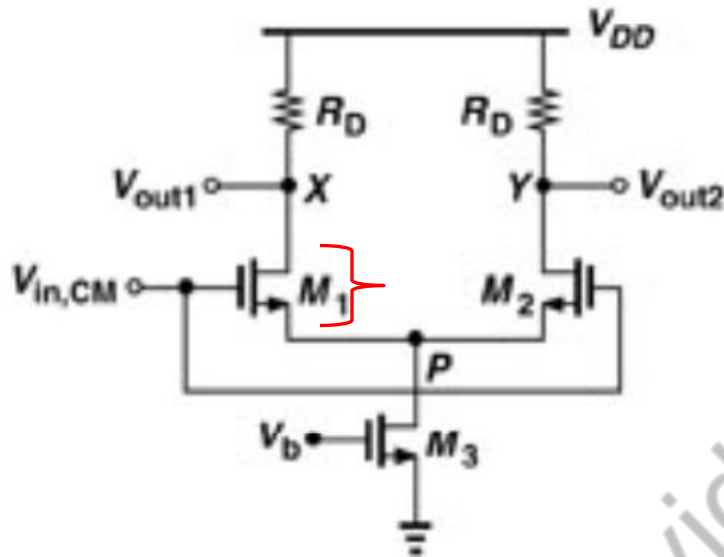


$$V_{GS1} + (V_{GS3} - V_{TH3}) \leq V_{in,CM} \leq \min[V_{DD} - R_D \frac{I_{SS}}{2} + V_{TH1}, V_{DD}]$$

Input common-mode range (*ICMR*) The input common-mode range is the range of common-mode voltages over which the differential amplifier continues to sense and amplify the difference signal with the same gain.

Typically, the *ICMR* is defined by the common-mode voltage range over which all MOSFETs remain in the saturation region

# CS stage with Source Degeneration.

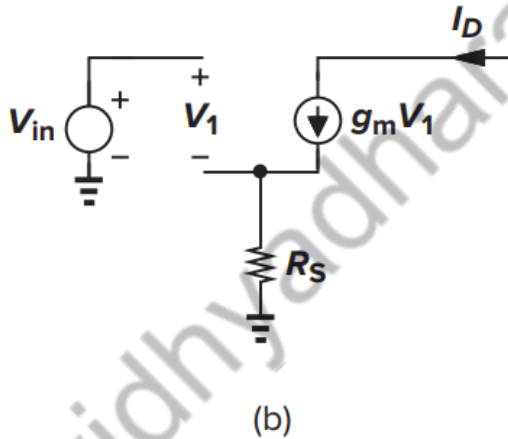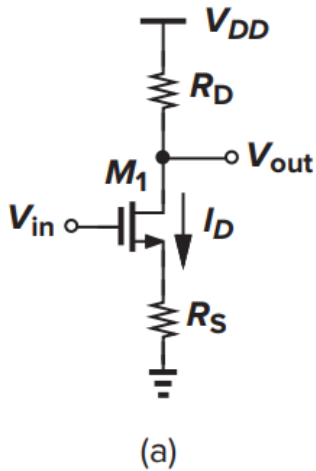

$$v_{in} = v_{gs} + i_d R_S$$

$$v_{in} = v_{gs} + g_m v_{gs} R_S$$

$$v_{in} = v_{gs} (1 + g_m R_S)$$

$$v_{out} = -i_d R_D$$


$$v_{out} = -v_{gs} g_m R_D$$

$$Gain = \frac{-g_m R_D}{1 + g_m R_S}$$

$$Gain = \frac{-R_D}{\frac{1}{g_m} + R_S}$$

# Common-Mode Response

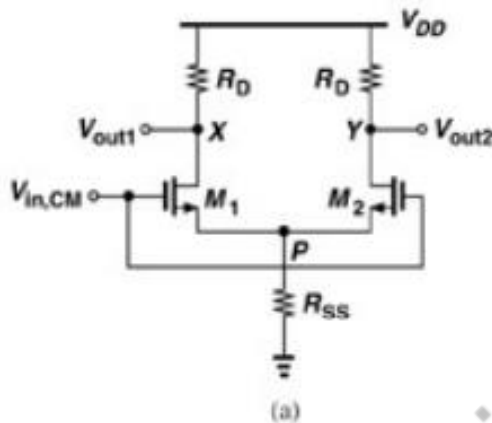
## Single-ended Common-Mode Response of a symmetric amplifier



As  $V_{in,CM}$  changes so does  $V_P$ . As a result,  $I_D$  currents change and  $V_X$  and  $V_Y$  change.  $V_X - V_Y$  continues to be zero

$$A_{V,CM} = \frac{V_{out}}{V_{in,CM}} = \frac{V_X}{V_{in,CM}} = \frac{V_Y}{V_{in,CM}}$$


$$= -\frac{R_D / 2}{1/(2g_m) + R_{SS}}$$

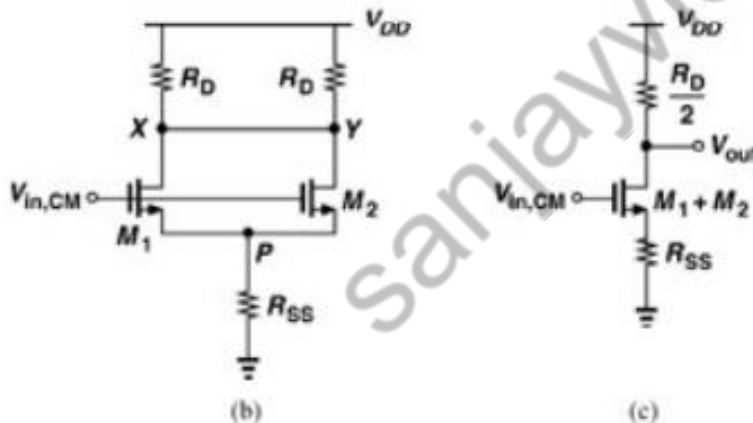

*How to Minimize  $A_{CM}$ ?*

# Example

## “Resistor current source” example

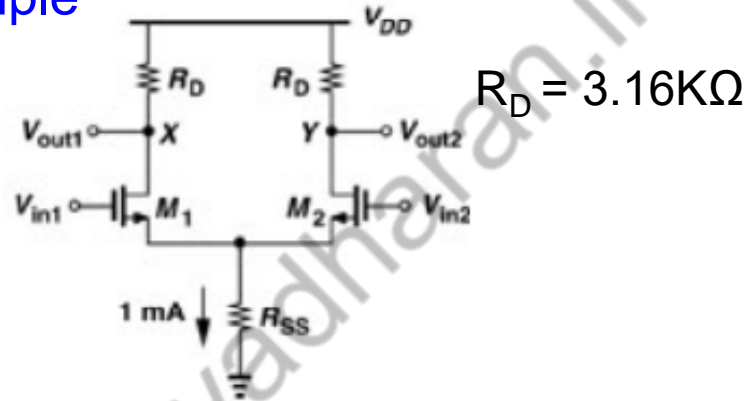


- Example: Let  $V_{DD}=3V$ ,  $(W/L)_1=(W/L)_2=25/0.5$
- $\mu_n C_{OX}=50\mu A/V^2$ ,  $V_{TH}=0.6V$ ,  $\lambda=0$ ,  $\gamma=0$ ,  $R_{SS}=500\Omega$
- Because  $I_{D1}=I_{D2}=0.5mA$ , we have:

$$V_{GS1} = V_{GS2} = \sqrt{\frac{2I_{D1}}{\mu_n C_{OX} \frac{W}{L}}} + V_{TH} = 1.23V$$

- Also:  $V_S = I_{SS} R_{SS} = 0.5V$
- Bias voltage at gates  $V_{in,CM} = V_{GS1} + V_S = 1.73V$

# Example

## “Resistor current source” example

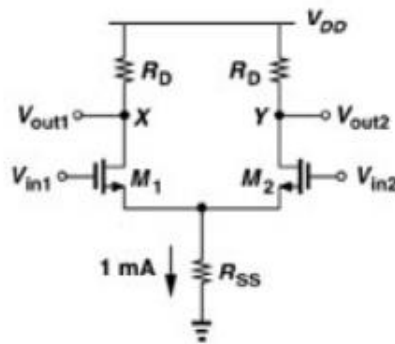

$$R_D = 3.16 \text{ K}\Omega$$

$$g_m = \sqrt{2\mu_n C_{OX} \frac{W}{L} I_{D1}} = \frac{1}{632 \Omega} \quad g_m = \sqrt{(2 * 50 * 10^{-6} * \frac{25}{0.5} * 0.5 * 10^{-3})}$$


Hence differential voltage gain =  $g_m R_D = 5$

$$V_{\text{out1}} = V_{\text{out2}} = V_{DD} - I_D R_D = 1.42 \text{ V} > V_{GS} - V_{TH}$$

$$V_{GS} - V_{TH} = 1.23 - 0.6 = 0.63 \text{ V (the overdrive)} \quad \text{What is max CM Voltage?}$$

# Example

“Resistor current source” example

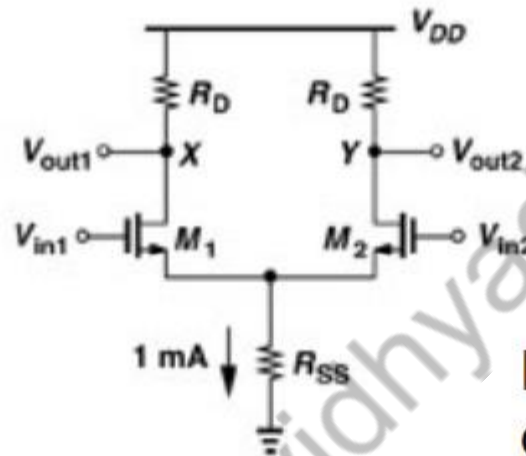

$$R_D = 3.16 \text{ K}\Omega$$


$$A_{V,CM} = \frac{\Delta V_{out}}{\Delta V_{in,CM}} = - \frac{R_D / 2}{1/(2g_m) + R_{SS}}$$

Large CM gain of 1.94 is due to the small  $R_{SS}$

$$\text{CMRR} = 5 / 1.94 = 51.7$$
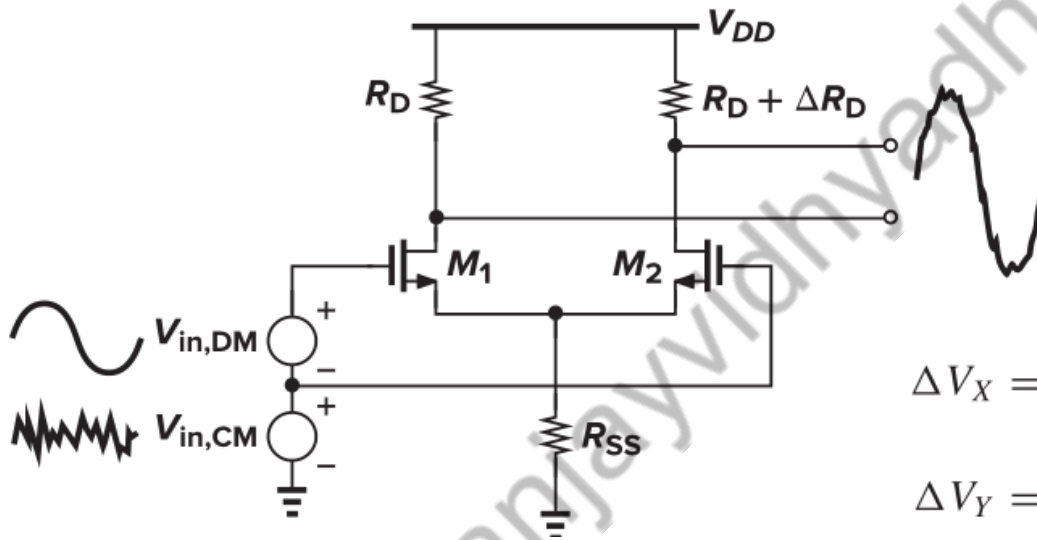
# Common-Mode Response

Common-mode response in the presence of resistor mismatch.



$$\Delta V_X = -\Delta V_{in,CM} \frac{g_m}{1 + 2g_m R_{SS}} R_D$$


$$\Delta V_Y = -\Delta V_{in,CM} \frac{g_m}{1 + 2g_m R_{SS}} (R_D + \Delta R_D)$$

$R_{SS}$  should be large for Noise immunity .


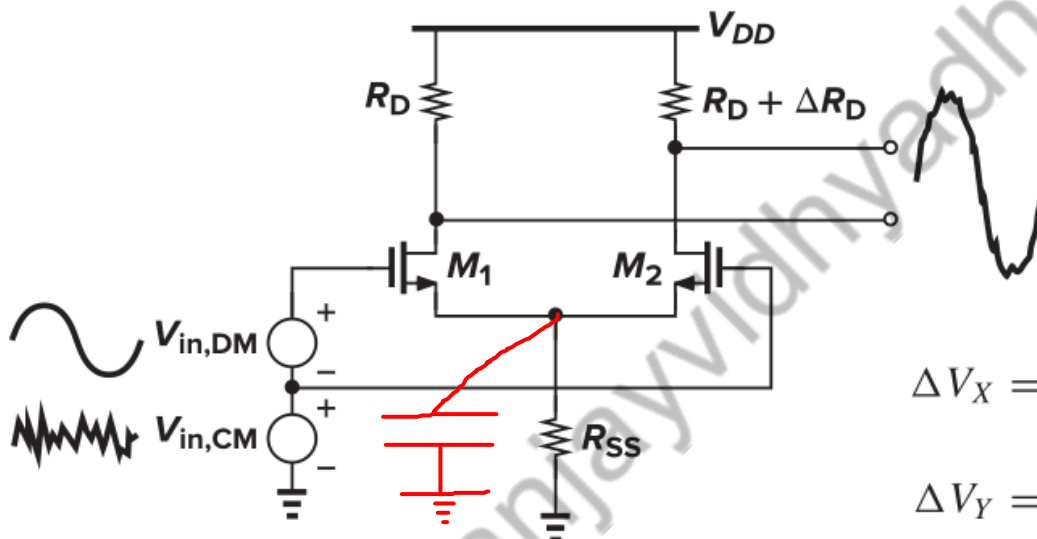
# Common-Mode Response


CM response with finite tail capacitance.



$$\Delta V_X = -\Delta V_{in,CM} \frac{g_m}{1 + 2g_m R_{SS}} R_D$$

$$\Delta V_Y = -\Delta V_{in,CM} \frac{g_m}{1 + 2g_m R_{SS}} (R_D + \Delta R_D)$$


# Common-Mode Response

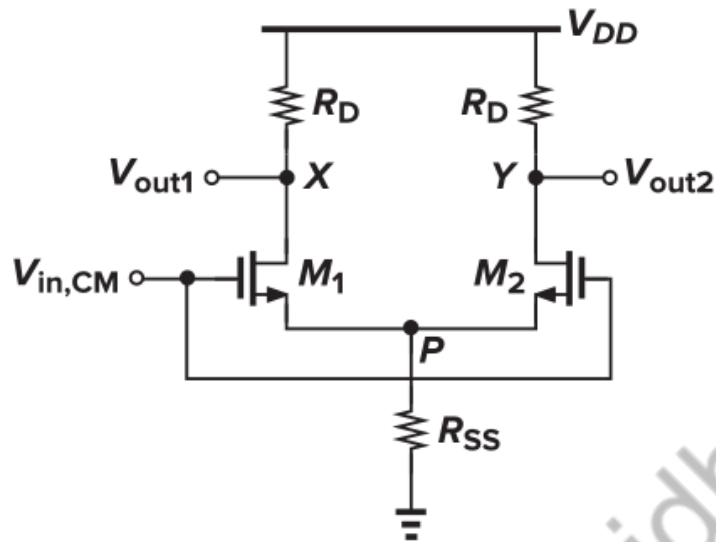

$$V_X = -g_{m1}(V_{in,CM} - V_P)R_D$$

$$= \frac{-g_{m1}}{(g_{m1} + g_{m2})R_{SS} + 1} R_D V_{in,CM}$$
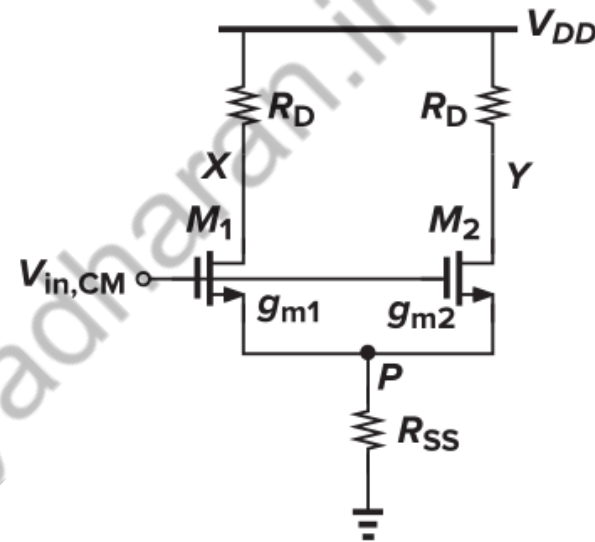
$$V_X - V_Y = -\frac{g_{m1} - g_{m2}}{(g_{m1} + g_{m2})R_{SS} + 1} R_D V_{in,CM}$$





$$V_Y = -g_{m2}(V_{in,CM} - V_P)R_D$$

$$= \frac{-g_{m2}}{(g_{m1} + g_{m2})R_{SS} + 1} R_D V_{in,CM}$$


$$A_{CM-DM} = -\frac{\Delta g_m R_D}{(g_{m1} + g_{m2})R_{SS} + 1}$$

A CM-DM denotes common-mode to differential-mode conversion

# Degenerated Differential Pairs

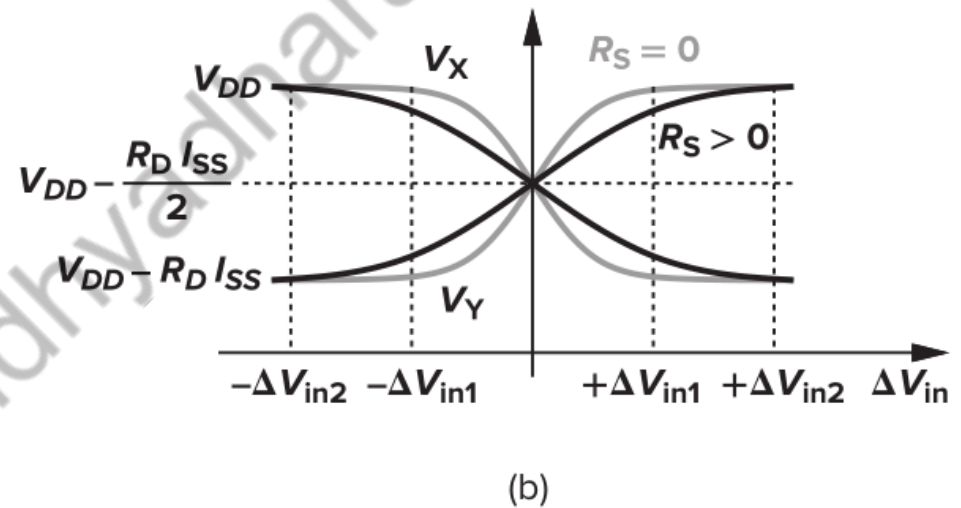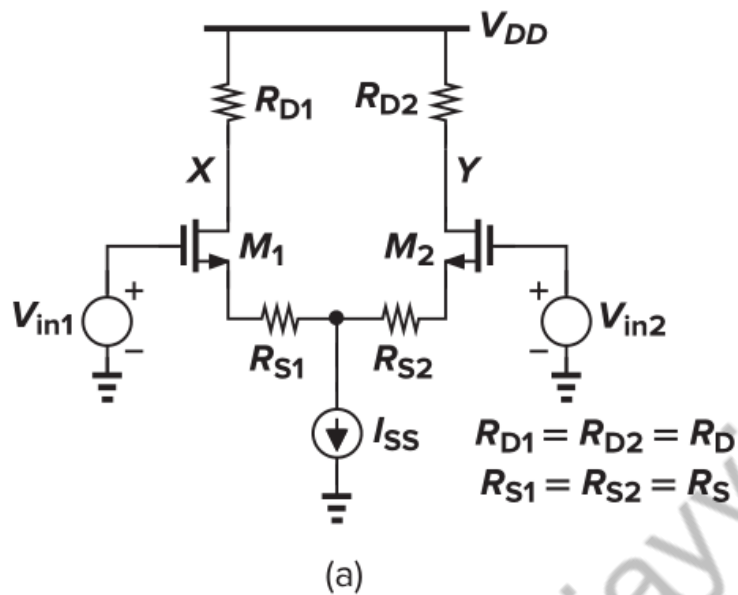

# Degenerated Differential Pairs

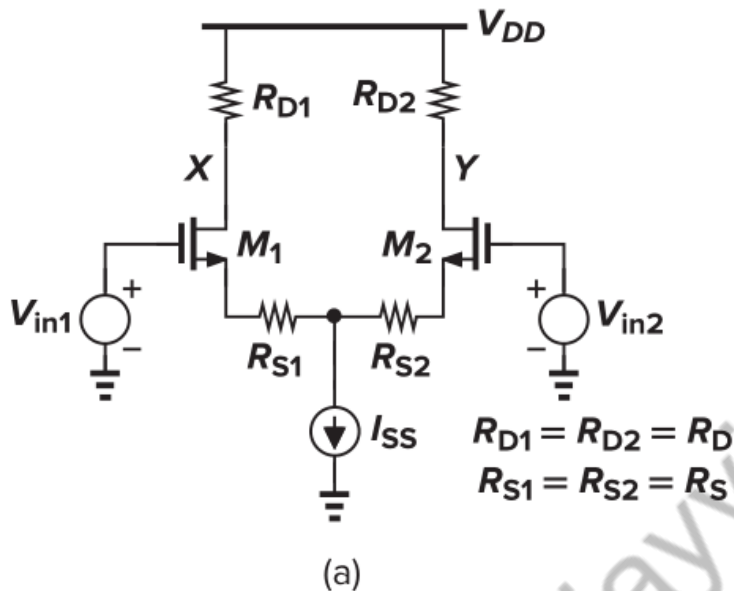

$$V_{in1} - V_{GS1} - R_S I_{SS} = V_{in2} - V_{TH}$$

$$V_{in1} - V_{in2} = V_{GS1} - V_{TH} + R_S I_{SS}$$

$$= \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} + R_S I_{SS}$$

$$\Delta V_{in2} - \Delta V_{in1} = R_S I_{SS}$$

*Guess the Drawback*


$$|A_v| = \frac{R_D}{\frac{1}{g_m} + R_S}$$

Trades gain for linearity

Each resistor sustains a voltage drop of  $R_S I_{SS}/2$
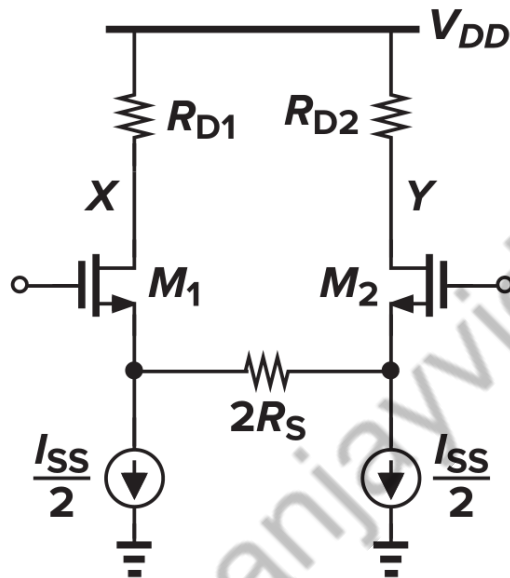
# Degenerated Differential Pairs

Degenerated differential pair with split tail current source.



**Thank you**