




Analog IC Design : 2022-23
Lecture 8
DC Voltage and DC Current Sources
Part-2

By Dr. Sanjay Vidhyadharan

Current Mirrors


NMOS Current Mirror

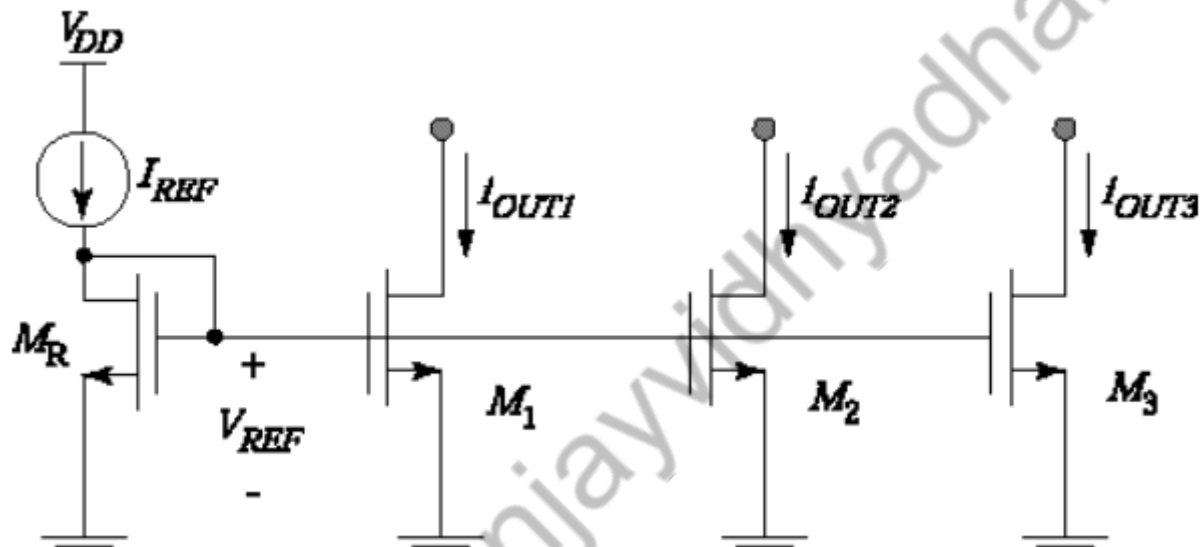

$$I_{OUTn} = I_{REF} \frac{\left(\frac{W}{L}\right)_n}{\left(\frac{W}{L}\right)_R}$$


Current Mirrors

PMOS Current Mirror

 

$$I_{OUTn} = I_{REF} \frac{\left(\frac{W}{L}\right)_n}{\left(\frac{W}{L}\right)_R}$$

Current Mirrors

 


$$I_{OUT1} = I_{REF} \frac{\left(\frac{W}{L}\right)_1}{\left(\frac{W}{L}\right)_R}$$

$$I_{OUT2} = I_{REF} \frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_R}$$

$$I_{OUT4} = I_{OUT1} \frac{\left(\frac{W}{L}\right)_4}{\left(\frac{W}{L}\right)_3} = I_{REF} \frac{\left(\frac{W}{L}\right)_4}{\left(\frac{W}{L}\right)_3} \frac{\left(\frac{W}{L}\right)_1}{\left(\frac{W}{L}\right)_R}$$

Generating I_{REF}

 

$$I_{REF} = \frac{V_{DD} - V_{OUT}}{R}$$

$$V_{OUT} = V_{Tn} + \sqrt{\frac{I_{REF}}{\frac{W}{2L} \mu_n C_{ox}}}$$

For large W/L :

$$I_{REF} \approx \frac{V_{DD} - V_{Tn}}{R}$$

Advantages

- I_{REF} set by value of resistor


Disadvantages

- V_{DD} also affects I_{REF} .

- V_{Tn} and R are functions of temperature

In the real world, more sophisticated circuits are used to generate I_{REF} that are V_{DD} and T independent.

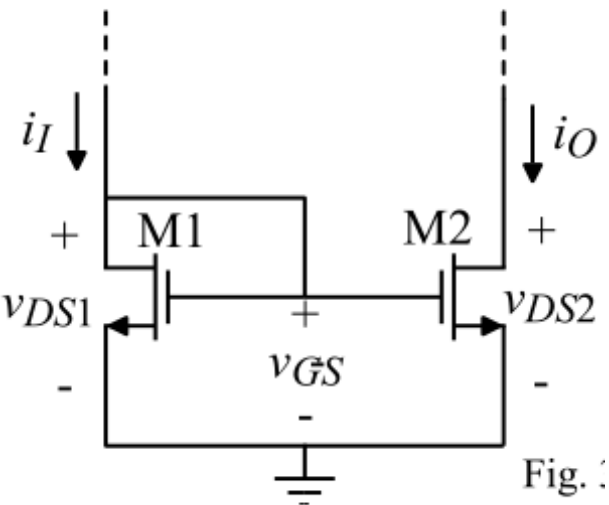Influence of the Channel Modulation Parameter λ



Assume that $v_{DS2} > v_{GS} - V_{T2}$, then

$$\frac{i_O}{i_I} = \left(\frac{L_1 W_2}{W_1 L_2} \right) \left(\frac{V_{GS} - V_{T2}}{V_{GS} - V_{T1}} \right)^2 \left[\frac{1 + \lambda v_{DS2} \left(\frac{K_2'}{K_1'} \right)}{1 + \lambda v_{DS1} \left(\frac{K_2'}{K_1'} \right)} \right]$$

If the transistors are matched, then $K_1' = K_2'$ and $V_{T1} = V_{T2}$

$$\frac{i_O}{i_I} = \left(\frac{L_1 W_2}{W_1 L_2} \right) \left(\frac{1 + \lambda v_{DS2}}{1 + \lambda v_{DS1}} \right)$$



If $v_{DS1} = v_{DS2}$, then

$$\frac{i_O}{i_I} = \left(\frac{L_1 W_2}{W_1 L_2} \right)$$


Therefore the sources of error are:

  - 1.) $v_{DS1} \neq v_{DS2}$
- 2.) M1 and M2 are not matched.

Common centroid design evens out the effect of the process variation.



 Common centroid design evens out the effect of the process variation.



Current Mirror Analysis

- As $V_{GS1} = V_{GS2}$ and assuming matched $V_{TH1} = V_{TH2}$


$$\frac{I_{OUT}}{I_{IN}} = \frac{\left(\frac{W}{L}\right)_2 (1 + \lambda V_{OUT})}{\left(\frac{W}{L}\right)_1 (1 + \lambda V_{IN})}$$

- The output resistance of current source is the output resistance of M2

$$R_O = \frac{1}{\lambda I_{D2}} = \frac{1}{\lambda I_{OUT}}$$

- Normally, larger L is used so that λ effect is reduced and the output resistance is higher.
- The current gain systematic error is:
 
$$E = \frac{I_{OUT} - I_{OUT_ideal}}{I_{OUT_ideal}} = \frac{(1 + \lambda V_{OUT})}{(1 + \lambda V_{IN})} - 1 = \frac{\lambda}{(1 + \lambda V_{IN})} (V_{OUT} - V_{IN}) \approx \lambda (V_{OUT} - V_{IN})$$





$$I_{OUT_ideal} = \frac{(W/L)_2}{(W/L)_1} I_{IN}$$

Systematic error

Standard Cascode Current Mirror

Output Resistance

  

$$v_{gs2} = 0, v_{gs4} = -i_t r_{o2}$$

$$i_t = \frac{v_t - v_{s4}}{r_{o4}} - g_{m4} i_t r_{o2}$$

$$i_t (1 + g_{m4} r_{o2}) = \frac{v_t - i_t r_{o2}}{r_{o4}}$$

$$R_O = \frac{v_t}{i_t} = r_{o4} (1 + g_{m4} r_{o2}) + r_{o2}$$


$$R_O = g_{m4} r_{o2}^2$$

If body effect is included: $R_O = (g_{m4} + g_{mb}) r_{o2}^2$

Features of Cascode current mirror:

- No current gain systematic error.
- Higher output resistance.
- Higher minimum output voltage.

Standard Cascode Current Mirror

 

All 4 MOSFETs have the same V_{TH} if body effect is ignored.

$$V_X = V_Y = V_{TH} + V_{OV}$$

$V_{GS3} = V_{OV} + V_{TH}$ as M1 and M3 carry the same “I”

$V_{G3} = V_{GS3} + V_X = 2V_{TH} + 2V_{OV}$ ignoring body effect.

$$V_{G4} = 2V_{TH} + 2V_{OV}$$

This should also be the case with body effect – only $2V_{TH}$ will become $V_{TH1} + V_{TH3}$.

$$\text{Min } V_{out} = V_X + V_{OV} = V_{TH} + 2V_{OV}$$

Note V_{OV} of M1 and M2 will equal


$$V_Y = V_T + V_{OV}$$

No Systematic error

Triple Cascode Current Mirror

A variation of this circuit known as triple Cascode current mirror where a device is added on the left and right is also possible. R_O in this case will be
 
$$\begin{aligned}
 R_O &= r_{o6} \left\{ 1 + g_{m6} [r_{o4} (1 + g_{m4} r_{o2}) + r_{o2}] \right\} \\
 &\quad + r_{o4} (1 + g_{m4} r_{o2}) + r_{o2} \\
 &= g_{m6} g_{m4} r_o^3 \\
 &\approx r_o (g_m r_o)^2
 \end{aligned}$$



Low Voltage Cascode Current Source 1

All transistors have the same overdrive except M3. $V_X = V_{TH} + V_{OD}$

Since $W_3 = 1/4 W_1$,
$$I_{REF} = \frac{1}{2} \mu C_{OX} \frac{1}{4} \left(\frac{W}{L} \right) (V_{GS3} - V_{TH})^2 = \frac{1}{2} \mu C_{OX} \left(\frac{W}{L} \right) V_{OD}^2$$

$$V_{GS3} = V_{TH} + 2V_{OD} \rightarrow V_{G3} = V_X + V_{GS3} = 2V_{TH} + 3V_{OD}$$

$$V_{G4} = V_{TH} + 2V_{OD} \rightarrow$$


$$V_Y = V_{OD}$$

$$V_{Omin} = 2V_{OD}$$

1. The output resistance remains the same as the Cascode current mirror.

$$2. E \approx \lambda(V_Y - V_X) = -\lambda V_{TH}$$

Gain systematic error is not zero

 

Low Voltage Cascode Current Source 2

All the transistors have the same overdrive. Set $V_B = V_{TH} + 2V_{OD}$

$$V_X = V_Y = V_B - (V_{TH} + V_{OD}) = V_{OD}$$

Then the minimum output voltage is:


$$V_{OUT} = 2V_{OD}$$

And since $V_X = V_Y \rightarrow$
no current gain systematic error.

Design all transistors' overdrive smaller than its V_{TH} .

Since $V_{DS3} = V_{GS1} - V_{DS1} = V_{TH} > V_{OD} \rightarrow$ M3
at saturation region.

 All transistors are at saturation region.



Low Voltage Cascode Current Source 2

- The low voltage cascode current source 2 has:

- High output resistance
- Low output voltage:
 $V_{OUT}=2V_{OD}$
- No current gain systematic error.


- How to generate $V_B=V_{TH}+2V_{OD}$?

- Two ways:

- Assuming same L for all transistors,
- Since $W_B=1/4W_1$ and same current

$$I_{REF} = \frac{1}{2} \mu C_{OX} \frac{1}{4} \left(\frac{W}{L} \right) (V_B - V_{TH})^2 = \frac{1}{2} \mu C_{OX} \left(\frac{W}{L} \right) V_{OD}^2$$

- $V_B=V_{GS1}=V_{TH}+2V_{OD}$

 

Low Voltage Cascode Current Source 2


- Another way to generate V_B :
- All transistor have the same overdrive except M6.
- $V_{DS6} = V_{GS6} - V_{GS7} \rightarrow V_{GS6} = V_{DS6} + V_{GS7}$
- Since $V_{GS7} > V_{TH}$, $V_{DS6} < V_{GS6} - V_{TH} \rightarrow$ linear region
- $V_{GS6} - V_{TH} = V_{DS6} + V_{GS7} - V_{TH} = V_{DS6} + V_{OD}$

$$I_{D6} = \frac{1}{3} \frac{W}{L} \mu C_{OX} \left[(V_{GS6} - V_{TH}) \cdot V_{DS6} - \frac{1}{2} V_{DS6}^2 \right]$$


$$I_{D7} = \frac{1}{2} \frac{W}{L} \mu C_{OX} V_{OD}^2$$

$$I_{D6} = I_{D7} \quad \text{and} \quad V_{GS6} - V_{TH} = V_{DS6} + V_{OD}$$

 - Solve the equations: $V_{DS6} = V_{OD}$
- $V_B = V_{GS5} + V_{DS6} = V_{TH} + 2V_{OD}$



Low Voltage Cascode Current Source 2

 

Full schematic of two types of low voltage Cascode current mirror 2.


Wilson Current Mirror

- Transistor M1 and M2 have the same overdrive:

$$\frac{I_{OUT}}{I_{IN}} = \frac{\left(\frac{W}{L}\right)_2 (1 + \lambda V_Y)}{\left(\frac{W}{L}\right)_1 (1 + \lambda V_X)}$$

- Use feedback to stabilize the output current.
- $V_{OUT} \uparrow \rightarrow I_{OUT} \uparrow \rightarrow V_Y \uparrow \rightarrow V_X \downarrow \rightarrow I_{OUT} \downarrow$
- High output resistance: $g_m r_o^2$
- Minimum output voltage: $V_{TH} + 2V_{OV}$
- Since $V_X \neq V_Y$, the current gain systematic error is not zero.

$$E \approx \lambda(V_Y - V_X)$$

 


Wilson Current Mirror

By adding M3, $V_X = V_Y$, the current gain systematic error is zero.

High output resistance: $g_m r_o^2$


Minimum output voltage: $V_{TH} + 2V_{OV}$

Not good for low-voltage design

 


Biasing Techniques


Simple CS Stage

 

Biasing Techniques

 


(d)

 

(e)


Biasing Techniques

Direct coupling between two stages.

 


Biasing Techniques

CS Stage with Current-Source Load

 


Biasing Techniques

CG Stage with Current-Source Load

 

Biasing Techniques

Source Follower Biasing

 

Thankyou