




VLSI Design: 2022-23
Lecture 11
Arithmetic Circuits: Part-1

By Dr. Sanjay Vidhyadharan

sanjayvidhyadharan.in


np-CMOS or NORA

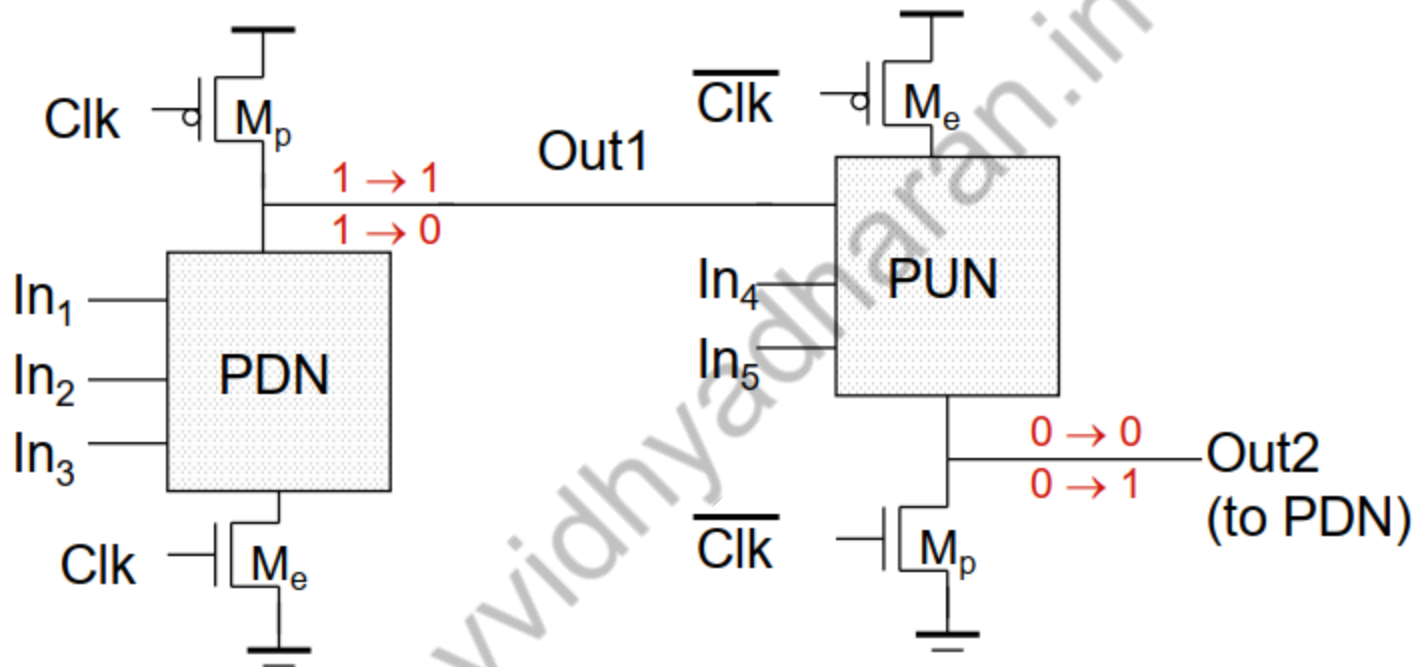


Only 0 → 1 transitions allowed at inputs of PDN
Only 1 → 0 transitions allowed at inputs of PUN

A disadvantage of the *np*-CMOS logic style is that the *p*-tree blocks are slower than the *n*-tree modules, due to the lower current drive of the PMOS transistors in the logic network. Equalizing the propagation delays requires extra area.

np-CMOS

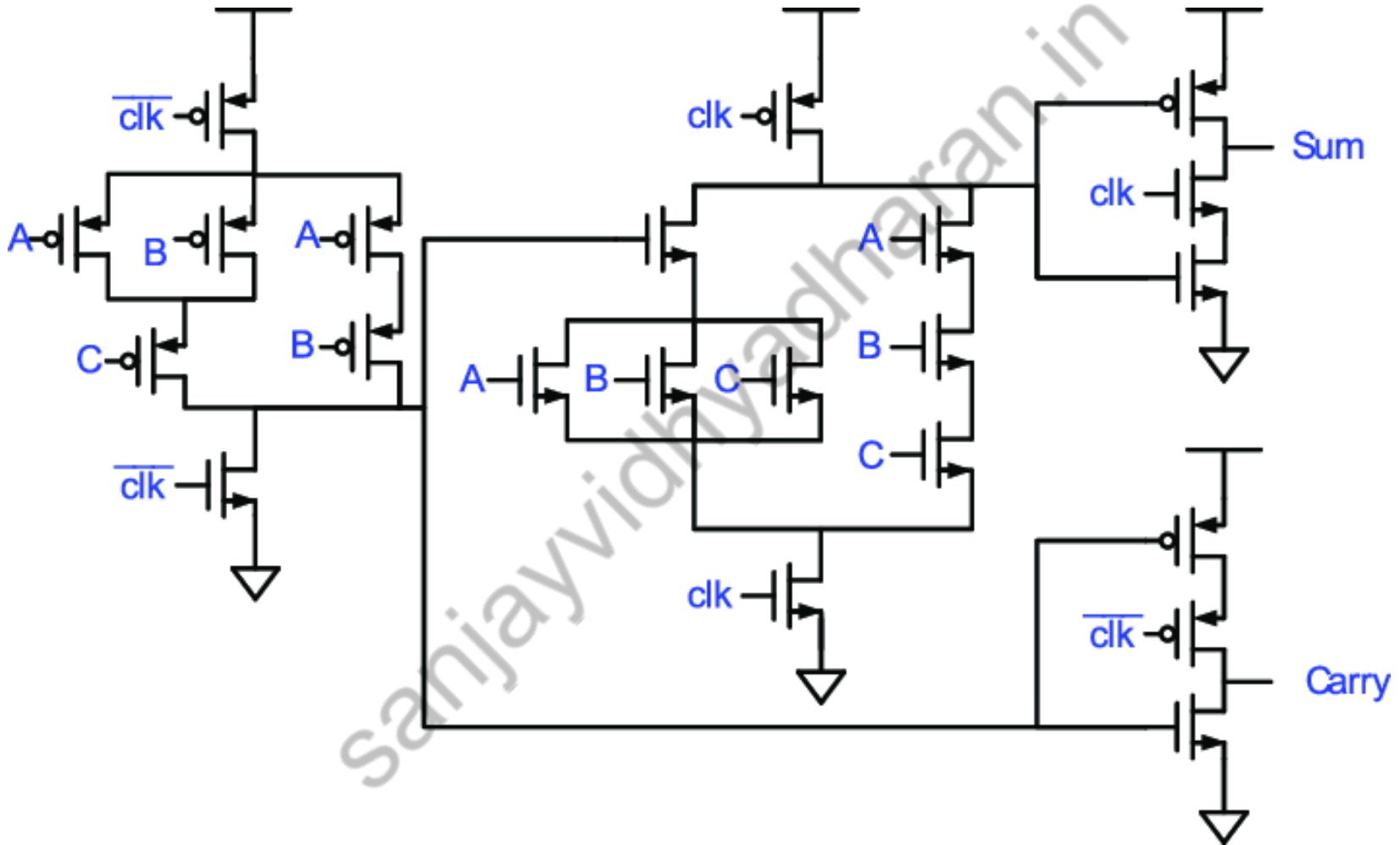


CMOS 28T Mirror Adder

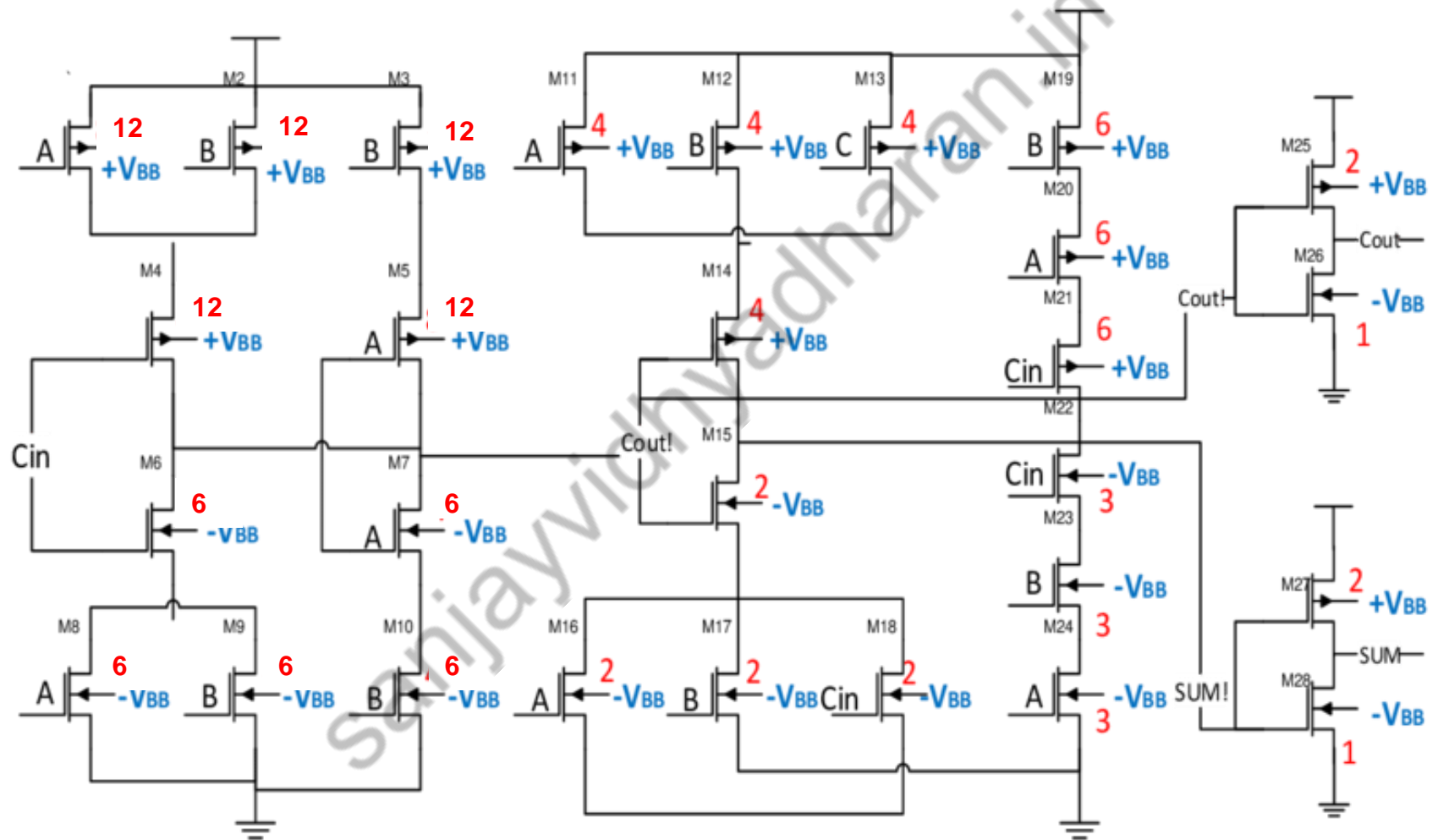

Carry Delay = 2 Gate Delay and Sum = 3 Gate Delays

Ripple Carry Adder

 This is called Ripple Carry Adder, because of the construction with full adders are connected in cascade.




4-bit Ripple Carry Adder

Delay = 3 Carry + 1 Sum = 9 Gate Delays

$$\text{Delay} = (N-1) t_{\text{carry}} + t_{\text{sum}}$$


Carry Look-Ahead Adder

1-bit CLA

 


Carry Look-Ahead Adder

CLA

 


CLLB

 

$$C_1 = G_0 + P_0 C_0$$


Carry Look-Ahead Adder

 



$$C_2 = G_1 + P_1 C_1$$

$$C_2 = G_1 + P_1 (G_0 + P_0 C_0)$$

$$= G_1 + P_1 G_0 + P_1 P_0 C_0$$

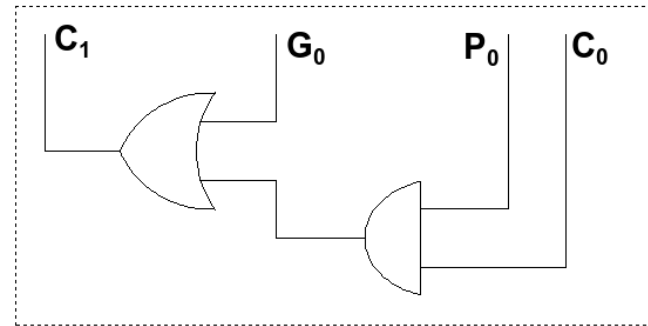

Carry Look-Ahead Adder

  

$$C_2 = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_1 = G_0 + P_0 C_0$$

Carry Look-Ahead Adder




$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

$$C_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$$

Carry Look-Ahead Adder

   


3 Gate Delay for G_3
2 Gate Delay for P_3

4 Gate Delay for C_4
4 Gate Delay for S_3

Carry Look-Ahead Adder


8 Bit Full Adder

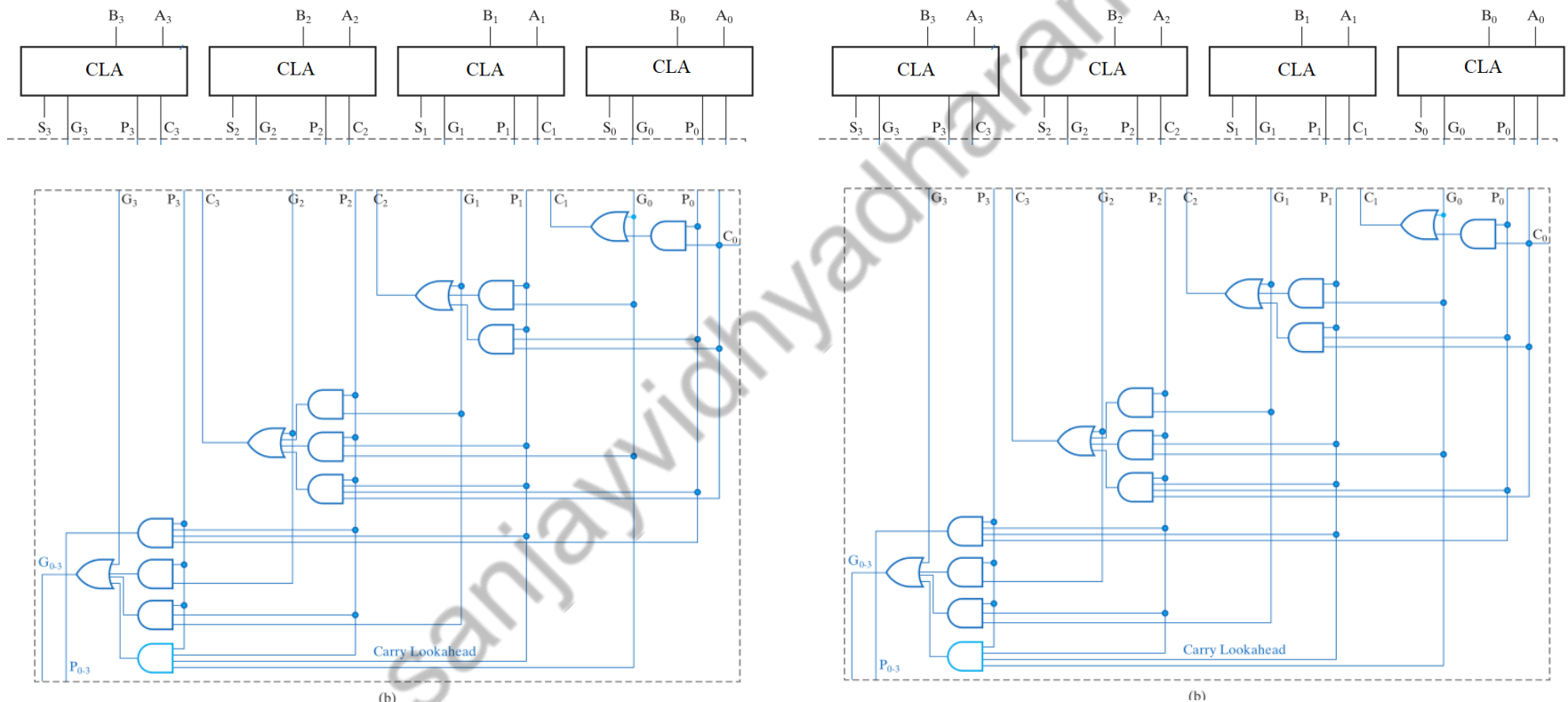

Delay = 4 + 4 = 8 Gate Delay for C₈
 = 4 + 4 = 8 Gate Delay for S₇

Carry Look-Ahead Adder

16 Bit Full Adder

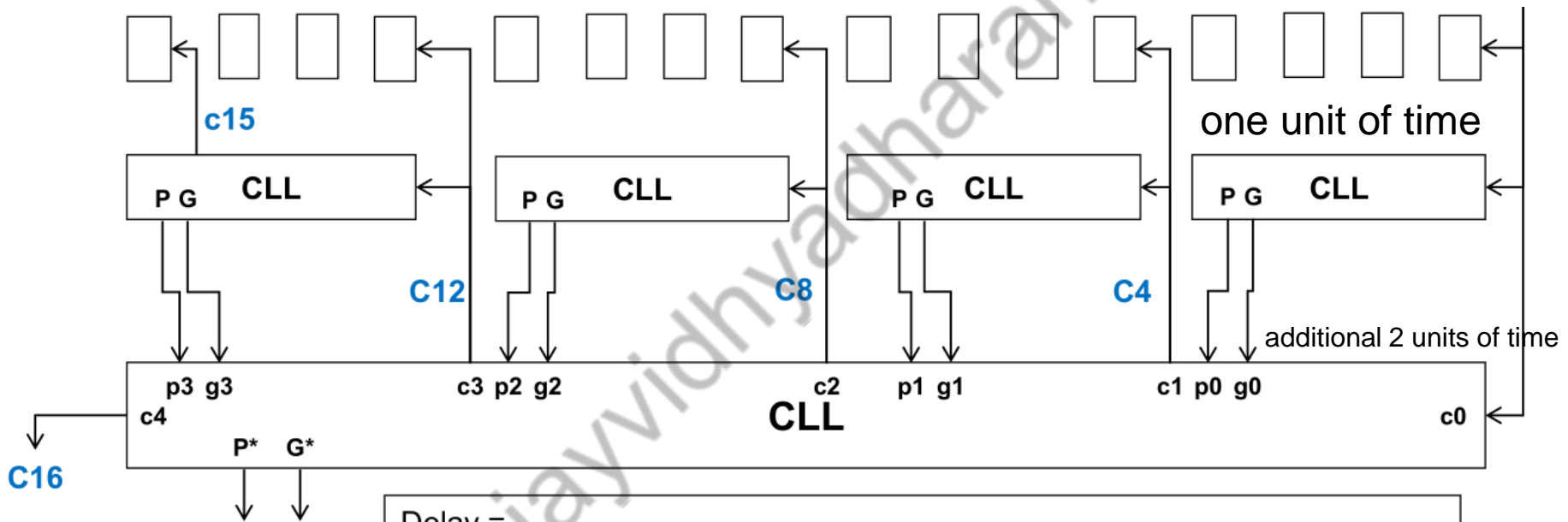

Delay =
 = 3 = Delay in producing P_i, G_i
 = 5 = Delay in producing P_i^*, G_i^*
 = 5 = Delay in producing C_4, C_8, C_{12} **6 Delays for C_{16}**
 = 7 = Delay in producing c_{15}
 = 8 = Delay in producing S_{15}






Carry Look-Ahead Adder

Delay of a k-bit Carry-Lookahead Adder



$$T_{\text{lookahead-adder}} = 4 \lceil \log_4 k \rceil$$

k	$T_{\text{lookahead-adder}}$	$T_{\text{ripple-carry-adder}}$
4	4	8
16	8	32
32	12	64
64	12	128
128	16	256
256	16	512


Carry Look-Ahead Adder

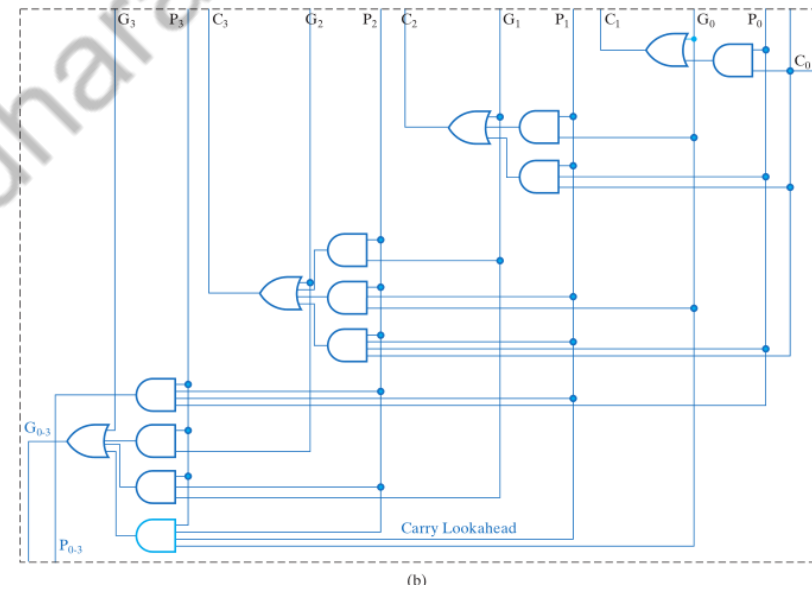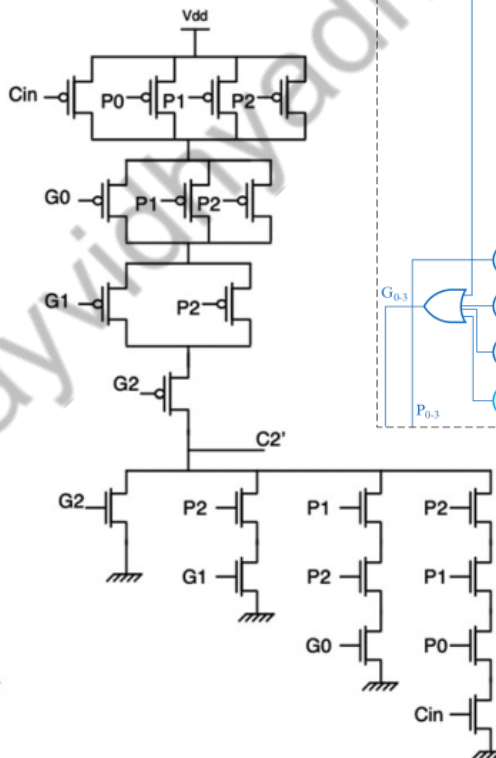   


Carry Look-Ahead Adder

 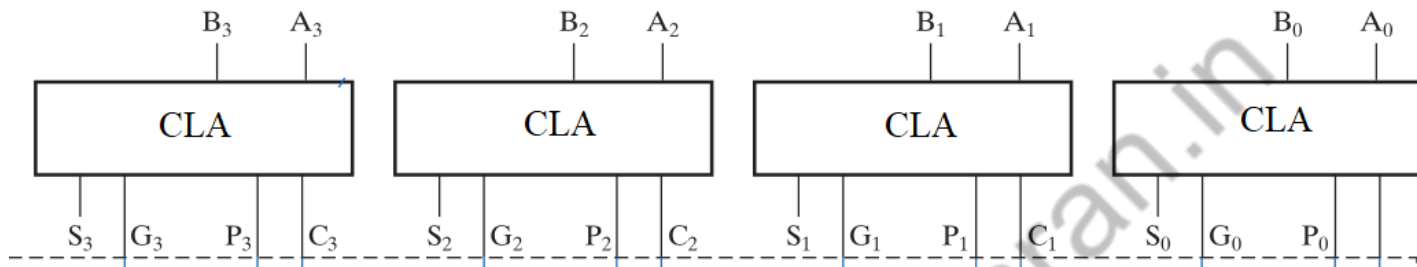


Manchester Carry Chain

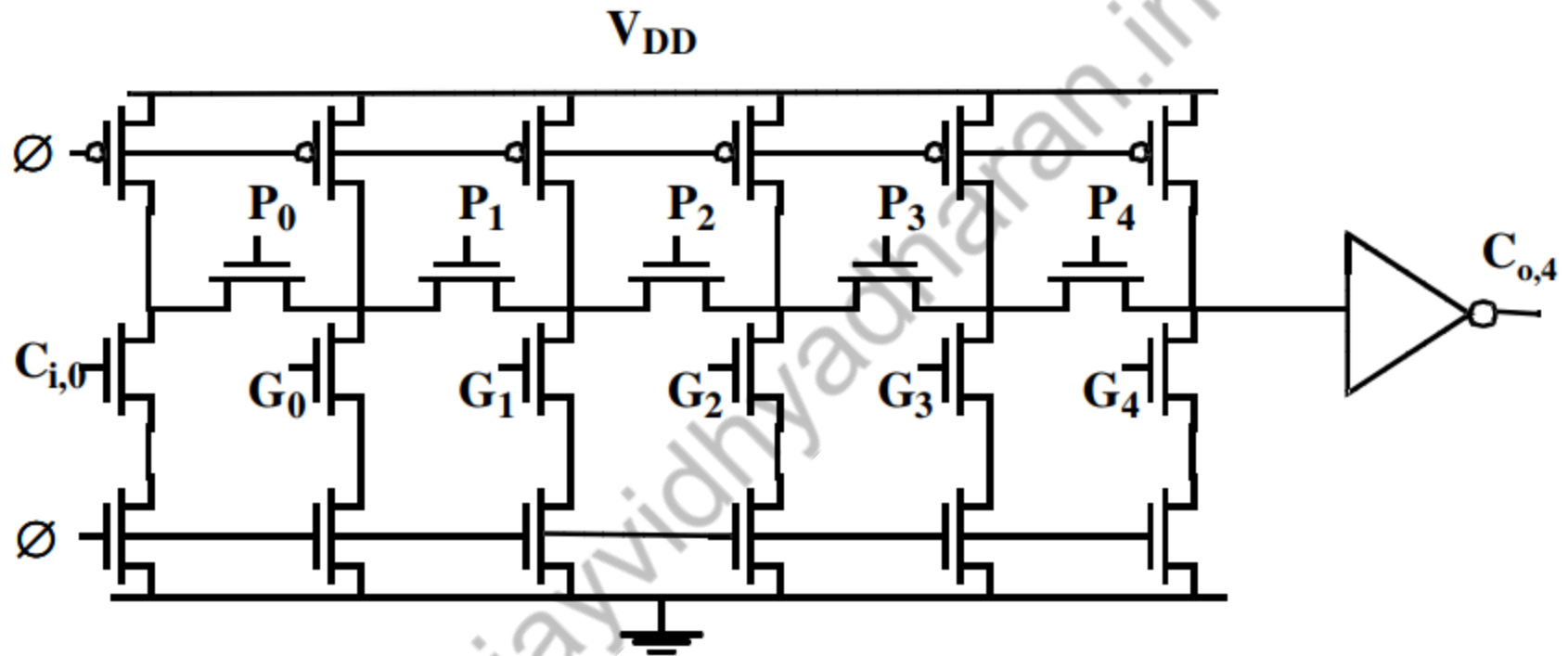

Carry Bypass or Carry Skip Adder

 

Carry Bypass or Carry Skip Adder

 


Design N-bit adder using N/M equal length stages

e.g. N = 16, M = 4


What is the critical path?

$$t_p = t_{\text{setup}} + Mt_{\text{carry}} + (N/M-1)t_{\text{bypass}} + Mt_{\text{carry}} + t_{\text{sum}}, \text{ i.e. } O(N)$$

Carry Ripple versus Carry Bypass

 


Linear Carry-Select Adder

 

$$t_{add} = t_{setup} + \left(\frac{N}{M}\right)t_{carry} + Mt_{mux} + t_{sum}$$

Square Root Carry-Select Adder

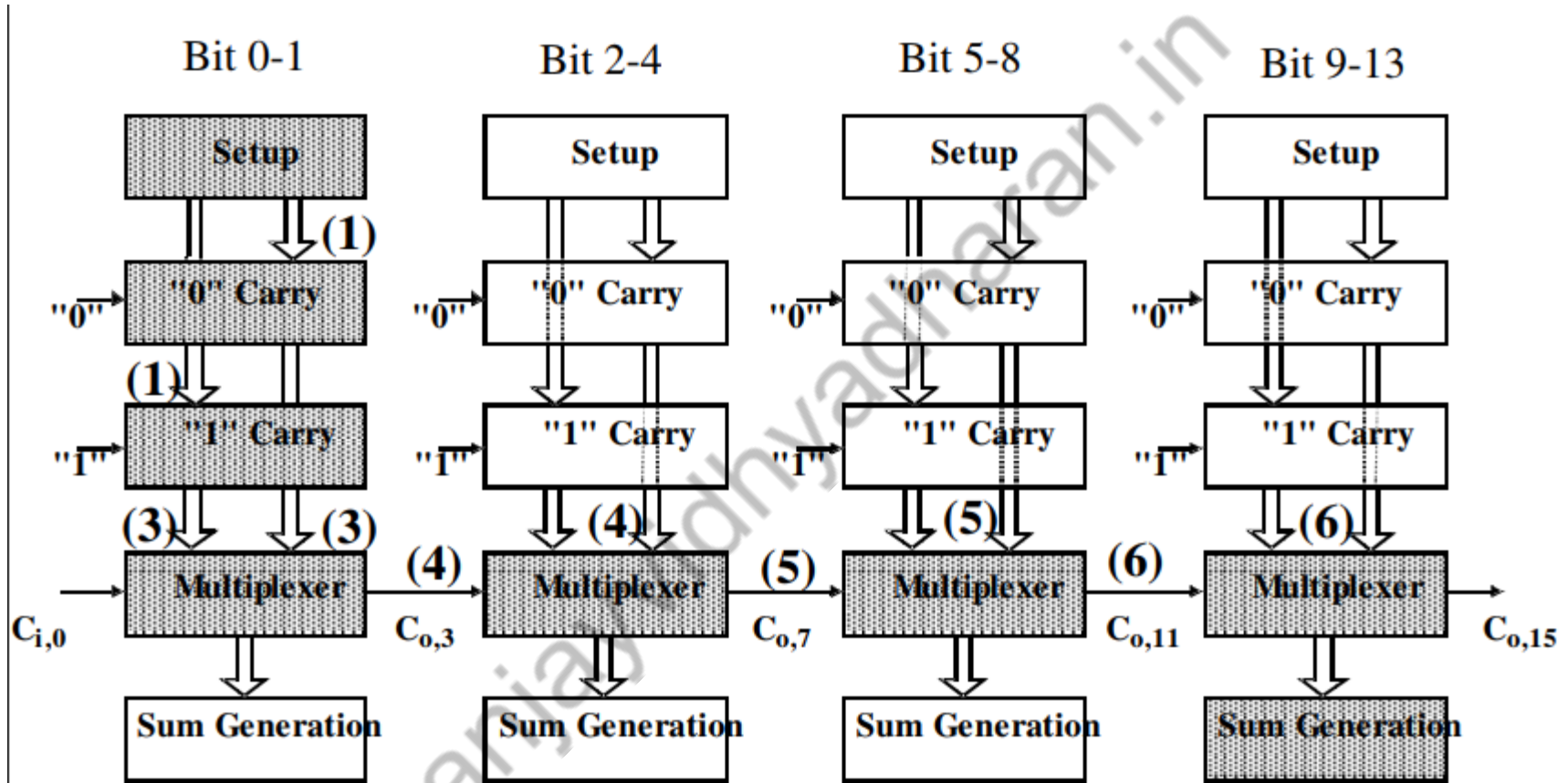

$$t_{add} = t_{setup} + Mt_{carry} + (\sqrt{2N})t_{mux} + t_{sum}$$

Square Root Carry-Select Adder

N Bit adder, M – Bits in First Stage, P – Number of Stages

$$N = M + (M + 1) + (M + 2) + (M + 3) + \dots + (M + P - 1)$$

$$N = MP + \frac{P(P - 1)}{2}$$

$$N = \frac{P^2}{2} + P\left(M - \frac{1}{2}\right)$$


$$M \ll N \text{ (e.g. } M = 2 \text{ and } N = 64)$$

$$N \approx \frac{P^2}{2}$$


Series: $a, a+d, a+2d, \dots, a+(n-1)d$

$$s_n = n/2(2a + (n-1)d)$$


Adder Delays - Comparison

 

Carry Increment Adder

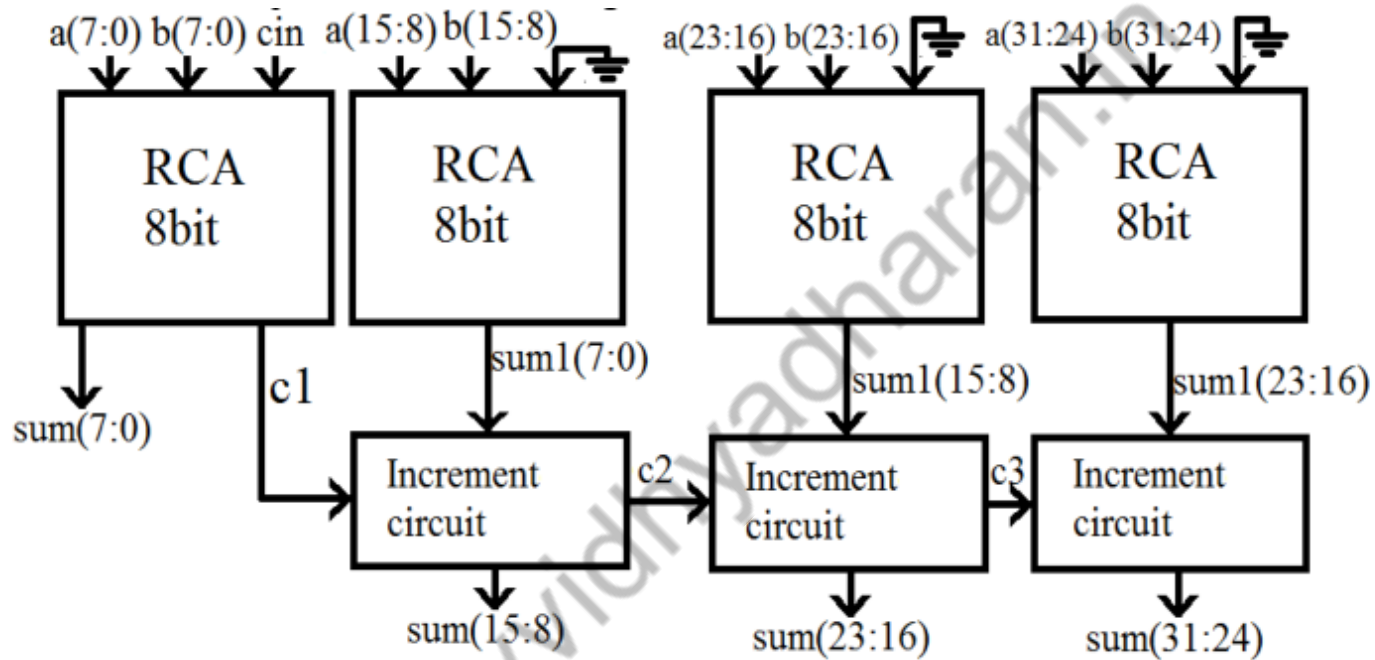

RCA - 65

 


$$CIA-16+8+8+8=40$$


Carry Save Adder

X: 1 0 0 1 : 9
 Y: 1 0 0 1 : 9
 Z: 1 0 1 1 : 11
 S: 1 0 1 1
 C: 1 0 0 1
 Sum: 1 1 1 0 1 : 29

4 Bit Carry Save Adder

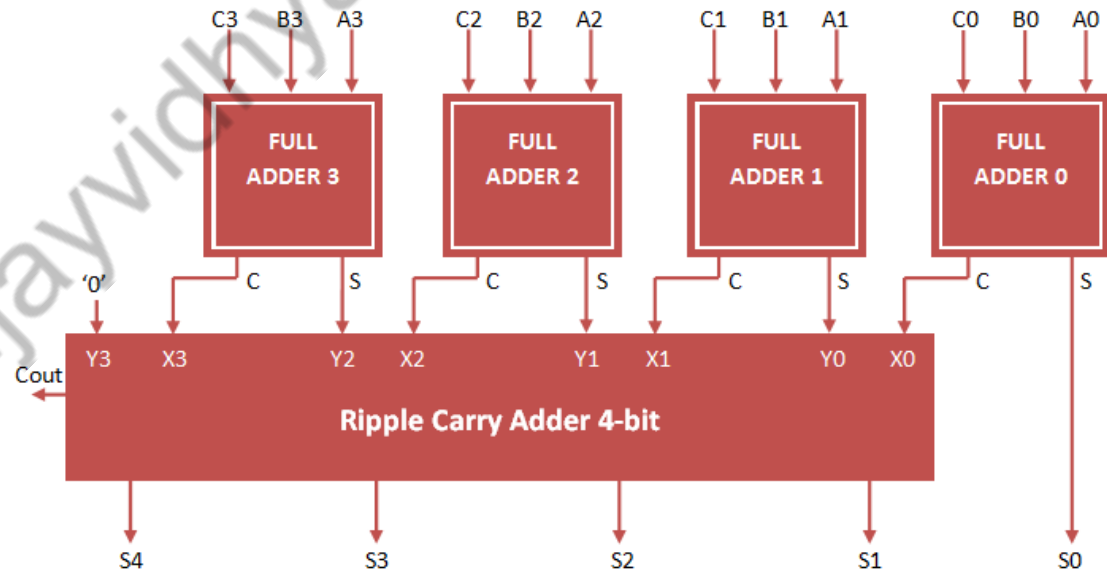

Serial Adder

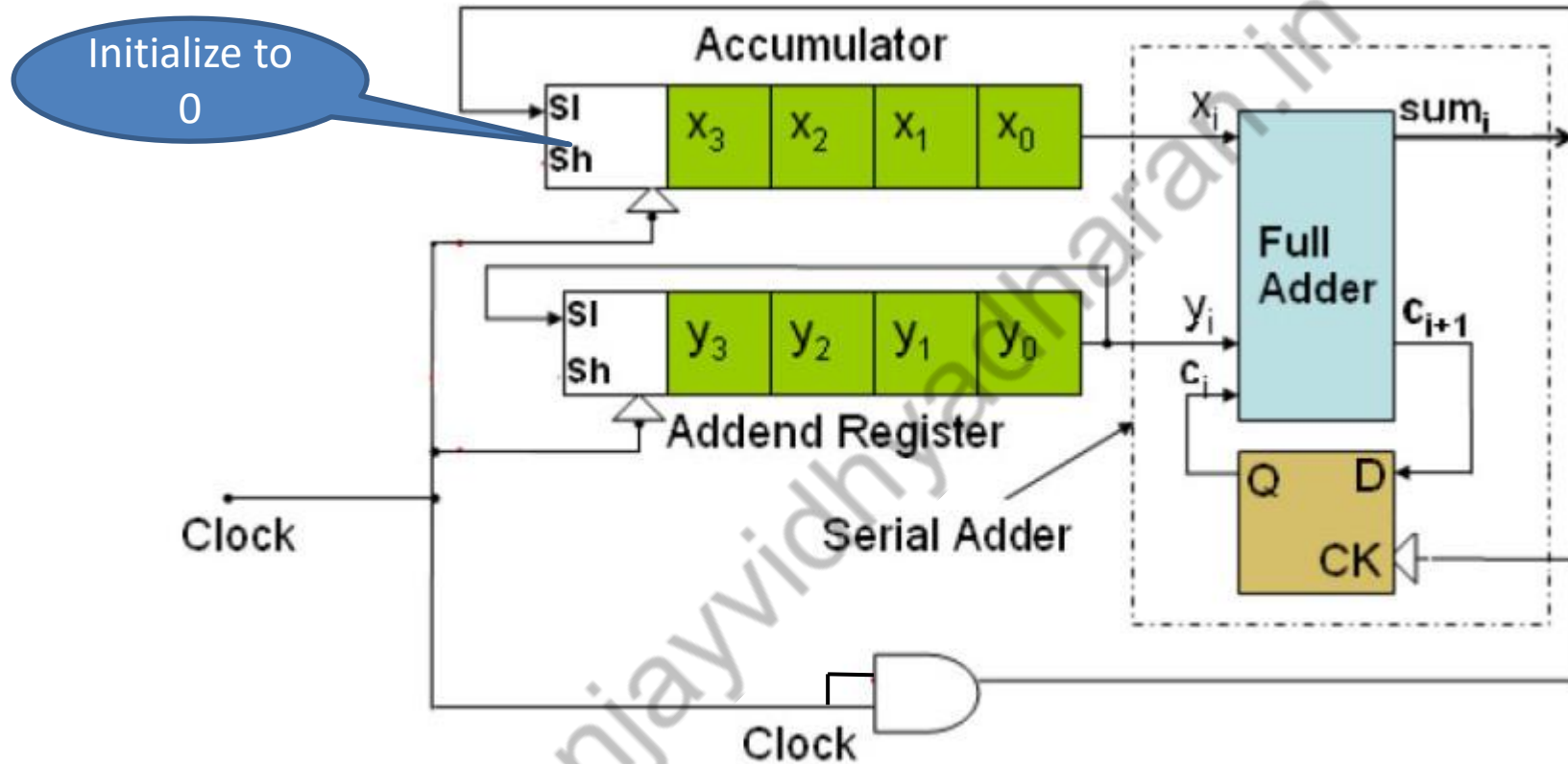

Block Diagram of a 4-bit Serial Adder with Accumulator

4 Bit-Adder Subtractor

Add 4 & -3

```

0100
1101
1 0001
    
```

Add -4 & -5

```

1100
1011
1 0111
    
```

Add -8 & 4


```

1000
0100
1100
    
```

Add 4 & 4

```

0100
0100
1000
    
```

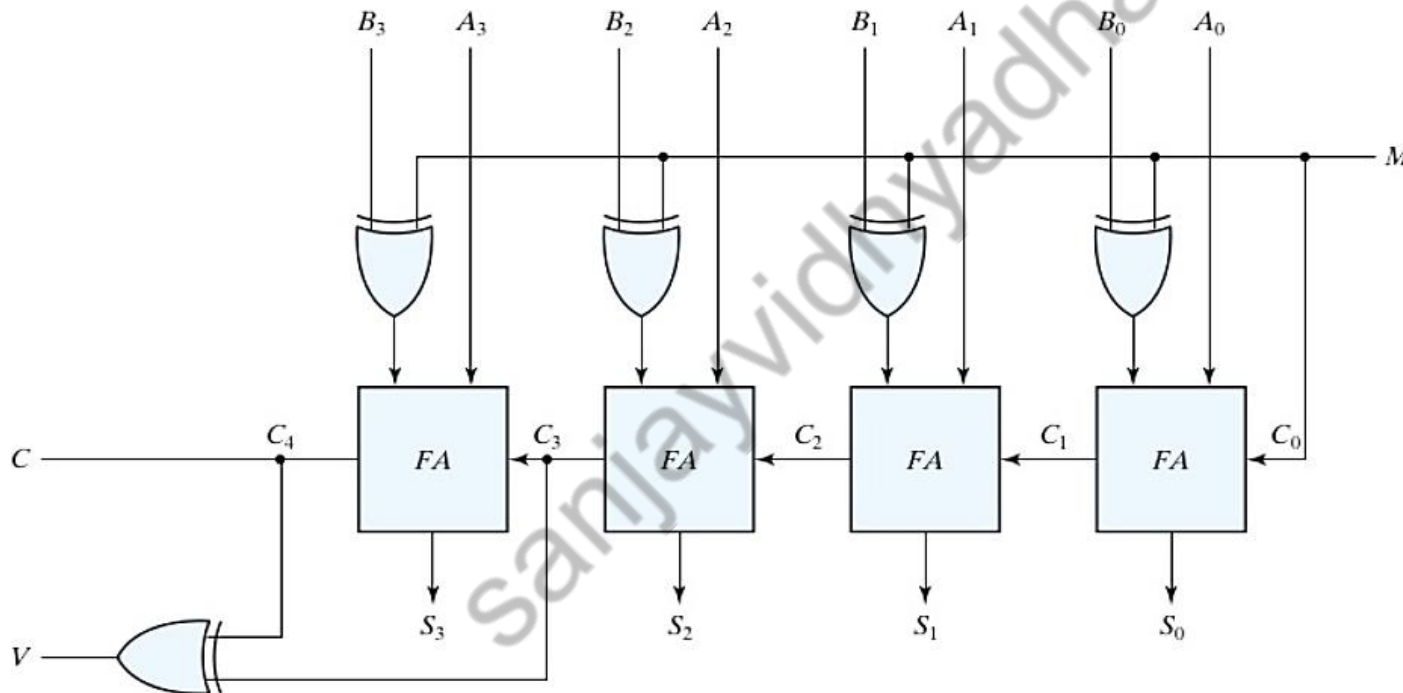


Overflow

Decimal	2's comp.
7	0111
6	0110
5	0101
4	0100
3	0011
2	0010
1	0001
0	0000
-0	-
-1	1111
-2	1110
-3	1101
-4	1100
-5	1011
-6	1010
-7	1001
-8	1000

Binary Coded Decimal

General digital systems

 User enters decimal \rightarrow BCD i/p \rightarrow Binary i/p \rightarrow compute in binary \rightarrow Binary o/p \rightarrow BCD o/p \rightarrow Decimal output shown to user



Binary Coded Decimal

BCD addition

$$4 + 5$$

4 0 1 0 0

5 0 1 0 1

9 1 0 0 1 Expected Result

$$4 + 8$$

4 0 1 0 0

8 1 0 0 0

1 1 0 0 Is this expected Result ?

Expected answer 0001 0010
is BCD of 12

Binary Coded Decimal

BCD addition

4 + 8 4 0 1 0 0

8 1 0 0 0

Greater than 9

1 1 0 0

0 1 1 0

0 0 0 1 0 0 1 0

1 2

Add correction of +6

= To skip 6 invalid
states (10 - 15) BCDs

Binary Coded Decimal

BCD addition

9 + 9 9 1 0 0 1

9 1 0 0 1

Carry out generated 1 0 0 1 0

Expected result ?

0 1 1 0

Add correction of +6


0 0 0 1 1 0 0 0

1 8

After addition if carry out is generated or if sum is greater than 9 there is need for correction

Binary Coded Decimal

BCD addition

 

0 0 0 0
 0 0 0 1
 0 0 1 0
 0 0 1 1
 0 1 0 0
 0 1 0 1
 0 1 1 0
 0 1 1 1
 1 0 0 0
 1 0 0 1

Thank you