



Analog IC Design : 2022-23




Lecture 12

Stability and Oscillators


By Dr. Sanjay Vidhyadharan

sanjayvidhyadharan.in

Stability

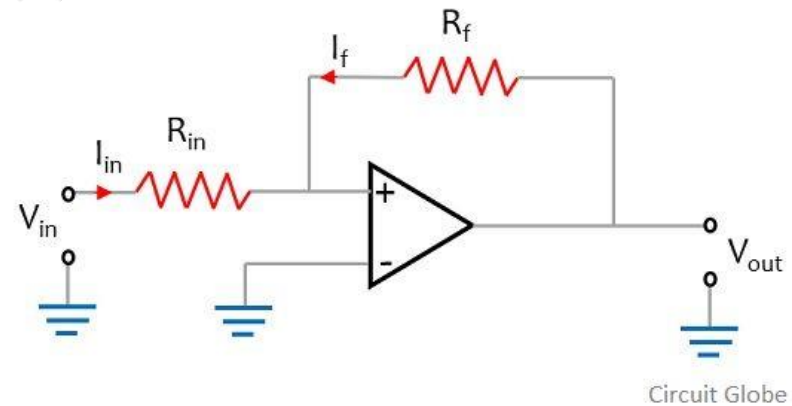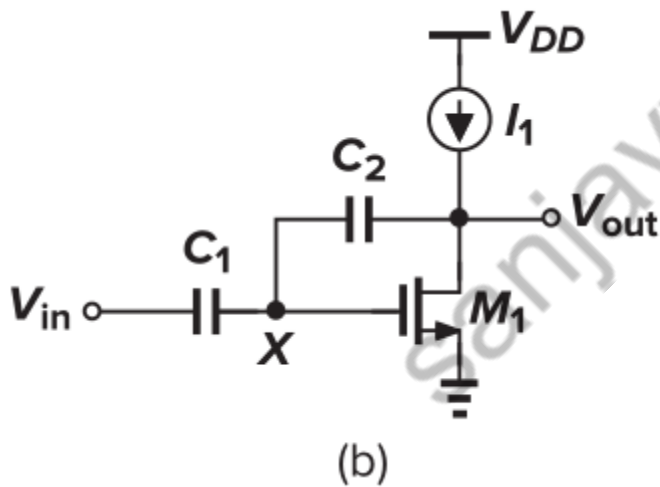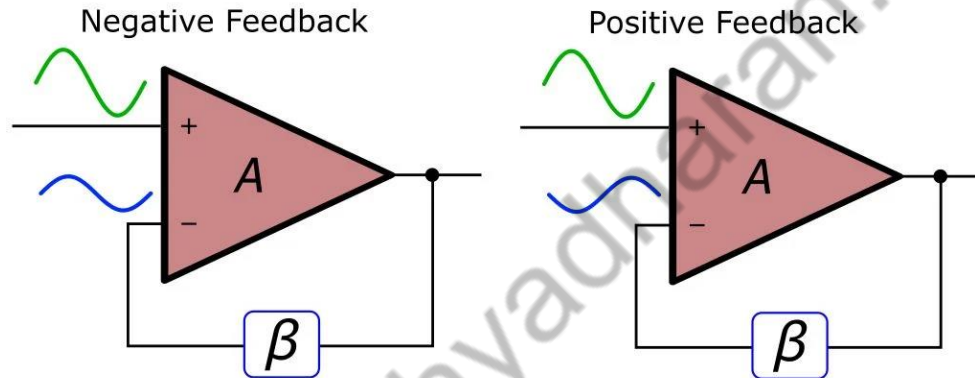


Stability

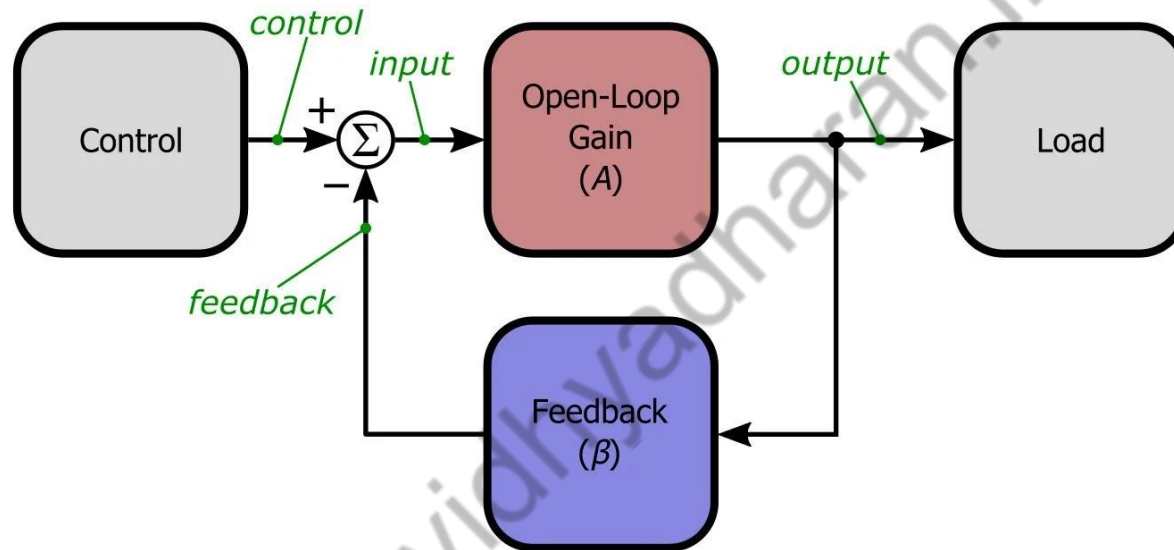

$$\text{Closed loop gain } A_f = \frac{A}{1 + A\beta}$$

Single Pole Response

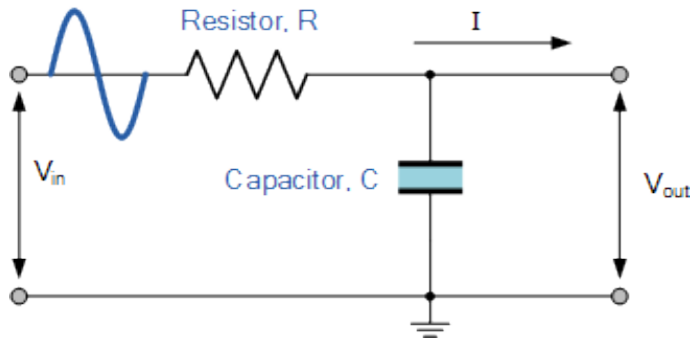

For $\omega \ll \omega_0$ $A_v = 1$ Power Gain = 0 dB, $\phi = 0$

For $\omega = \omega_0$ $A_v = \frac{1}{\sqrt{2}}$ Power Gain = -3 dB, $\phi = -45^\circ$

For $\omega > \omega_0$ Slope 20 dB/decade for $\omega \gg \omega_0$ $\phi = -90^\circ$

$$V_{out} = V_{in} \frac{-jX_c}{R - jX_c} \quad \omega_0 = \frac{1}{RC}$$

$$\text{Gain} = \frac{V_{out}}{V_{in}} = \frac{-jX_c}{R - jX_c} = \frac{1}{1 + jRC\omega} = \frac{1}{1 + j\frac{\omega}{\omega_0}}$$

$$\text{Gain}(j\omega) = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2}} \angle -\tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$

$$\text{Power Gain in dB} = 20 \log(A_v)$$

$$\text{Half Power Gain in dB} = 20 \log \frac{1}{\sqrt{2}} = -3 \text{ dB}$$

$$A_{v1} = \frac{1}{\sqrt{1 + \left(\frac{\omega_1}{\omega_0}\right)^2}}$$

$$A_{v2} = \frac{1}{\sqrt{1 + \left(\frac{10\omega_1}{\omega_0}\right)^2}} \approx A_{v1} / 10$$


$$\text{Gain in dB} = 20 \log\left(\frac{1}{10}\right) = -20 \text{ dB}$$

Single Pole Response



For $\omega \ll \omega_0$ $A_v = 1$ Power Gain = 0 dB, $\phi = 0$

For $\omega = \omega_0$ $A_v = \frac{1}{\sqrt{2}}$ Power Gain = -3 dB, $\phi = -45^\circ$


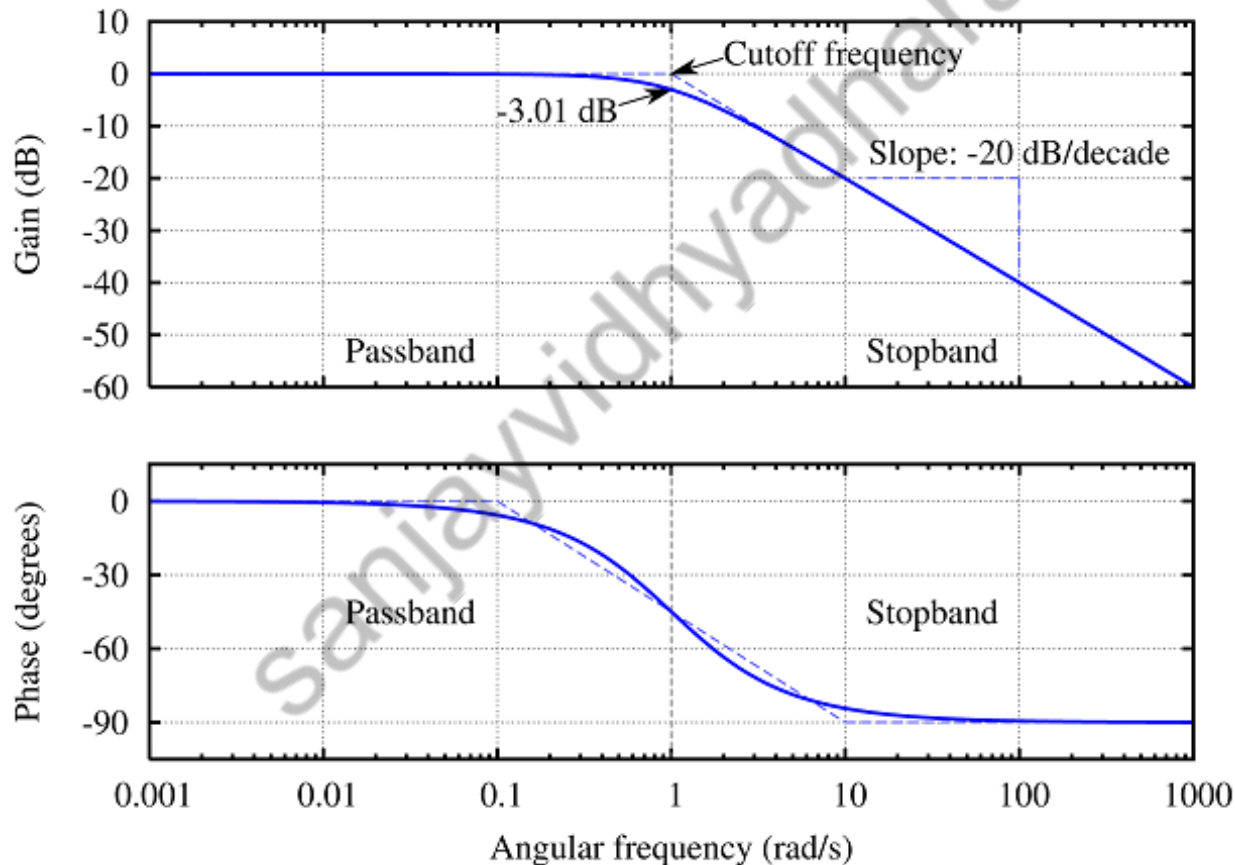
For $\omega > \omega_0$ Slope 20 dB/decade for $\omega \gg \omega_0$ $\phi = -90^\circ$



Two Pole Response

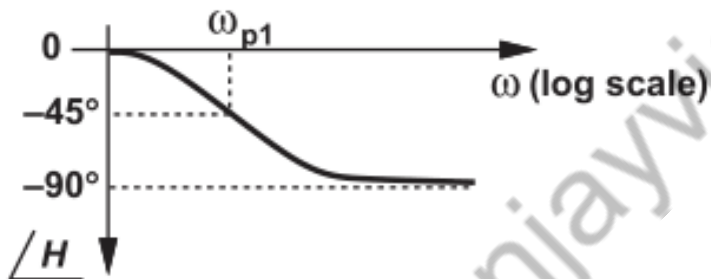
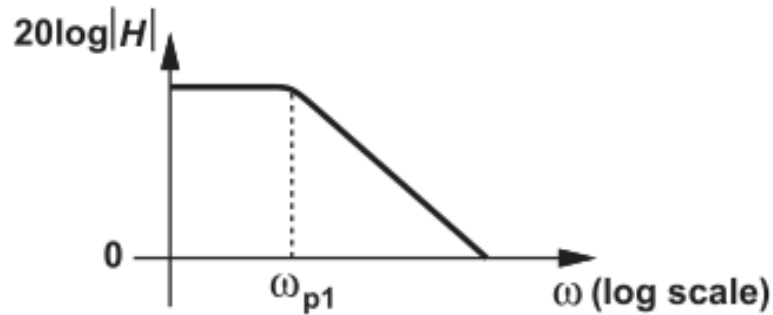


(a)

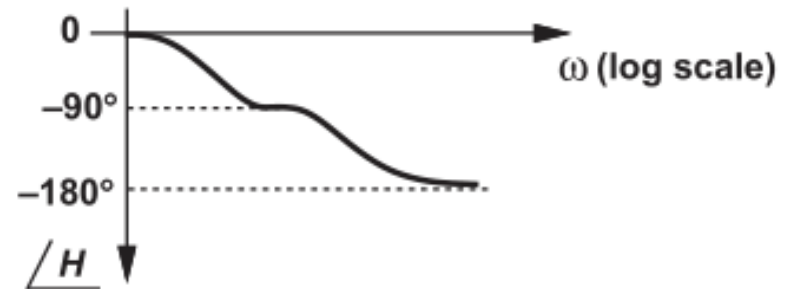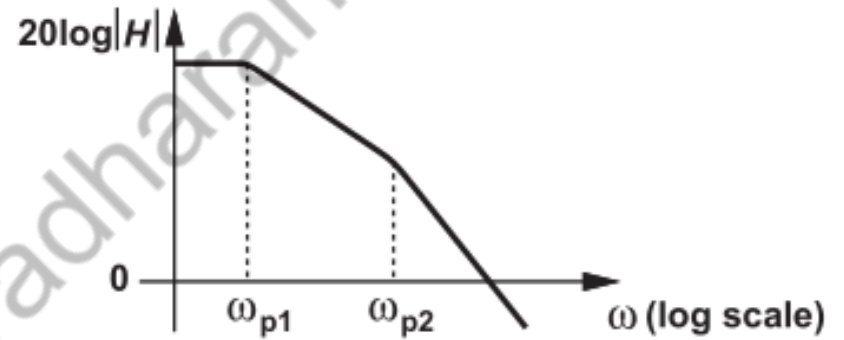


(b)

Three Pole Response

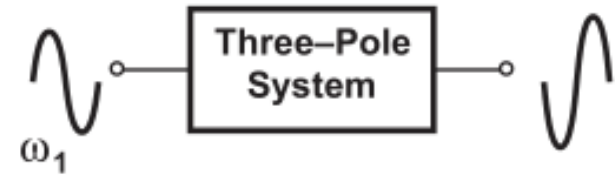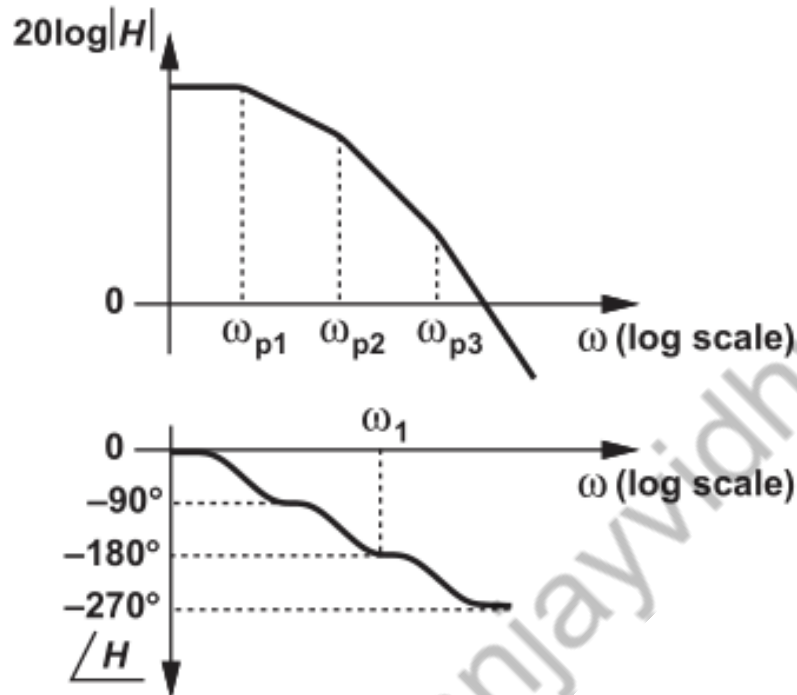


Stability

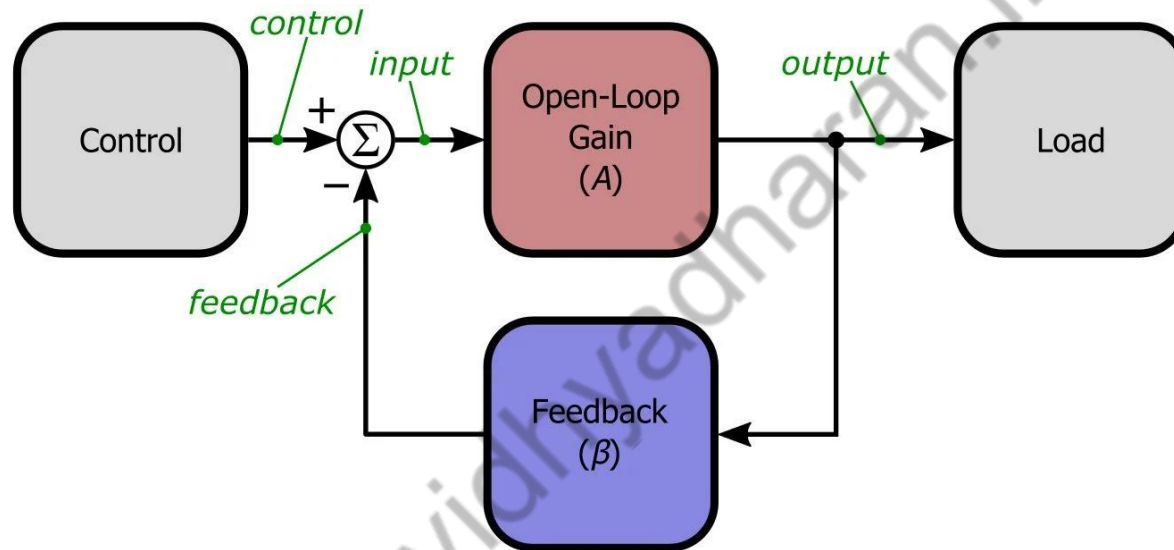


$$\text{Closed loop gain } A_f = \frac{A}{1 + A\beta}$$


Stability

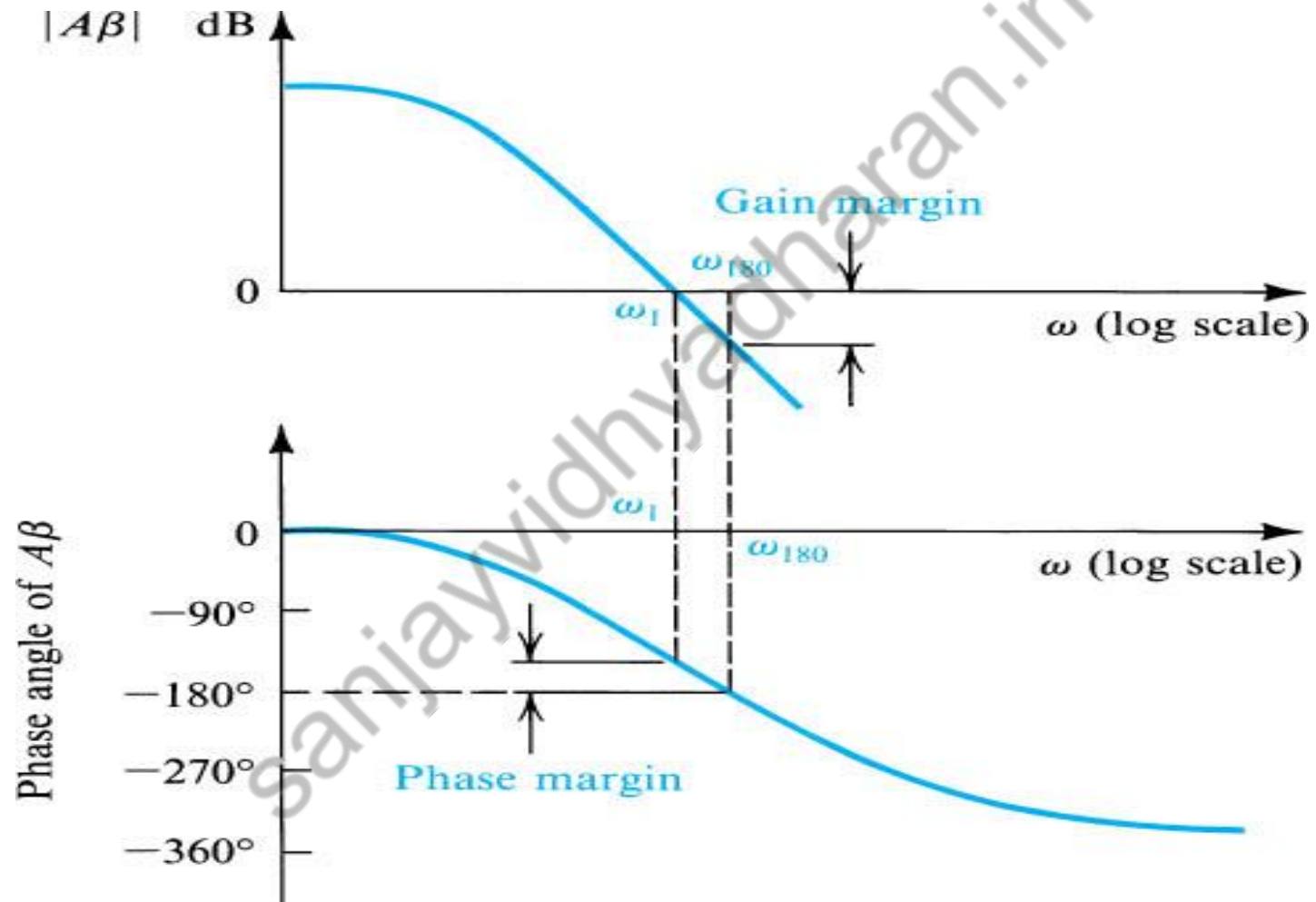

Stability

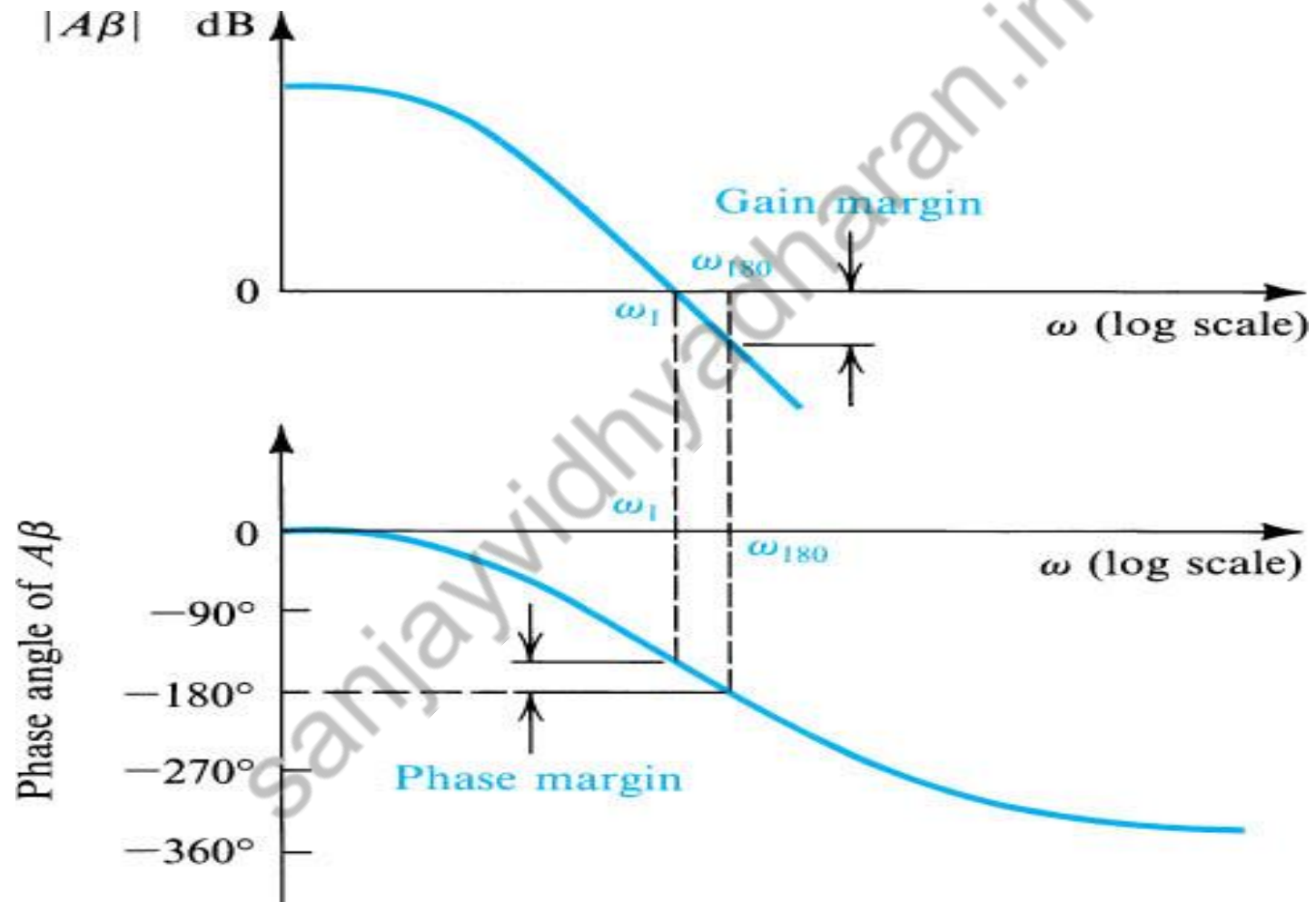

Stability

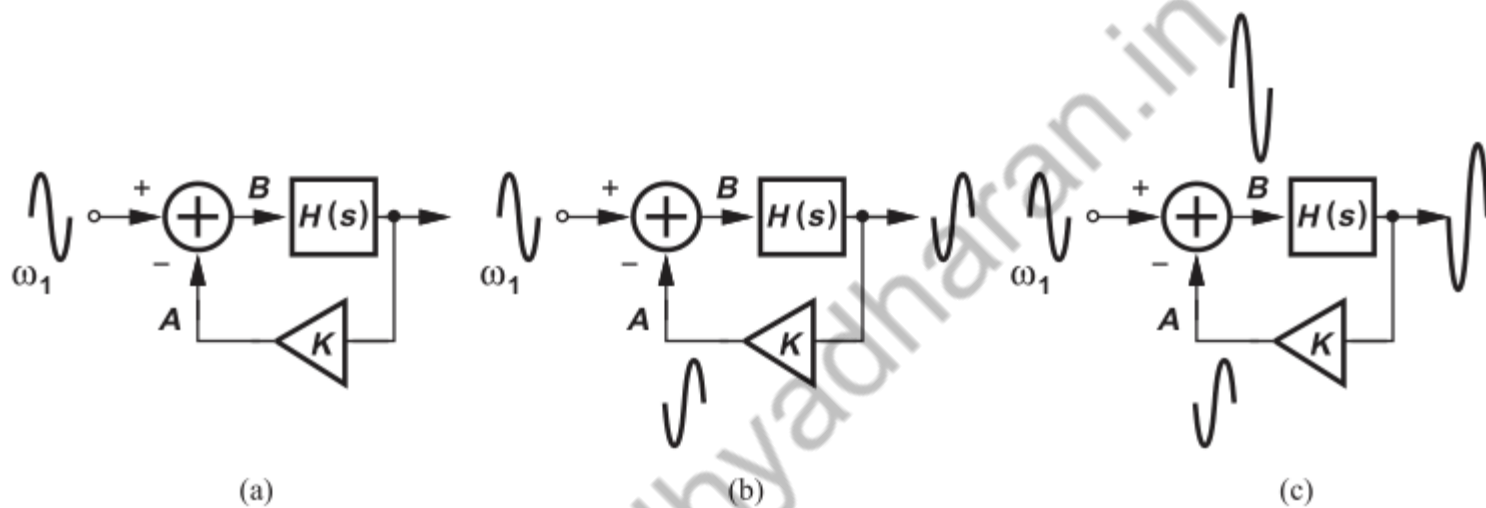


(a) a component at ω_1 is sensed at input, (b) the component returns to subtractor with a 180° phase shift, (c) the subtractor enhances the signal at node B.


A negative feedback system may become unstable if the forward amplifier introduces a phase shift of -180° at a finite frequency, ω_1 , and the loop transmission $|KH|$ is equal to unity at that frequency

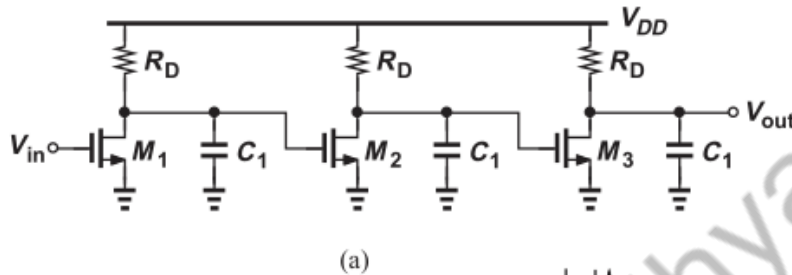Example-1

We wish to apply negative feedback with $K = 1$ around the three-stage amplifier shown in Fig. 12.67(a). Neglecting other capacitances and assuming identical stages, plot the frequency response of the circuit and determine the condition for stability. Assume $\lambda = 0$.



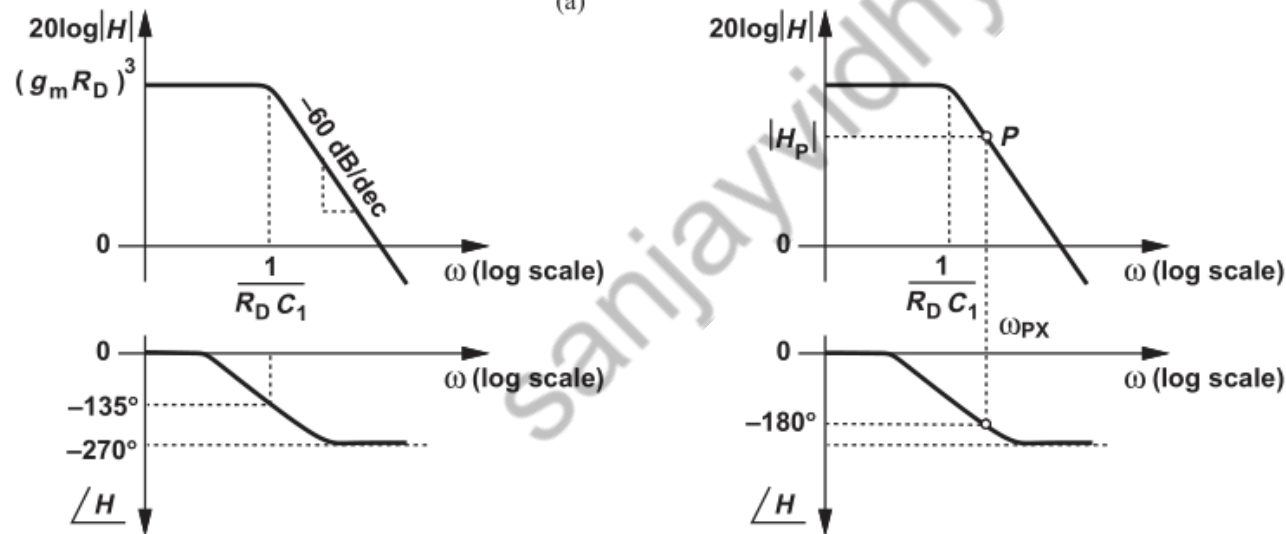The phase begins to change at one-tenth of this frequency, it reaches -135° at ω_p , and approaches -270° at $10\omega_p$.



Example-1

We wish to apply negative feedback with $K = 1$ around the three-stage amplifier shown in Fig. Neglecting other capacitances and assuming identical stages, plot the frequency response of the circuit and determine the condition for stability. Assume $\lambda = 0$.

$$H(s) = \frac{(g_m R_D)^3}{\left(1 + \frac{s}{\omega_p}\right)^3},$$

$$\angle H(j\omega) = -3 \tan^{-1} \frac{\omega}{\omega_p},$$

The phase crossover occurs if $\tan^{-1}(\omega/\omega_p) = 60^\circ$ and hence


$$\omega_{PX} = \sqrt{3}\omega_p.$$

$$\frac{(g_m R_D)^3}{\left[\sqrt{1 + \left(\frac{\omega_{PX}}{\omega_p}\right)^2}\right]^3} < 1.$$

$$g_m R_D < 2.$$

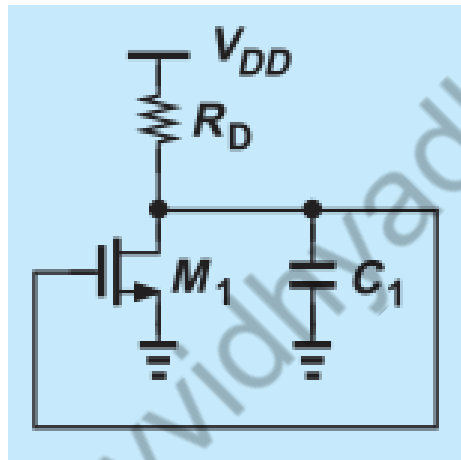
Example-2

A common-source stage is placed in a unity-gain feedback loop as shown in Fig. Explain why this circuit does not oscillate.




Since the circuit contains only one pole, the phase shift cannot reach 180° at any frequency. The circuit is thus stable.


Frequency Compensation

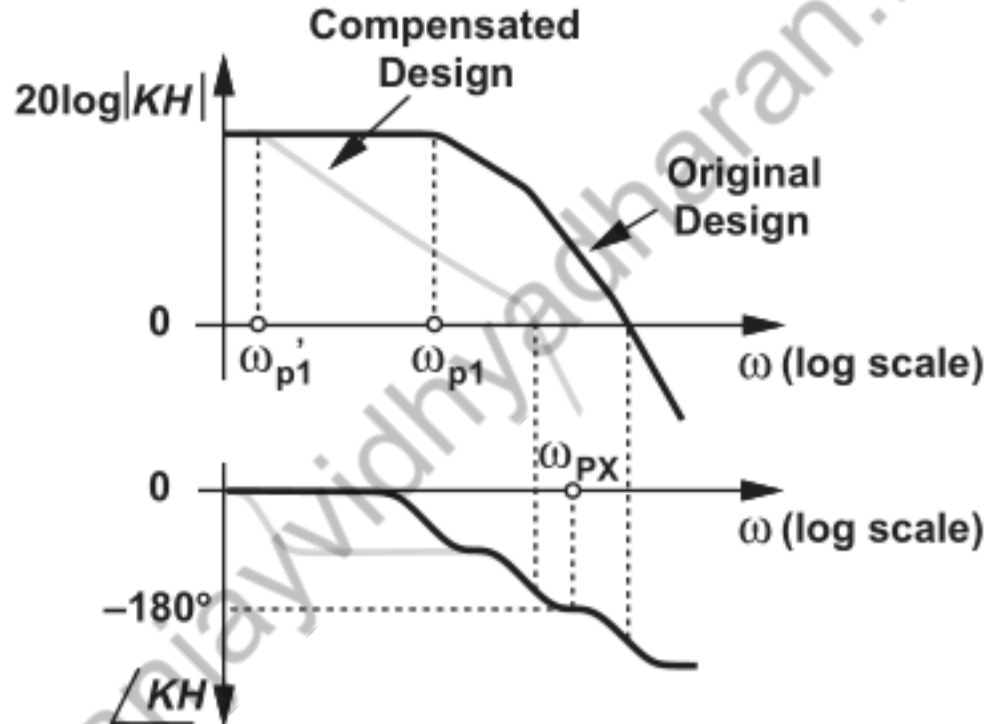


Frequency Compensation

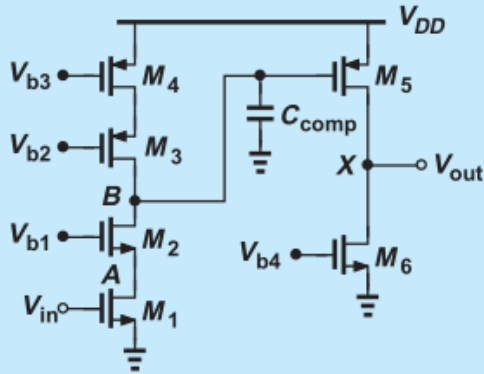

(a)

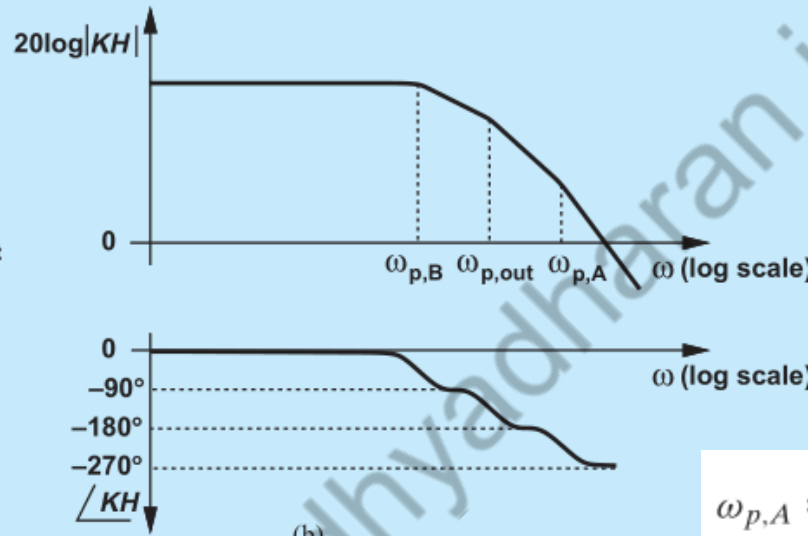

(b)

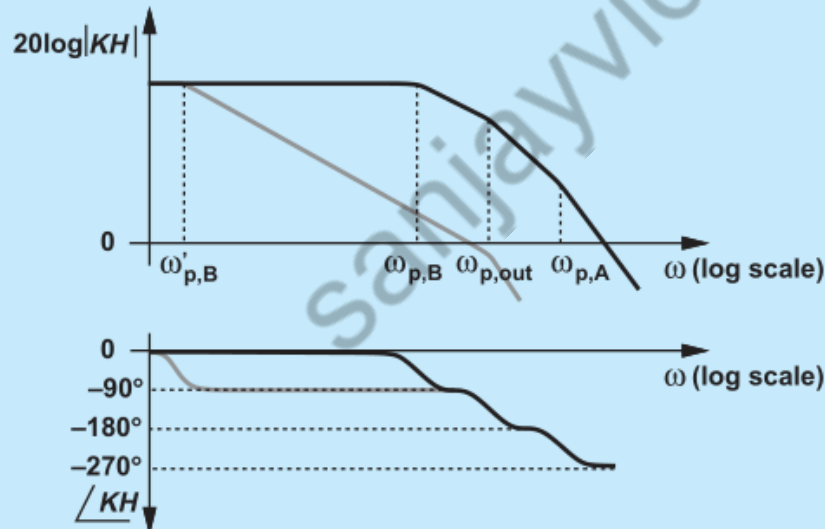


$$\omega_{p,A} \approx \frac{g_{m2}}{C_A}$$

$$\omega_{p,B} \approx \frac{1}{[(g_{m2}r_{O2}r_{O1}) || (g_{m3}r_{O3}r_{O4})]C_B}$$


$$\omega_{p,out} = \frac{1}{(r_{O5} || r_{O6})C_{out}}$$

Miller Compensation

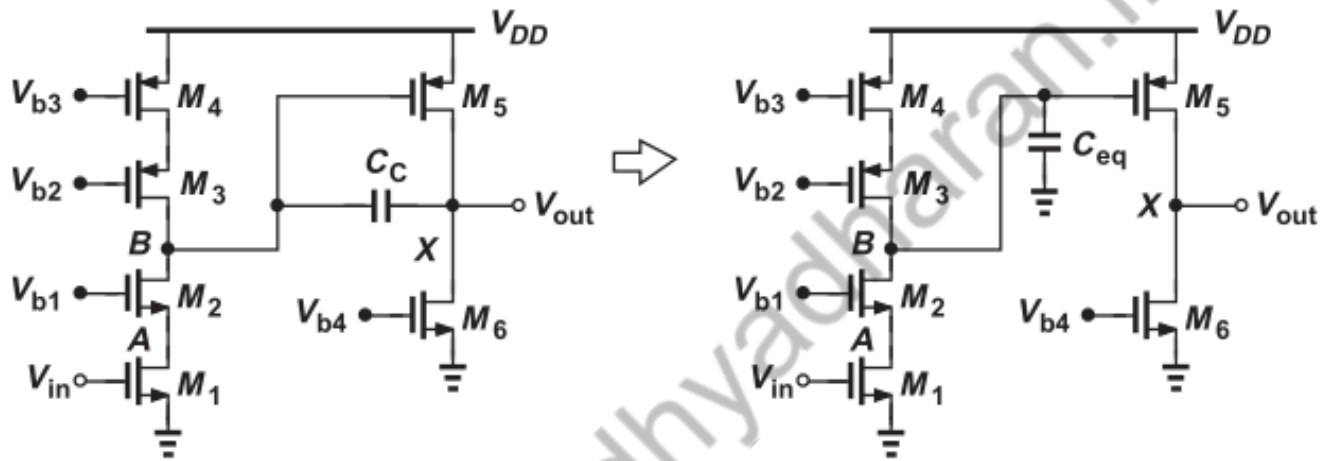

$$C_{eq} = (1 - A_v)C_c$$
$$= [1 + g_{m5}(r_{O5} || r_{O6})]C_c.$$

Oscillators

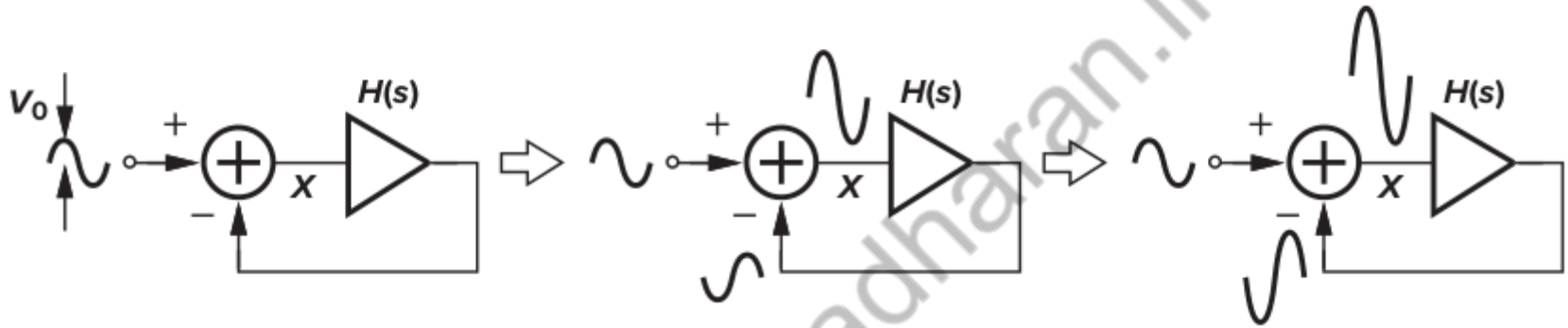


“Barkhausen criteria,”

$$|H(j\omega_0)| \geq 1$$

$$\angle H(j\omega_0) = 180^\circ$$

Oscillators

Three-stage ring oscillator.

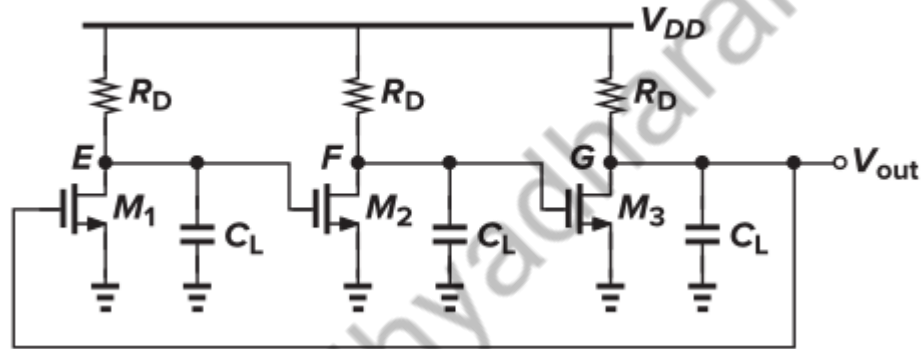

$$\tan^{-1} \frac{\omega_{osc}}{\omega_0} = 60^\circ$$



$$\omega_{osc} = \sqrt{3}\omega_0$$

$$\frac{A_0^3}{\left[\sqrt{1 + \left(\frac{\omega_{osc}}{\omega_0} \right)^2} \right]^3} = 1$$

$$A_0 = 2$$

Oscillators


LC oscillator.

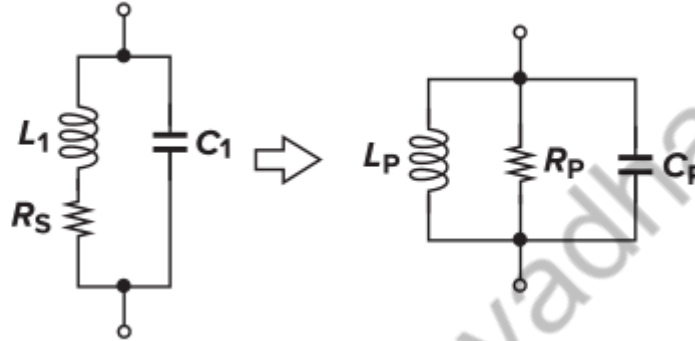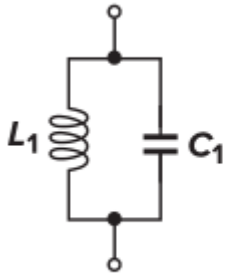


$$L_P \approx L_1$$

$$R_P \approx \frac{L_1^2 \omega^2}{R_S}$$
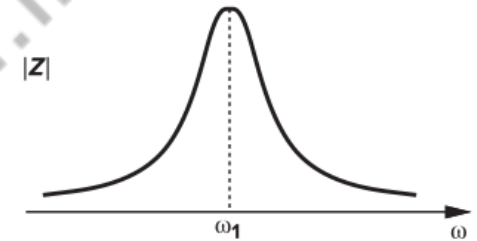
$$R_P \approx \frac{L_1^2 \omega^2}{R_S} \approx Q^2 R_S$$



(a)


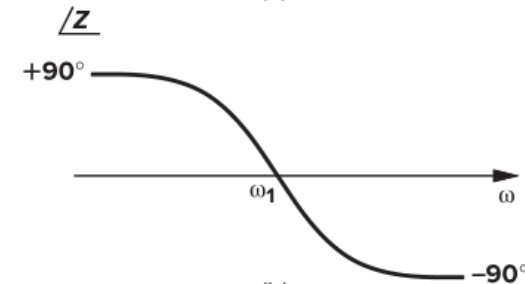


(b)

Impedance:
$$\frac{1}{Z} \equiv \frac{I_{max}}{\mathcal{E}_{max}} = \sqrt{\frac{1}{R^2} + \left(\frac{1}{\omega L} - \omega C\right)^2}$$



Oscillators

LC oscillator.

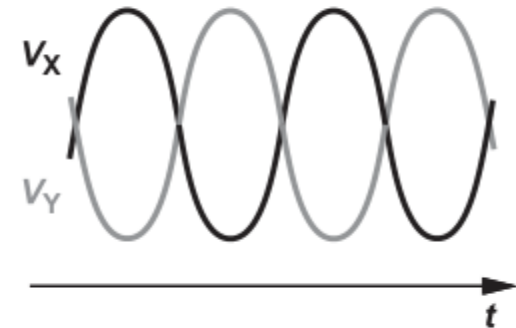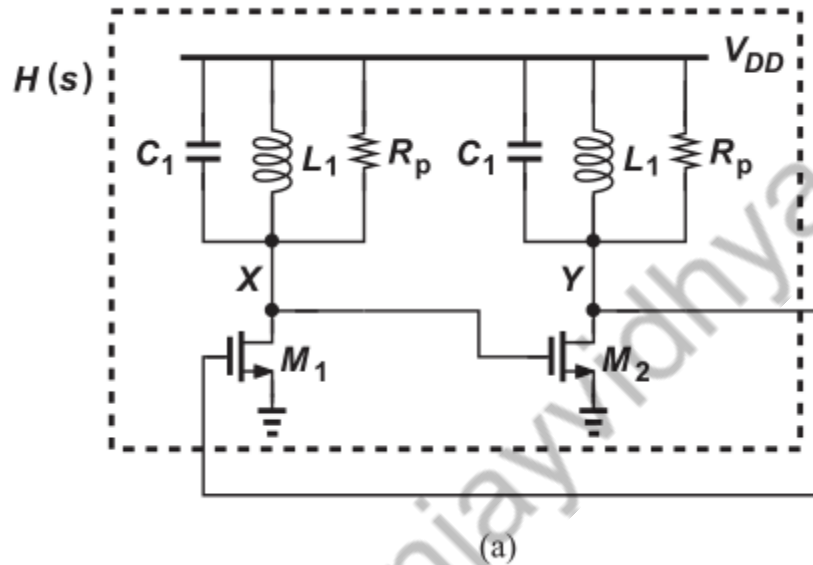



Oscillators

LC oscillator.

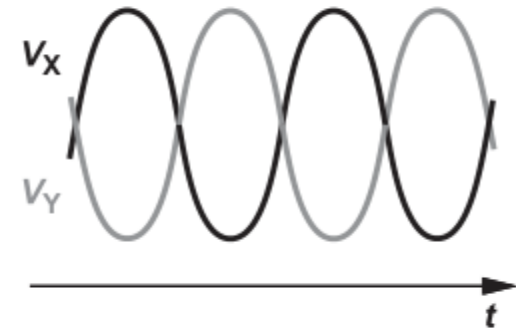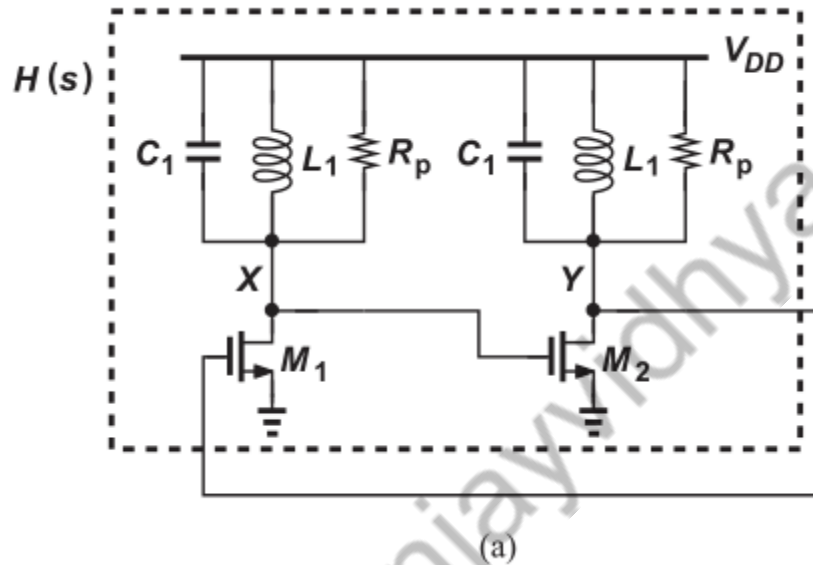

Oscillators

PHASE SHIFT OSCILLATOR

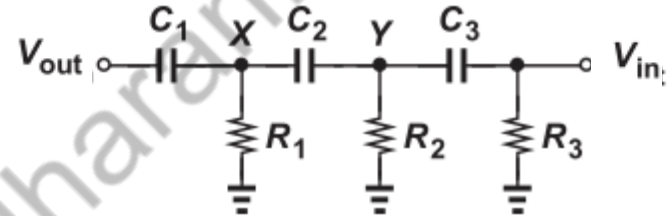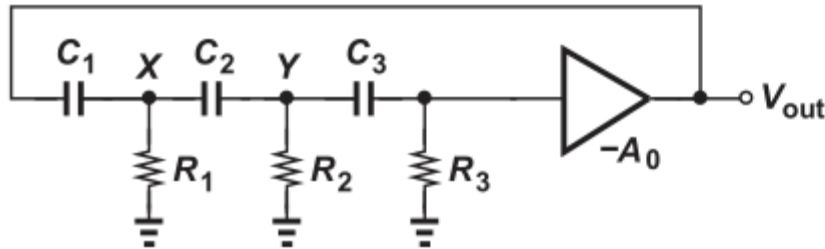

$$V_X = \frac{R}{R + \frac{1}{Cs}} = \frac{RCs}{1 + RCs}$$

$$\frac{V_{out}}{V_{in}} = \frac{(RCs)^3}{(RCs + 1)^3}$$

That is, the gain of the amplifier must be at least:
 $A = 2$.


For oscillation to occur at ω_1 , this phase must reach 180° :

$$\tan^{-1}(RC\omega_1) = 30^\circ.$$


It follows that

$$\omega_1 = \frac{1}{\sqrt{3}RC}.$$

Oscillators

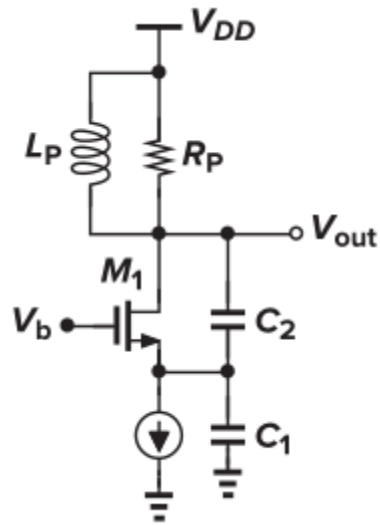

Colpitts oscillator

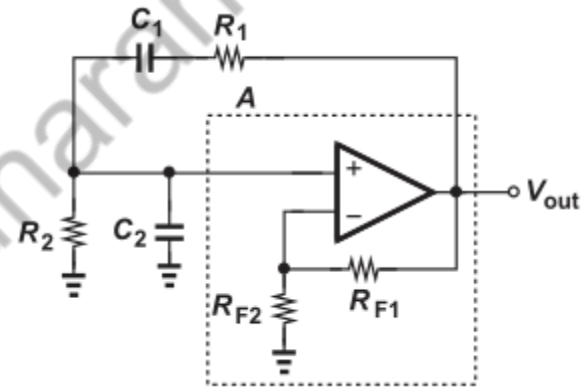

Wien-bridge oscillator.

$$\omega_1 = \frac{1}{RC}.$$

$$A = 3.$$

That is, we choose $R_{F1} \geq 2R_{F2}$.

Thankyou

sanjayvidhyadharan.in