

Testability of VLSI

Lecture 2: Fault Modelling

By Dr. Sanjay Vidhyadharan

Defects, Errors, and Faults

Defect. A defect in an electronic system is the unintended difference between the implemented hardware and its intended design.

Example : unwanted wire (short to ground)

1. Process Defects – missing contact windows, parasitic transistors, oxide breakdown, etc.
2. Material Defects – bulk defects (cracks, crystal imperfections), surface impurities, etc.
3. Package Defects – contact degradation, seal leaks, etc
4. Age Defects – dielectric breakdown, electromigration, etc.

Fault. A representation of a “defect” at the abstracted function level is called a fault

Example: Stuck to Zero Fault





Error. A wrong output signal produced by a defective system is called an error. An error is an “effect” whose cause is some “defect.”

Example: output = 0, when a=b=1 for a AND gate

Failure : Deviation from expected behavior **Example: computer crash**

Defect → Fault → Error → Failure


Fabrication Faults

    

Fabrication Faults


- **Random defects**

 - ◆ Caused by random factors such as particles, scratches, ...
- ◆ No correlation across wafers, dies



- **Systematic defects**

 - ◆ Caused by deterministic factors such as mask, lithography, ...
- ◆ Strong correlation across wafers, dies



Fault Models

Why Fault Modelling?

1. Defects are hard to handle

How many possible defects in a circuit ? **Way too many**

Number of faults can be easily calculated in a circuit

2. Fault models makes test **automation** possible

Automatic test pattern generation (ATPG) generate test patterns

Fault simulation

Evaluate test quality

Automatic diagnosis




Locate defects

Fault Models

- 1. Assertion Fault:** An assertion expresses a property of a high-level function in the form: “antecedent consequent,” where antecedent and consequent can be simple predicates like “line L takes symbolic value v” or conjunctions of simple predicates.
- 2. Behavioural Faults (*Functional or High level*):** When the behavior of an electronic system is described in computer-readable form, it is generally written in a programming language (such as C) or some other hardware description language that resembles a programming language.
- 3. Structural Faults:** The structure of a circuit may refer to its topology or to physical geometry. Examples of structural faults are single stuck-at faults and bridging faults.
Focus is on manufacturing defects not functional aspect of DUT.

➤ **Please refer to other types of faults in the textbook**

Functional Versus Structural Testing

   

Functional Test Vectors $2^{129} = 6.8 * 10^{38}$

Required time with Clock of 1 GHz \approx 22 years


Max Structural Test vectors required $64 * (10 + 17)$

Actual Structural Test vectors required could be much less as multiple sa faults gets detected with single vector

Common Structural Fault Models


- Single stuck-at faults
 - Transistor open and short faults
 - Bridging Faults
 - Delay faults (transition, path)
 - Analog faults
- **Please refer to other types of faults in the textbook**

Single Stuck-at faults

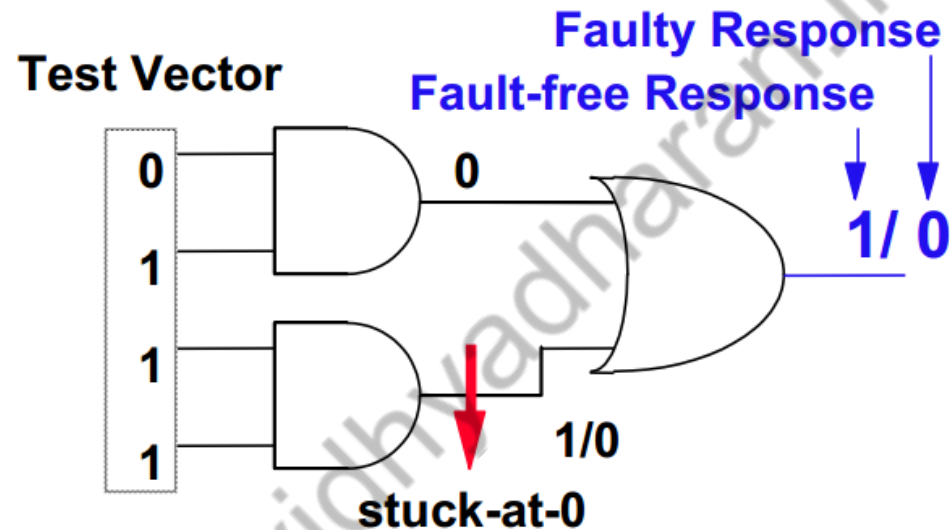

- Assumptions:
- Only one line is faulty.
 - Faulty line permanently set to 0 or 1.
 - Fault can be at an input or output of a gate.

Single Stuck-at faults

 

How many Fault Sites ? 3

How many Fault ? **Total six faults: a/0, a/1, b/0, b/1, c/0, c/1**


Minimum test length for 100% SSF fault coverage ? 3

Input <i>a b</i>	Fault-free Output	Faulty Output Value with SSF					
		<i>a/0</i>	<i>a/1</i>	<i>b/0</i>	<i>b/1</i>	<i>c/0</i>	<i>c/1</i>
0 0	0	0	0	0	0	0	<u>1</u>
0 1	0	0	<u>1</u>	0	0	0	<u>1</u>
1 1	1	<u>0</u>	1	<u>0</u>	1	<u>0</u>	1
1 0	0	0	0	0	<u>1</u>	0	<u>1</u>

Single Stuck-at faults

Properties of single stuck-at fault

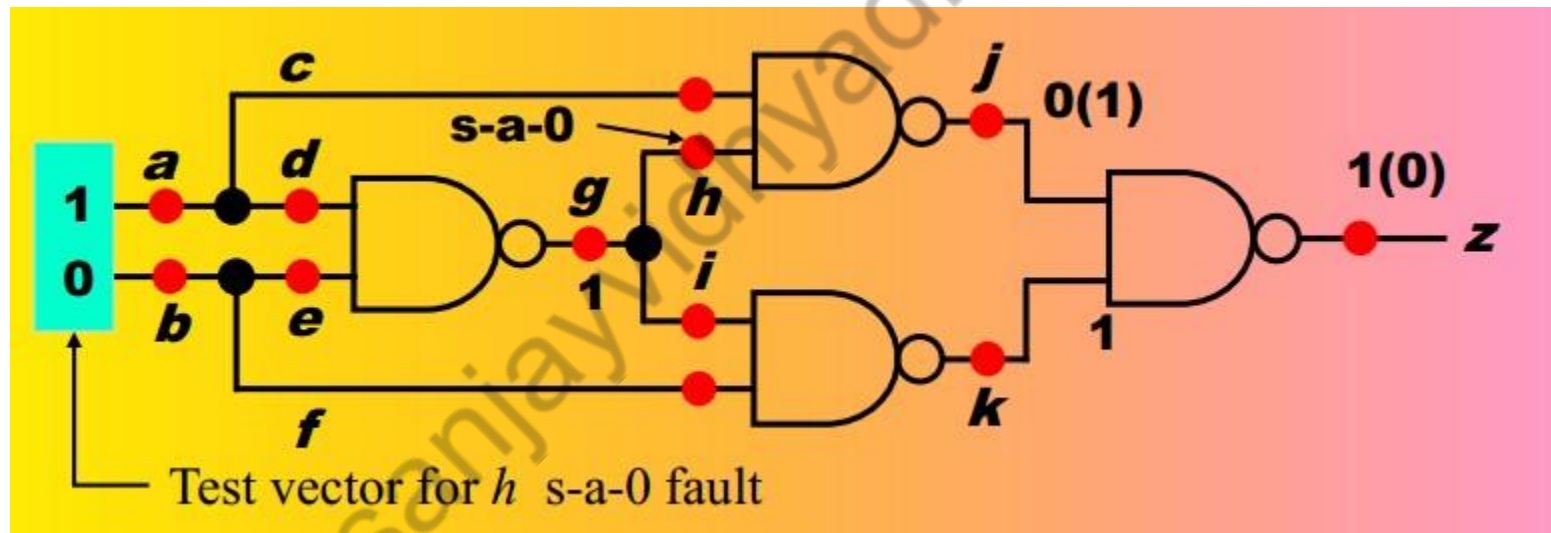- Only one line is faulty
- The faulty line is permanently set to 0 or 1
- The fault can be at an input or output of a gate




XOR circuit has 12 fault sites (●) and 24 single stuck-at faults

Single Stuck-at faults

SSF on fanout wires *not equivalent to* SSF on fanout branches

Faults on stems and faults on branches are **counted separately**

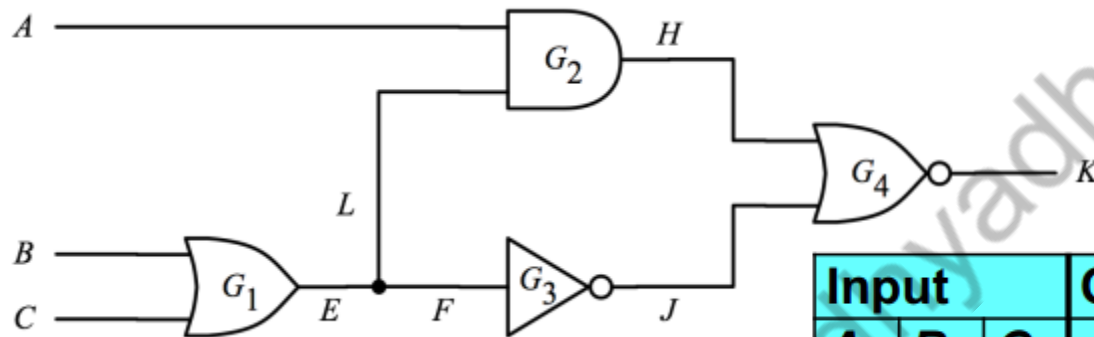Example: *E* is fanout stem; *L, F* are fanout branches



Input			Output						
A	B	C	good	E/0	F/0	L/0	E/1	F/1	L/1
0	0	0	0	0	0	0	1	1	0
0	0	1	1	0	0	1	1	1	1
0	1	0	1	0	0	1	1	1	1
0	1	1	1	0	0	1	1	1	1
1	0	0	0	0	0	0	0	1	0
1	0	1	0	0	0	1	0	0	0
1	1	0	0	0	0	1	0	0	0
1	1	1	0	0	0	1	0	0	0

$$K = \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC$$

$$K = \bar{A}(\bar{B}C + B\bar{C} + BC)$$

$$K = \bar{A}(B + C)$$

$$K = \overline{A + \overline{(B + C)}}$$

Multiple Stuck-at faults

- **Several stuck-at faults occur at the same time**
 - Important in high density circuits

If there are N possible fault locations in a circuit

Total possibilities is 3^N as a line be be sa0 , sa1 or good

One possibility of circuit being good


$2N$ possibilities of single fault

Possibilities of multiple fault $3^N - 1 - 2N$

MSF Not Considered in Practice

Multiple Stuck-at faults

 - How effective is SSF test sets for multiple stuck-at faults?
 - ◆ 14-input ALU 74LS181 circuit
 - ◆ 400 single stuck-at faults
 - ◆ 79,600 double stuck-at faults
 - ◆ 16 different test sets




Test Set	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16
Length	12	12	12	12	12	12	12	14	14	14	14	17	35	124	135	352
Undetected Double-stuck faults	9	8	1	9	28	13	19	4	14	11	3	30	0	0	0	0

- Observation #1: Some shorter tests are **better than** longer tests
 - ◆ Smart test generation/selection is important
- Observation #2: **Most** double SA faults are detected by SSF test sets

Hughes, J.L.A., and E.J. McCluskey, “An Analysis of the Multiple Fault Detection Capabilities of Single Stuck-at Fault Test Sets,” Proc. of Int’l Test Conf, Philadelphia, PA, Oct. 1984, pp. 52–58.


Multiple Stuck-at faults

 

What should be the test vector ?

011


Multiple Stuck-at faults

 


What should be the test vector ? **011 SA1 is Masking SA0**

What should be the test vector ? **010 detects the MSF {c SA0, a SA1}.**


Bridging faults

 

Input to Output Short

 

Input to Input Short

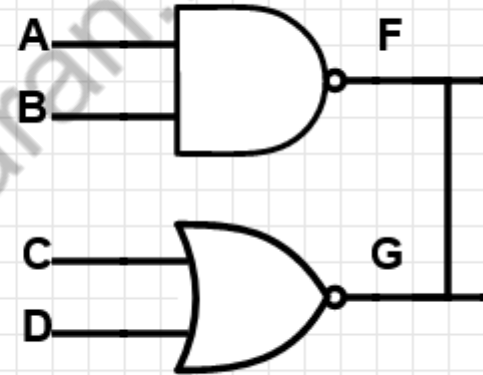


Output to Output Short

- Improper masking or etching
- Loose or excess bare wires
- Defective printed circuit boards
- Shorting of pins of a chip

Test Vectors for Input and Output Stuck-at Faults cover Input-to-Output Shorts

Bridging faults

Input to Output Short

 


1. Can cause oscillations
2. Creates Memory

Test Vectors for Input and Output Stuck-at Faults cover Input-to-Output Shorts

sanjayvidhyadharan.in

Bridging faults

 

Short is Modeled as Low Resistance

Original Fault-free FG	Wired-OR Faulty FG	Wired-AND Faulty FG	F-dominant Faulty FG
0 0	0 0	0 0	0 0
0 1	1 1	0 0	0 0
1 0	1 1	0 0	1 1
1 1	1 1	1 1	1 1


If $F, G = 0, 0$ can be detected as F s-a-0

If $F, G = 1, 1$ can be detected as G s-a-1

High Resistance Bridges do not affect the logic value, and hence are undetectable by a static logic test.

Bridging faults

Different Models Need Different Patterns

 

Inputs A B C	Fault-free Output	Wired OR	Wired AND	A dominant
0 0 0	0	0	0	0
0 0 1	1	1	1	1
0 1 0	1	0	0	0
0 1 1	1	0	0	1
1 0 0	0	0	0	0
1 0 1	0	0	0	0
1 1 0	0	0	0	0
1 1 1	0	0	0	0

Bridging faults


Table 1. Results of 74LS181 simulations.

Test Set	Bry2	Bry6	Goel	Hugh	Krish	McC4	Micz2
Test Length	14	12	35	135	12	124	17
Number of missed AND faults	24	28	4	0	33	0	46
Number of missed OR faults	35	44	5	0	66	1	18
Coverage of AND faults (%)	99.18	99.04	99.86	100.0	98.87	100.0	98.43
Coverage of OR faults (%)	98.79	98.48	99.83	100.0	97.72	99.97	99.38
Total number of each type of fault	2926						

[Millman 88] S.D. Millman, McCluskey, “Detecting bridging faults with stuck-at test sets,” ITC 1988.

Delay faults

Delay Fault

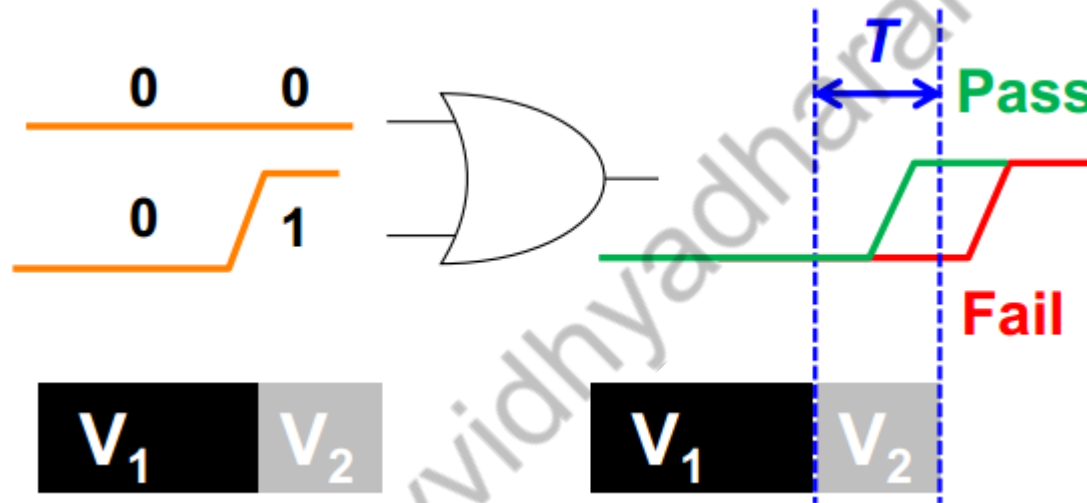


Slow to rise (**STR**), slow to fall Transition (**STF**), faults due to V_t Variation, Doing Variation, Improper contacts etc

No fault detected at static and low frequency operation but glitches can be there at high operating frequencies and cause errors in sequential circuits

Delay Faults requires two test vectors

Delay faults



Delay Fault

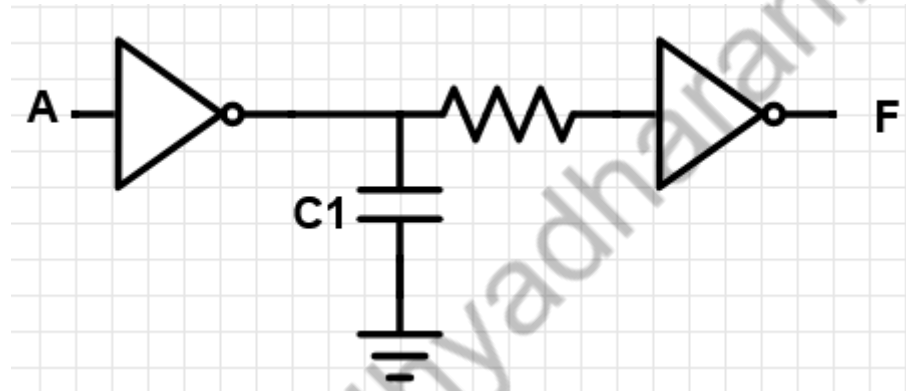

Can be modelled a RC delay but can be because of poor MOSFET being fabricated or nay other fab defects .


Delay Faults requires two test vectors

Delay faults

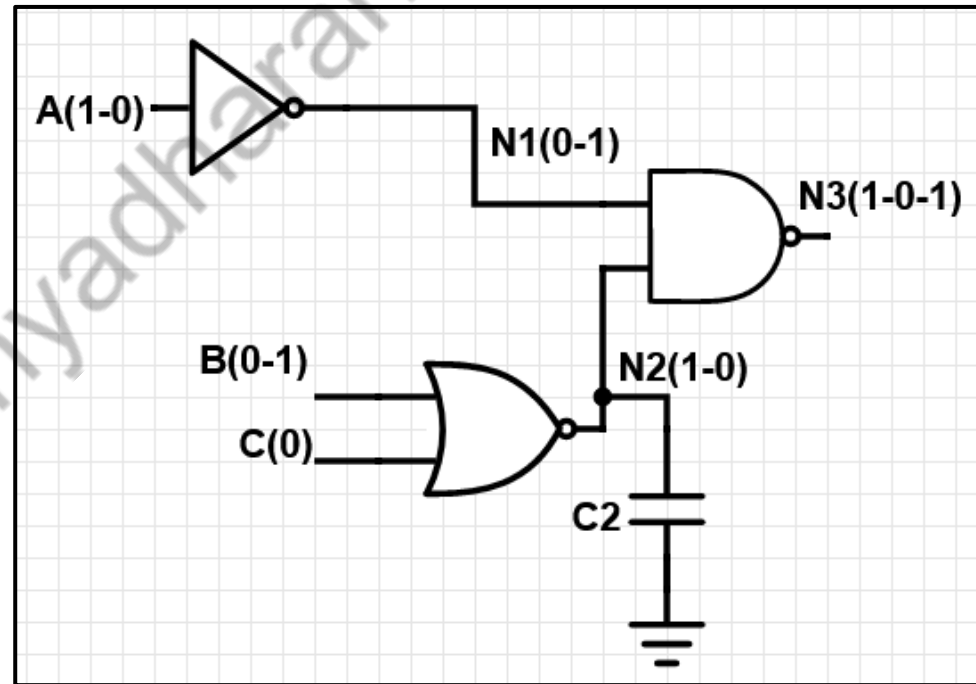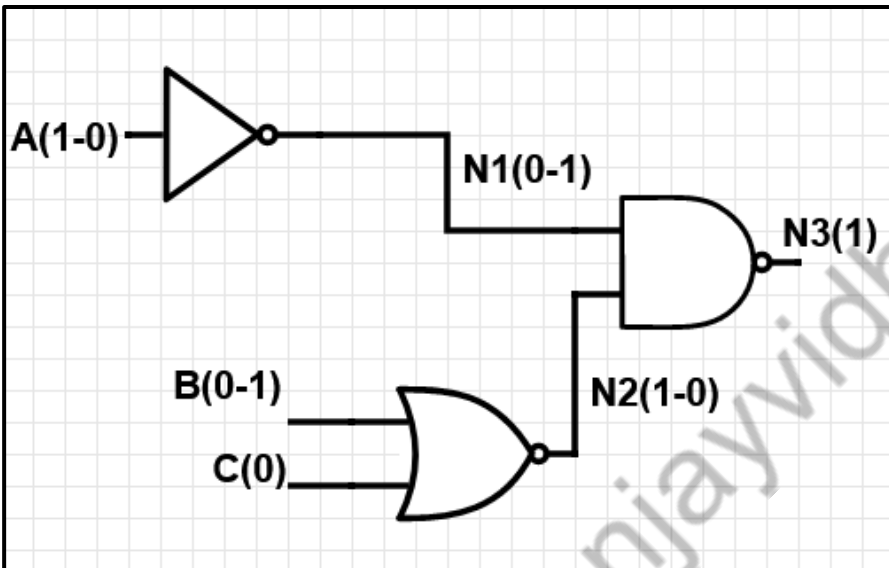

Path Delay Fault

Delay faults

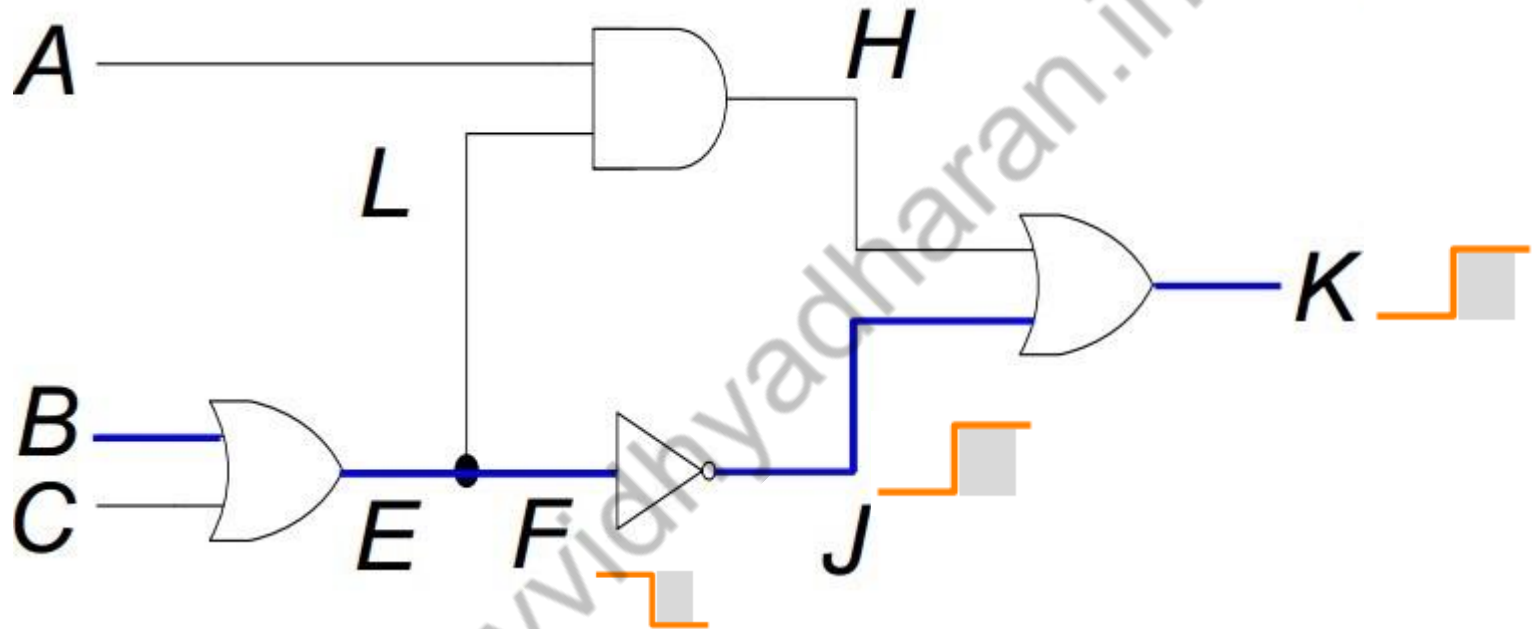


How Many Paths ? 5 paths: {AHK, BELHK, BEFJK, CELHK, CEFJK}

How Many set of test vectors ? 10 sets


Test vector to detect STF fault at F ?

001-000

Delay faults

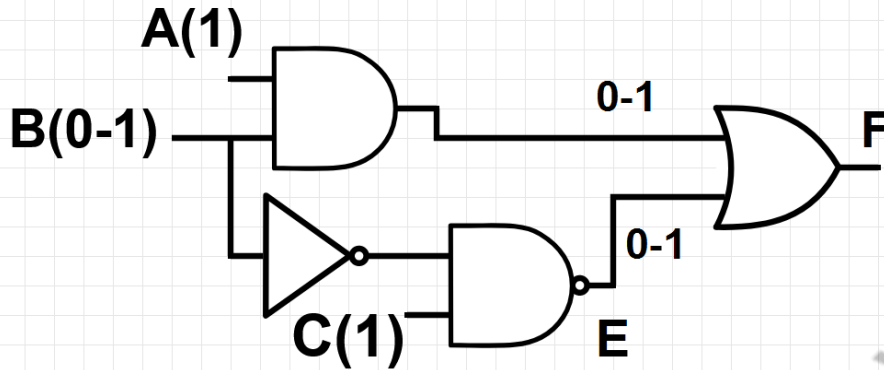

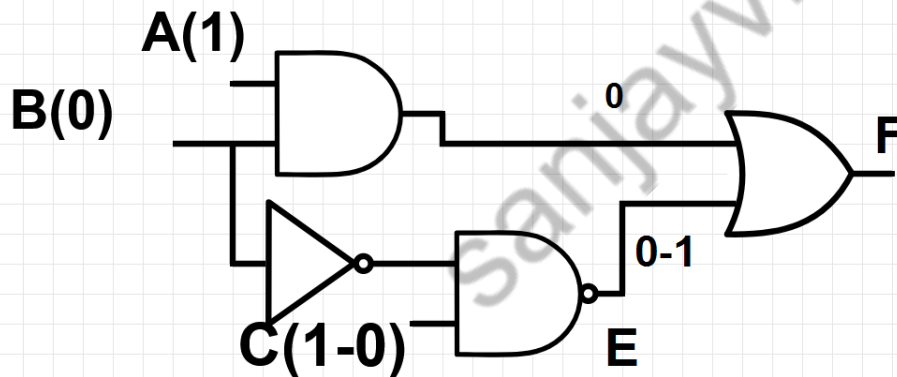
(101,111) : Non-robust test for path STR at E



(101,100) : Robust test for path STR at E

Delay faults

Robust Testing may note possible always

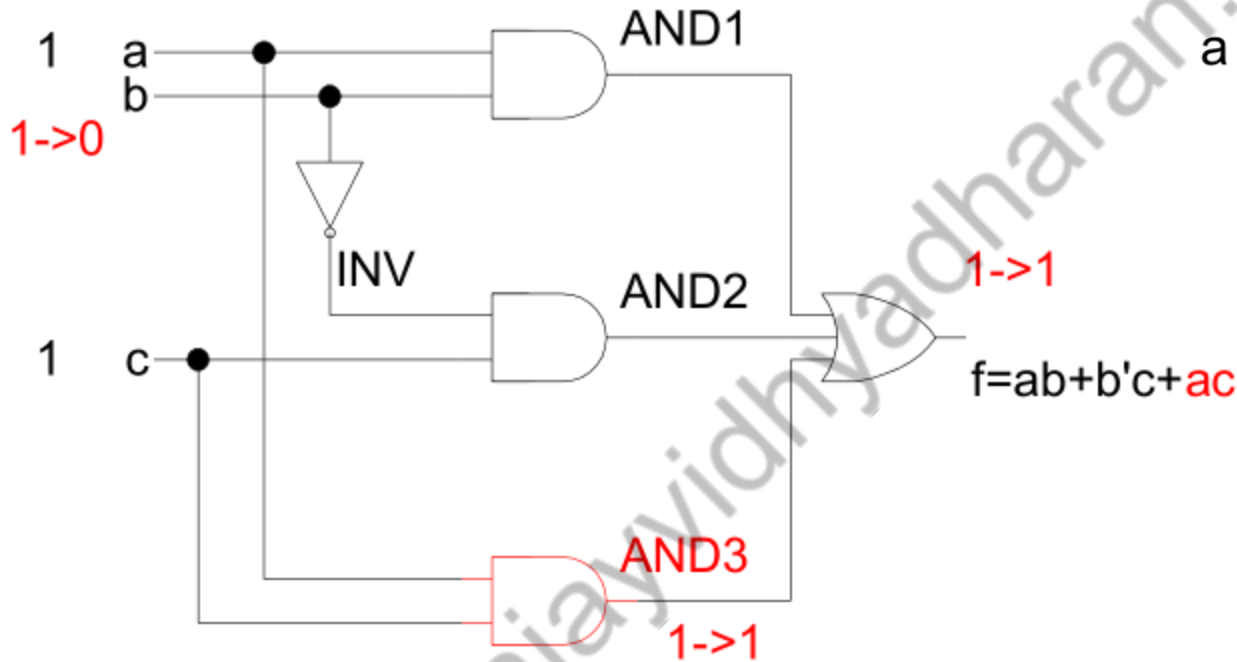

	bc	00	01	11	10
a	0	0	1	0	0
1	1	0	1	1	1


$$f = ab + b'c + ac$$

AND1 Check : $B=1, C=0$ AND2 Check : $A=0, C=1$

AND3 Check : $A=0$, Will render Both AND1 and AND 3 to Low

$A=1, B=0$ will activate AND2 and $B=0$ will activate AND 14

Experimental Results

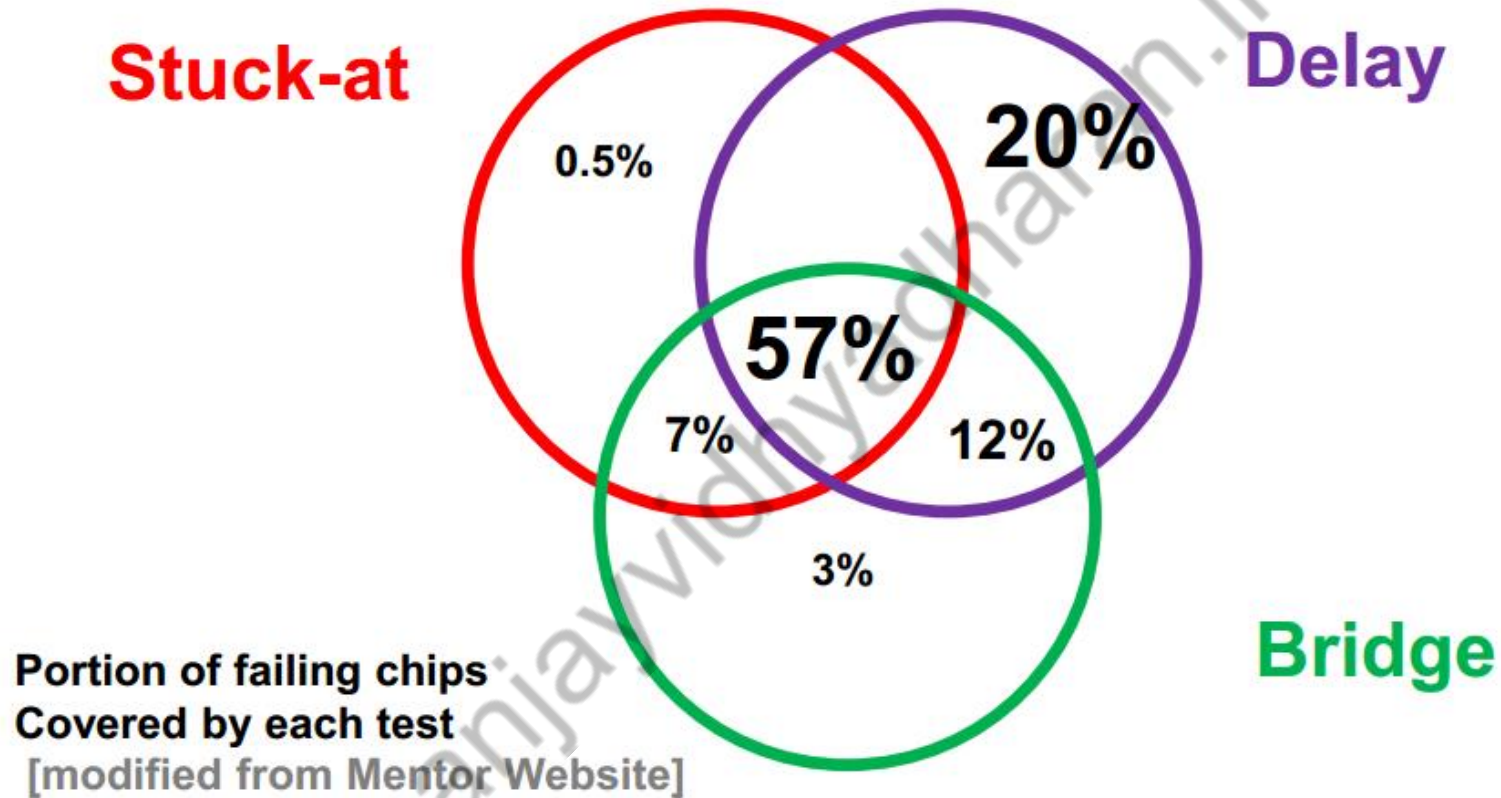


[2]/ Video lectures by Professor James Chien-Mo Li

Fault Models

in_0	in_1	Ctrl	Out	Detected SSF
0	1	0	0	
1	0	0	1	
1	0	1	0	
1	1	1	1	

Note: only four vectors for 3 inputs

 

Transistor faults


Two types of Transistor Faults

- Stuck-open -- a single transistor is permanently stuck in the open state irrespective of its gate voltage. Single Stuck-open detection requires two test patterns
- Stuck-short -- a single transistor is permanently shorted irrespective of its gate voltage. Detection by quiescent I_{DD}

http://ece-research.unm.edu/jimp/vlsi_test/slides/html/faults2.html

Transistor faults

Stuck-open

 

Fault-free circuit: $z = \overline{a+b}$

Faulty circuit: $z^f = \overline{a+b} + \overline{ab}z$


z : Previous value of z

Case 1: $a = b = 1$, z pulled down to 0

Case 2: $a = 1$, $b = 0$, z retains previous state

A test for a stuck-open fault requires two patterns
{ $ab = 00$, $ab = 10$ }

Transistor faults

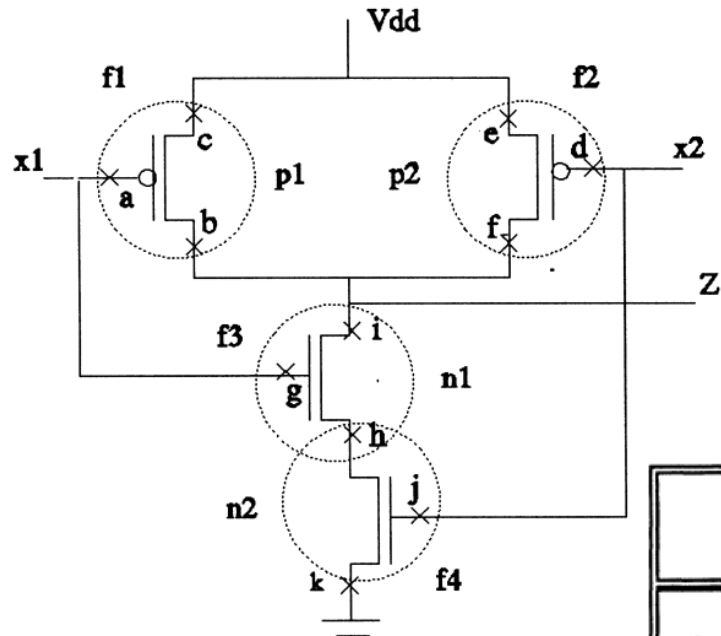


Two-pattern Tests for Stuck-open Faults

Faults	f1 (a,b,c)	f2 (d,e,f)	f3, f4 (g,h,i,j,k)
Initialization Vector (T1)	x1, x2 1 1	x1, x2 1 1	x1, x2 0 0 0 1 1 0
Test Vector (T2)	0 1	1 0	1 1

Automation available to optimize Stuck-at and Stuck-open Fault


Transistor faults

Stuck-on fault

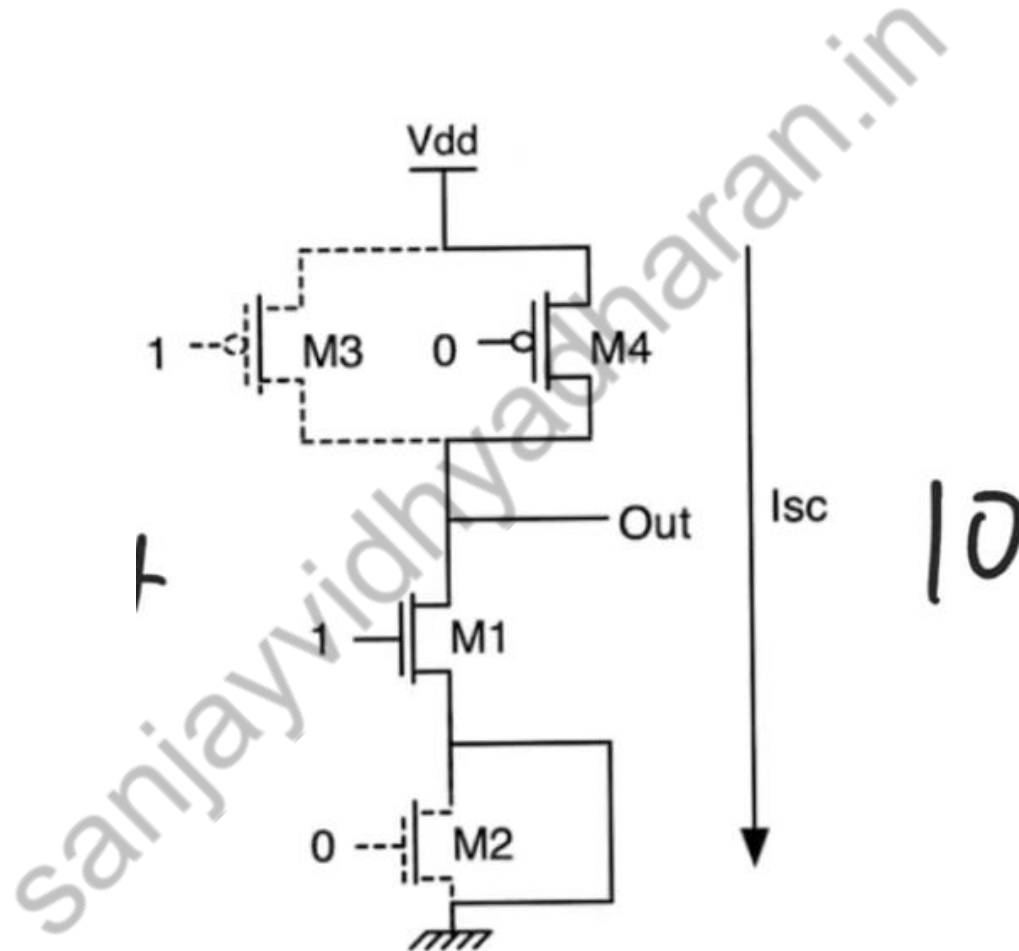

Transistor faults


SOP \neq TDF

 

$A_1B_1 \rightarrow A_2B_2$	Out_{good}	Detected SOP	Detected TDF
11 \rightarrow 01	0 \rightarrow 1	A_p	A STF; Out STR
10 \rightarrow 01	1 \rightarrow 1	-	A STF
11 \rightarrow 10	0 \rightarrow 1	B_p	B STF; Out STR
01 \rightarrow 10	1 \rightarrow 1	-	B STF
00 \rightarrow 11	1 \rightarrow 0	$A_N B_N$	A STR; B STR Out STF

[2]. Video lectures by Professor James Chien-Mo Li

Cell Aware Fault Model

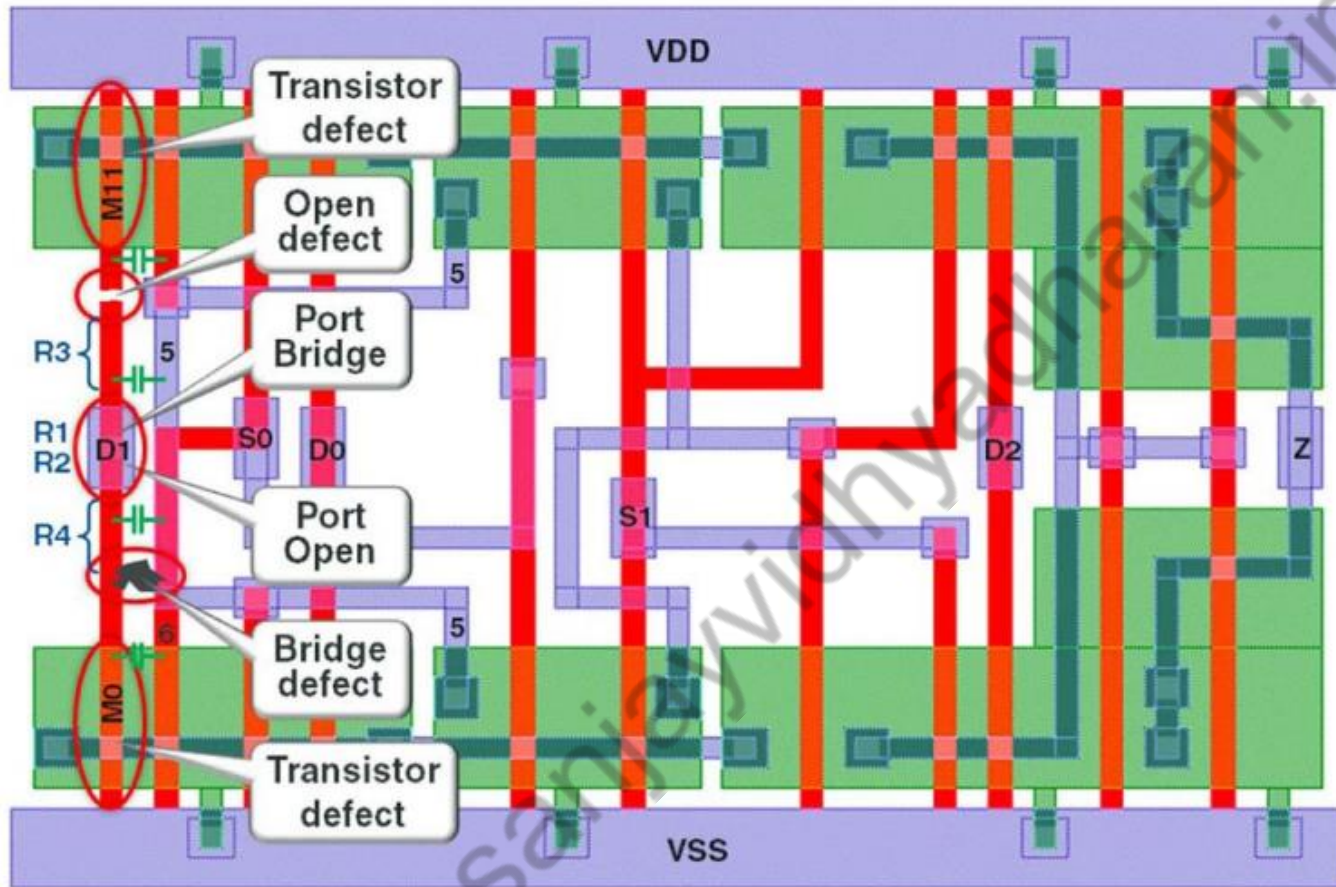


3X1 Mux

Hapke, Friedrich & Redemund, Wilfried & Glowatz, Andreas & Rajski, Janusz & Reese, M. & Hustava, Marek & Keim, Martin & Schlöffel, Jürgen & Fast, Anja. (2014). Cell-Aware Test. Computer-Aided Design of Integrated Circuits and Systems, IEEE Transactions on. 33. 1396-1409. 10.1109/TCAD.2014.2323216.

Cell Aware Fault Model

3X1 Mux

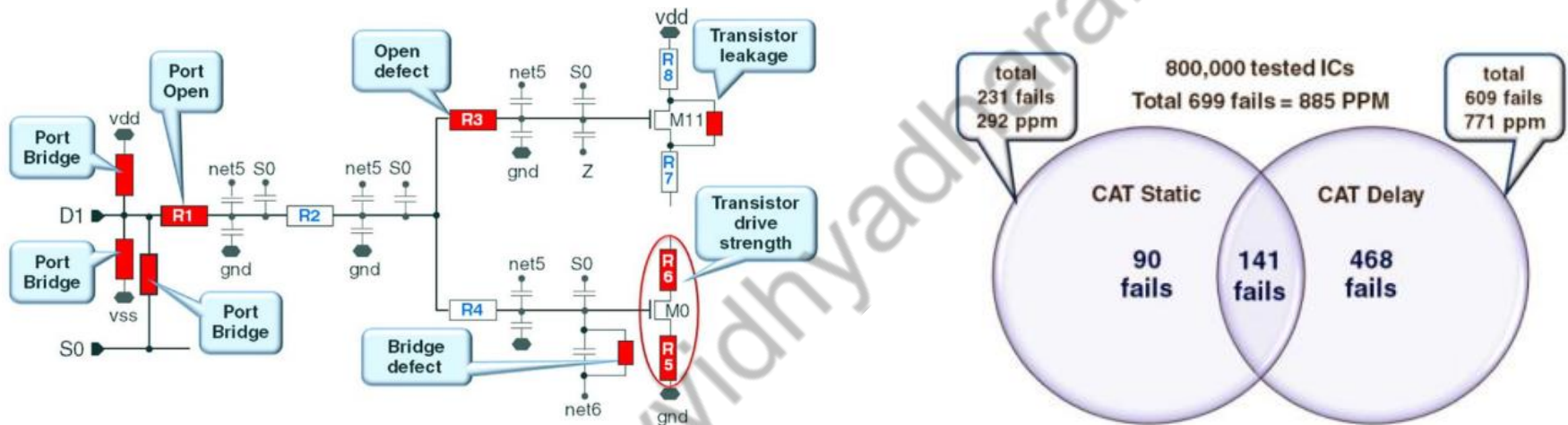


PPM reduction AMD 32 nm notebook processor.

Hapke, Friedrich & Redemund, Wilfried & Glowatz, Andreas & Rajski, Janusz & Reese, M. & Hustava, Marek & Keim, Martin & Schlöffel, Jürgen & Fast, Anja. (2014). Cell-Aware Test. Computer-Aided Design of Integrated Circuits and Systems, IEEE Transactions on. 33. 1396-1409. 10.1109/TCAD.2014.2323216.

Cell Aware Fault Model

in_0	in_1	Ctrl	Out	Detected SSF
0	1	0	0	In_0 (Sa1), Out (Sa1), Cntrl (Sa1)
1	0	0	1	In_0 (Sa0), Out (Sa0),
1	0	1	0	In_1 (Sa1), Cntrl (Sa0)
1	1	1	1	In_1 (Sa0)
0	0	1	0	Bridging w and in_0

 

Hapke, Friedrich & Redemund, Wilfried & Glowatz, Andreas & Rajski, Janusz & Reese, M. & Hustava, Marek & Keim, Martin & Schlöffel, Jürgen & Fast, Anja. (2014). Cell-Aware Test. Computer-Aided Design of Integrated Circuits and Systems, IEEE Transactions on. 33. 1396-1409. 10.1109/TCAD.2014.2323216.

References

1. “Essentials of Electronic Testing, for Digital, Memory and Mixed-Signal VLSI Circuits”, Michael L. Bushnell and Vishwani D. Agrawal, – Kluwer Academic Publishers (2000).
2. Video lectures by Professor James Chien-Mo Li
Lab. of Dependable Systems Graduate Institute of Electronics Engineering
National Taiwan University
https://www.youtube.com/watch?v=yfcoKOUV5DM&list=PLvd8d-SyI7hjk_Ci0zpTqImAtpEjdK5JF&index=1
3. http://ece-research.unm.edu/jimp/vlsi_test/slides/html/faults2.html

Thankyou

sanjayvidhyadharan.in