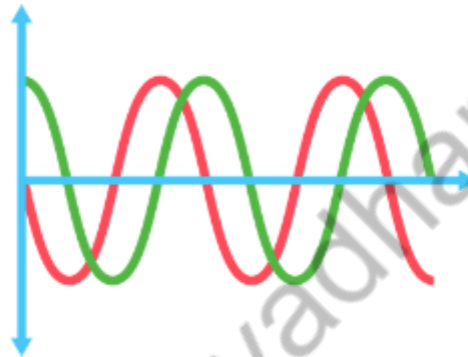


# Course: Advanced Analog IC Design



## Lecture 1: Bandgap Reference Circuits


Reference: Design of Analog CMOS Integrated Circuits by Behzad Razavi

**Prof. Sanjay Vidhyadharan**



**website: [sanjayvidhyadharan.in](http://sanjayvidhyadharan.in)**

## Current Mirrors

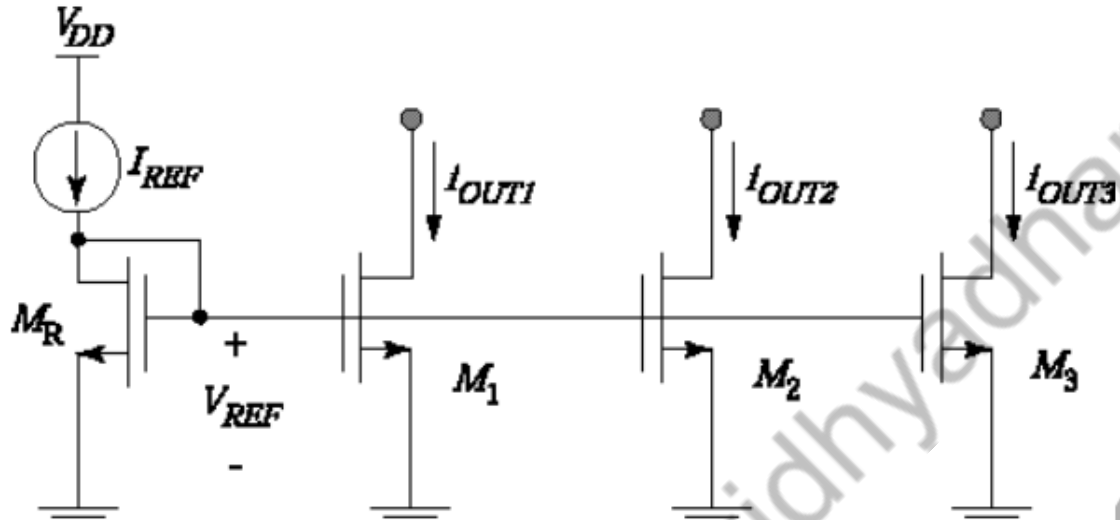

Desirable Specs for  $I_{REF}$

$$I_{REF} = \frac{1}{2} \mu_n C_{ox} (V_{GS} - V_{TN})^2 \cdot \left(\frac{W}{L}\right)_R$$

$$I_{OUT1} = \frac{1}{2} \mu_n C_{ox} (V_{GS} - V_{TN})^2 \cdot \left(\frac{W}{L}\right)_{OUT1}$$

$$I_{OUTN} = I_{REF} \frac{\left(\frac{W}{L}\right)_{OUTN}}{\left(\frac{W}{L}\right)_R}$$


1. Independent of Temp
2. Independent of Process variation
3. Independent of VDD

Circuit requirement could be

1. Constant GM
2. Proportional to Absolute Temperature

## 2. Constant Current Sources
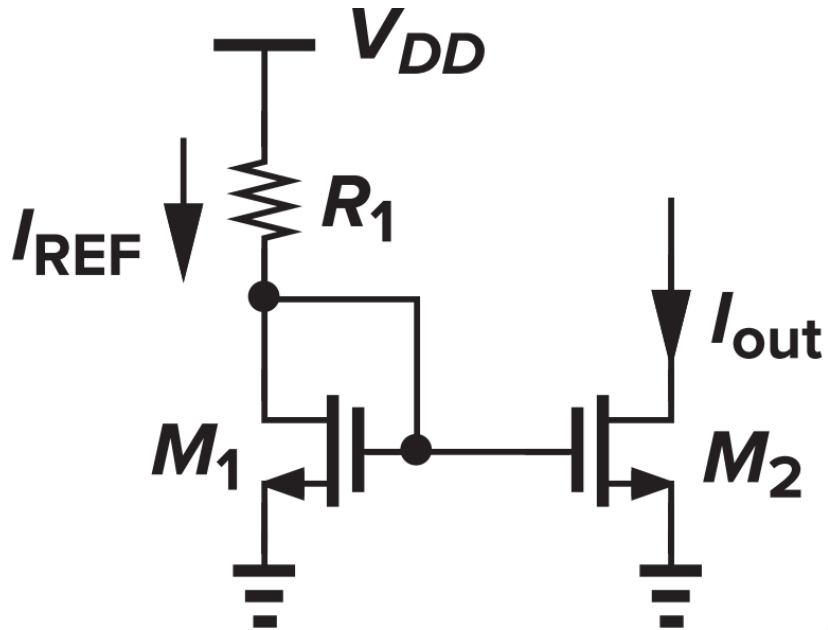
### Current mirror biasing using a resistor



$$I_{REF} = \frac{1}{2} \mu_n C_{ox} (V_{GS} - V_{TN})^2 \cdot \left(\frac{W}{L}\right)_R$$

$$I_{REF} = \frac{1}{2} \mu_n C_{ox} (V_{DD} - I_{REF} R - V_{TN})^2 \cdot \left(\frac{W}{L}\right)_R$$

$$\frac{\delta I_{REF}}{\delta V_{DD}} = \frac{1}{2} \mu_n C_{ox} 2(V_{DD} - I_{REF} R - V_{TN}) \cdot \left(\frac{W}{L}\right) \left(1 - R \frac{\delta I_{REF}}{\delta V_{DD}}\right)$$

$$g_m = \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_{TN})$$

$$\frac{\delta I_{REF}}{\delta V_{DD}} = g_{m1} \left(1 - R \frac{\delta I_{REF}}{\delta V_{DD}}\right)$$


$$\frac{\delta I_{REF}}{\delta V_{DD}} (g_{m1} + R) = g_{m1}$$

$$\Delta I_{REF} = \frac{g_{m1} \Delta V_{DD}}{g_{m1} + R}$$

$$\Delta I_{OUT} = \frac{\Delta V_{DD}}{1 + R/g_{m1}} \frac{(W/L)_2}{(W/L)_1}$$

# 2. Constant Current Sources

## Supply-Independent Biasing

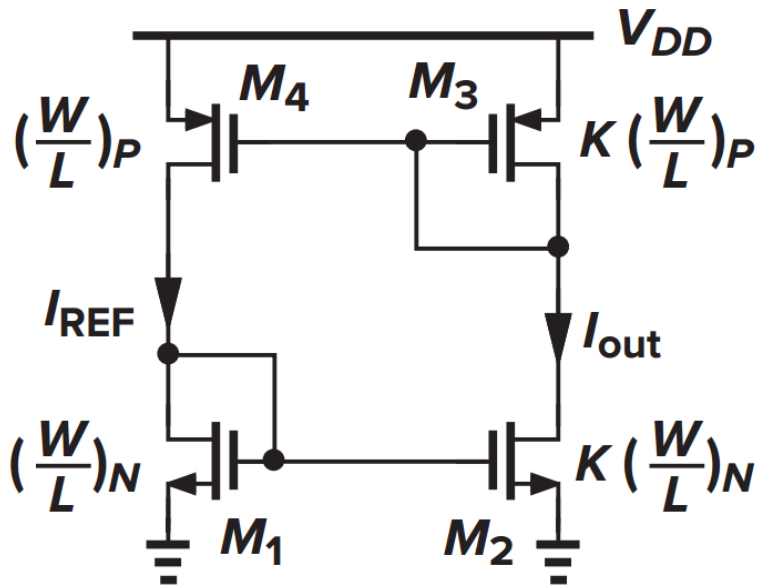

$$(W/L)_1 = 1 \quad (W/L)_2 = 10$$

$$(W/L)_4 = 2 \quad (W/L)_3 = 20$$

**Case 1**  $V_{DD} = 1.8 \text{ V}$ ,

From  $M_1$   $I_D$  Eqn :  $I_{REF} = 10 \mu\text{A} = \frac{1}{2} 200 \mu (V_{GS1} - 0.5)^2 1$

$$V_{GS1} = 0.82 \text{ V}$$

$$I_{OUT} = K I_{REF} = 100 \mu\text{A}$$

From  $M_3$   $I_D$  Eqn:  $I_3 = 100 \mu\text{A} = \frac{1}{2} 100 \mu (1.8 - V_{G3} - 0.5)^2 20$

$$V_{G3} = 0.98 \text{ V} = V_{DS2}$$

$$V_{ov2} = 0.82 - 0.5 = 0.32 \text{ V i.e } M_2 \text{ in saturation}$$

$$V_{SD} = 1.8 - 0.82 = 0.98 \text{ V}$$

$$V_{ov4} = 0.32 \text{ } M_4 \text{ in saturation}$$

**Case 2**  $V_{DD} = 1.6 \text{ V}$ ,

$$V_{G3} = 0.78 \text{ V } M_2 \text{ in saturation}$$

$$I_{REF} = \frac{1}{2} \mu_n C_{ox} (V_{GS1} - V_{TN})^2 \cdot \left(\frac{W}{L}\right)_1$$


$$I_{OUT} = \frac{1}{2} \mu_n C_{ox} (V_{GS1} - V_{TN})^2 \cdot \left(\frac{W}{L}\right)_2$$

$$I_{OUT} = K I_{REF}$$

Parameter	NMOSFETS	PMOSFETS	Units
$V_{TH0}$	0.5	-0.5	V
$\mu C_{ox}$	200	100	$\mu\text{A}/\text{V}^2$

# 2. Constant Current Sources

## Supply-Independent Biasing

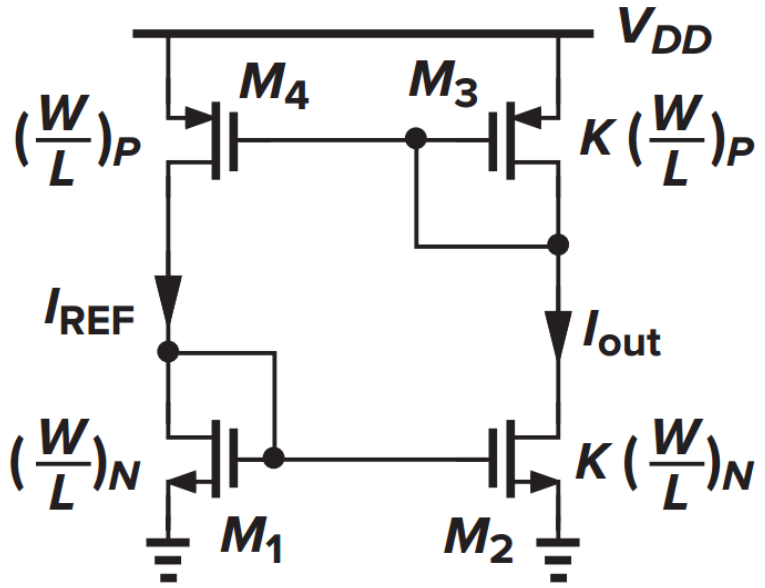

$(W/L)_1 = 1$   $(W/L)_2 = 10$   
 $(W/L)_4 = 2$   $(W/L)_3 = 20$

**Case 3**  $V_{DD} = 1.8 V$ ,

From  $M_1$   $I_D$  Eqn :  $I_{REF} = 20 \mu A = \frac{1}{2} 200 \mu (V_{GS1} - 0.5)^2 1$

$V_{GS1} = 0.95 V$

$I_{OUT} = K I_{REF} = 200 \mu A$

From  $M_1$   $I_D$  Eqn:  $I_3 = 200 \mu A = \frac{1}{2} 100 \mu (1.8 - V_{G3} - 0.5)^2 20$

$V_{G3} = 0.85 V = V_{DS2}$

$V_{ov2} = 0.95 - 0.5 = 0.45 V$  i.e  $M_2$  in saturation

$V_{SD} = 1.8 - 0.82 = 0.98 V$

$V_{ov4} = 0.32$   $M_4$  in saturation

**Case 4**  $V_{DD} = 1.6 V$ ,

$V_{G3} = 0.75 V$   $M_2$  in saturation


$I_{REF} = \frac{1}{2} \mu_n C_{ox} (V_{GS1} - V_{TN})^2 \cdot (\frac{W}{L})_1$

$I_{OUT} = \frac{1}{2} \mu_n C_{ox} (V_{GS1} - V_{TN})^2 \cdot (\frac{W}{L})_2$

$I_{OUT} = K I_{REF}$

Parameter	NMOSFETS	PMOSFETS	Units
$V_{TH0}$	0.5	-0.5	V
$\mu C_{ox}$	200	100	$\mu A/V^2$
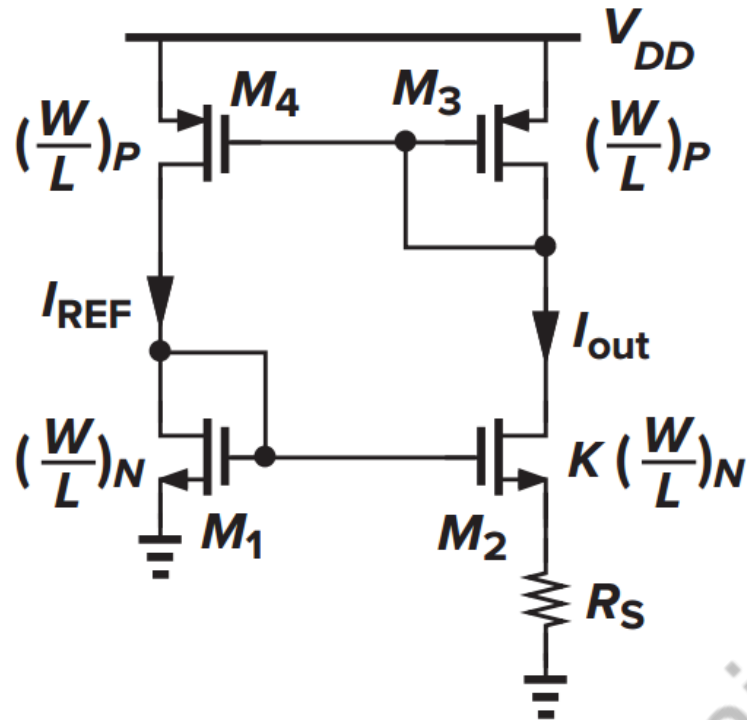
### Addition of $R_S$ to define the currents



Since M3 and M4 are identical  $I_{out} = I_{REF}$


$$\sqrt{\frac{2I_{out}}{\mu_n C_{ox} (W/L)_N} + V_{TH1}} = \sqrt{\frac{2I_{out}}{\mu_n C_{ox} K (W/L)_N} + V_{TH2} + I_{out} R_S}$$

$$\sqrt{\frac{2I_{out}}{\mu_n C_{ox} (W/L)_N} \left(1 - \frac{1}{\sqrt{K}}\right)} = I_{out} R_S$$


$$I_{out} = \frac{2}{\mu_n C_{ox} (W/L)_N} \cdot \frac{1}{R_S^2} \left(1 - \frac{1}{\sqrt{K}}\right)^2$$

The current is independent of the supply voltage but still a function of process and temperature.

## 2. Constant Current Sources

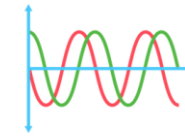
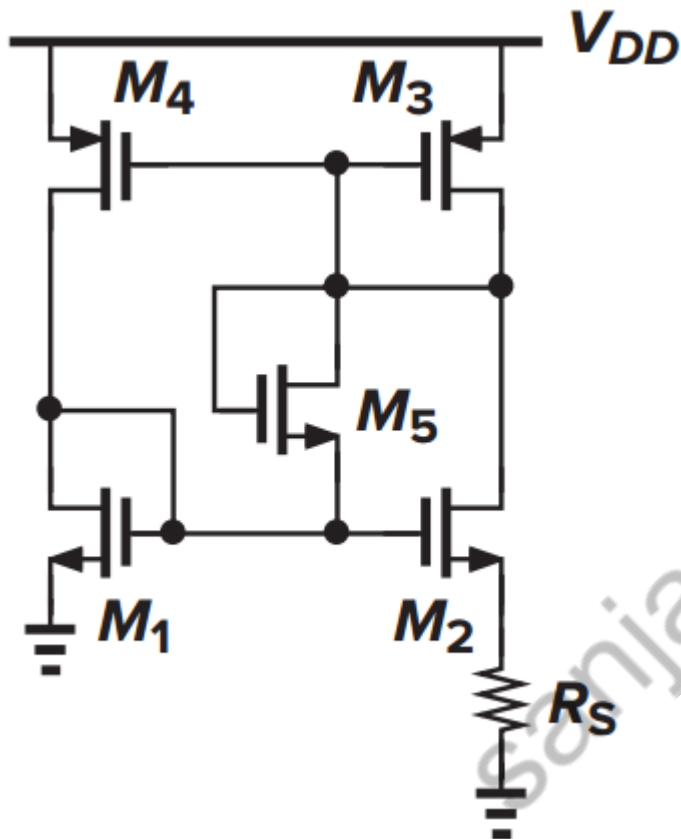
### Addition of start-up device to the circuit




$M_5$  provides a current path from  $V_{DD}$  through  $M_3$  and  $M_1$  to ground upon start-up.

$$V_{TH1} + V_{TH5} + |V_{TH3}| < V_{DD}$$

Latter to ensure that  $M_5$  remains off after start-up.

$$V_{GS1} + V_{TH5} + |V_{GS3}| > V_{DD}$$

# 3. Temperature-Independent References

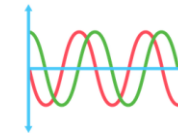

## Negative-TC Voltage

For a bipolar device

$$I_C = I_S \exp(V_{BE}/V_T)$$

$$I_S = bT^{4+m} \exp \frac{-E_g}{kT} \quad \text{saturation current}$$

$E_g \approx 1.12$  eV is the bandgap energy of silicon.

$$V_T = kT/q.$$


$I_C$  approximately doubles for every  $10^\circ\text{C}$  rise in temperature

$$V_{BE} = V_T \ln(I_C/I_S)$$

$$\frac{\partial V_{BE}}{\partial T} = \frac{\partial V_T}{\partial T} \ln \frac{I_C}{I_S} - \frac{V_T}{I_S} \frac{\partial I_S}{\partial T}$$

With  $V_{BE} \approx 750$  mV and  $T = 300$  K
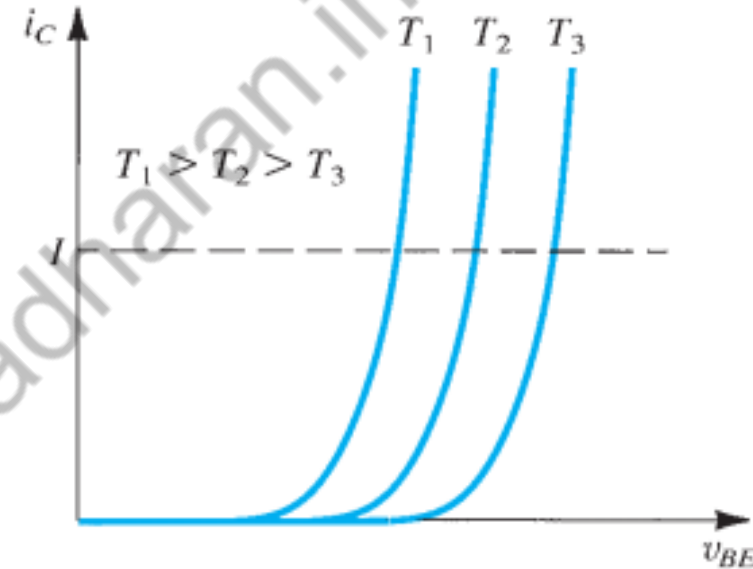
$$\partial V_{BE}/\partial T \approx -1.5 \text{ mV/K}$$




Effect of temperature on the  $i_C$ - $V_{BE}$  characteristic. At a constant emitter current (broken line),  $V_{BE}$  changes by  $-2$  mV/ $^\circ\text{C}$ .

Ref: Sedra Smith



# 3. Temperature-Independent References

## Positive-TC Voltage

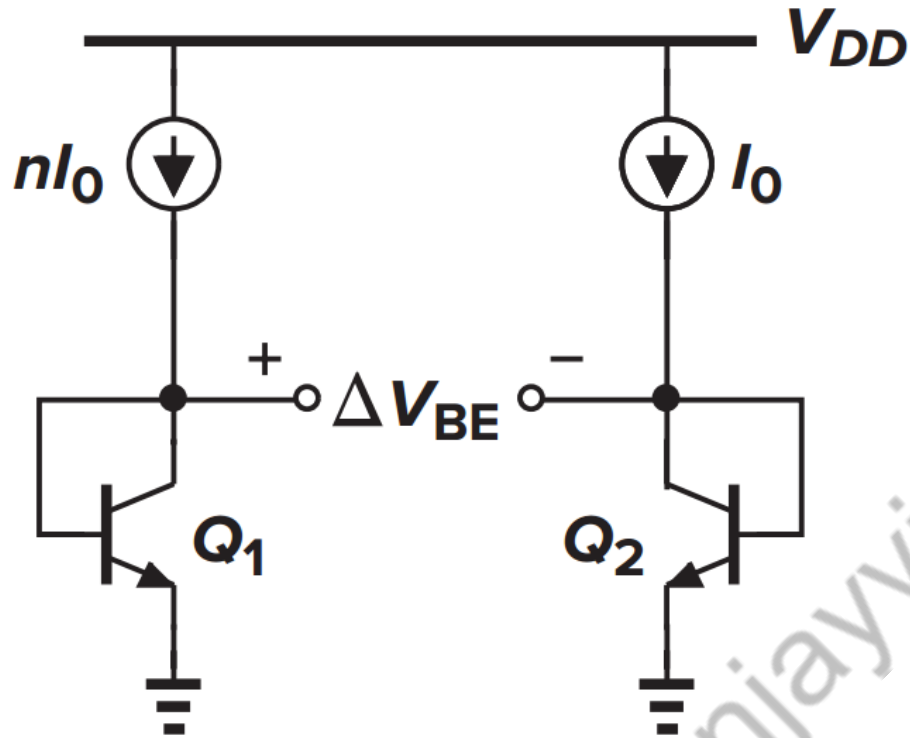

PTAT : Proportional To Absolute Temperature

## Generation of PTAT voltage.

$$\begin{aligned} \Delta V_{BE} &= V_{BE1} - V_{BE2} \\ &= V_T \ln \frac{nI_0}{I_{S1}} - V_T \ln \frac{I_0}{I_{S2}} \\ &= V_T \ln n \end{aligned}$$

## Positive-TC Voltage

$$V_T = kT/q$$

$$K = 1.380649 \times 10^{-23} \text{ m}^2 \text{ kg s}^{-2} \text{ K}^{-1}$$

$$Q = 1.60217663 \times 10^{-19} \text{ coulombs}$$


$$\partial V_T / \partial T \approx +0.087 \text{ mV/K,}$$

$$\frac{\partial \Delta V_{BE}}{\partial T} = \frac{k}{q} \ln n$$

we have  $\ln n \approx 17.2$  and hence  $n = 2.95 \times 10^7$ !! We can have TC of +1.5 mV/K so as to cancel the TC of the base-emitter voltage at  $T = 300 \text{ K}$

# 3. Temperature-Independent References

## Positive-TC Voltage

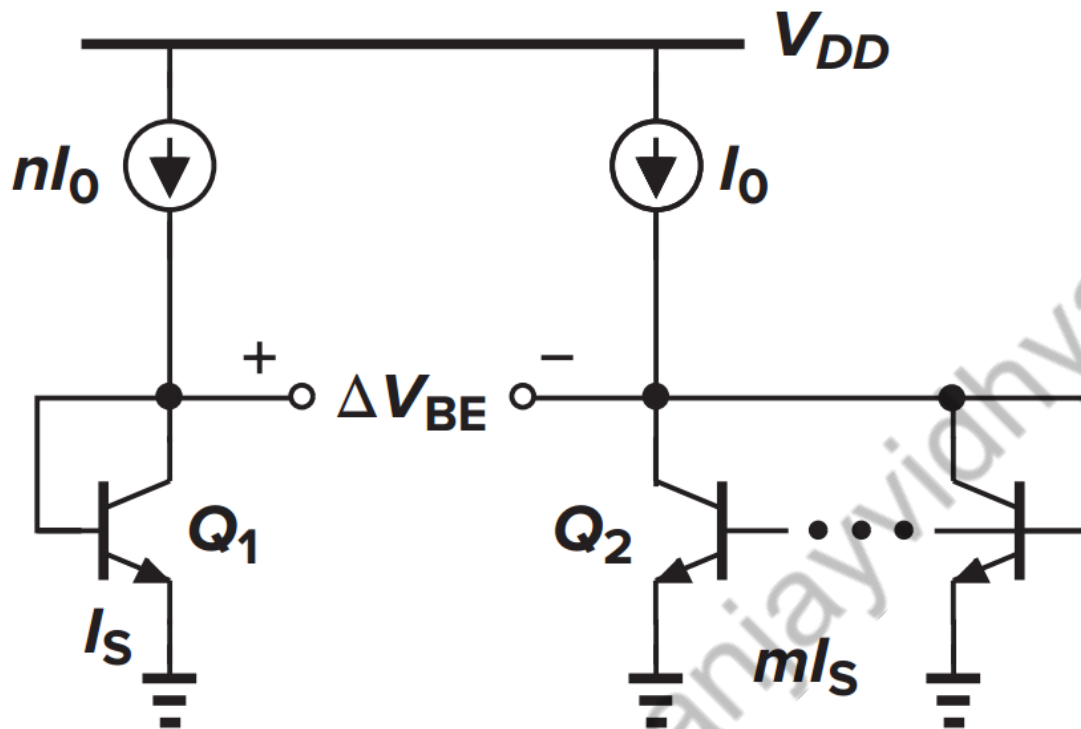

$$\begin{aligned} \Delta V_{BE} &= V_T \ln \frac{nI_0}{I_S} - V_T \ln \frac{I_0}{mI_S} \\ &= V_T \ln(nm) \end{aligned}$$

Temperature coefficient =  $(k/q) \ln(nm)$

# 3. Temperature-Independent References

## Band gap Reference

Assuming  $V_{O1} = V_{O2}$


$$V_{BE1} = RI + V_{BE2}$$

$$RI = V_{BE1} - V_{BE2} = V_T \ln n$$


$$V_{O2} = V_{BE2} + V_T \ln n$$

$V_{O2}$  is a temperature-independent reference if  $\ln n \approx 17.2$
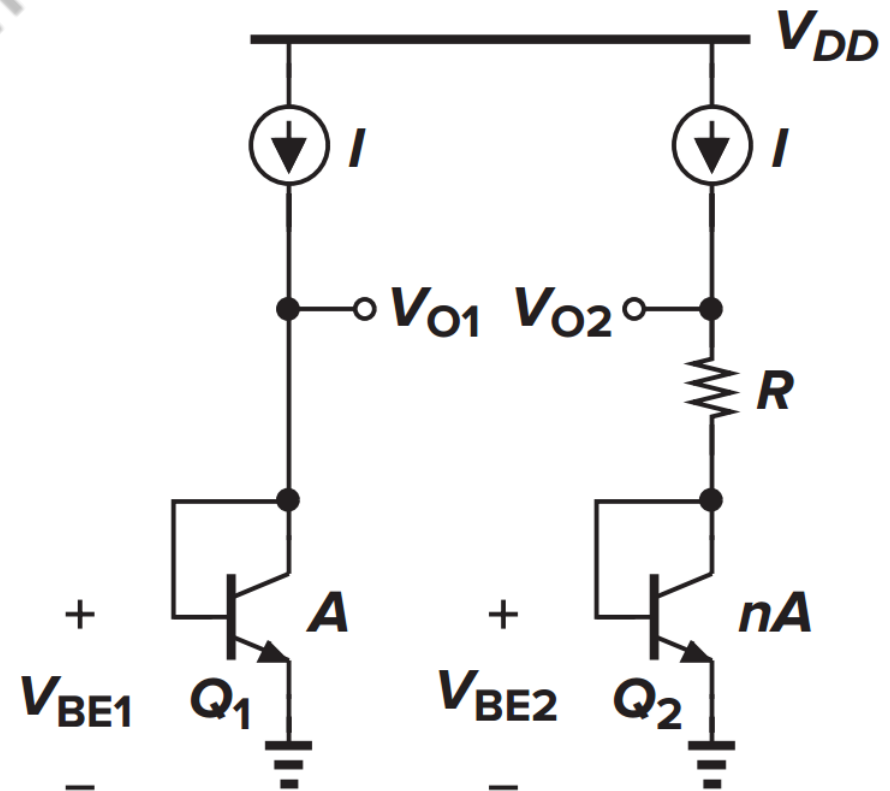
$$V_{REF} \approx V_{BE} + 17.2V_T \approx 1.25 \text{ V}$$



# 3. Temperature-Independent References

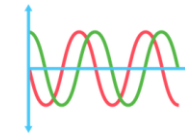

## Band gap Reference

Assuming  $V_{O1} = V_{O2}$

$$V_{BE1} = RI + V_{BE2}$$

$$RI = V_{BE1} - V_{BE2} = V_T \ln n$$


$$V_{O2} = V_{BE2} + V_T \ln n$$

$V_{O2}$  is a temperature-independent reference if  $\ln n \approx 17.2$


### Three Issues

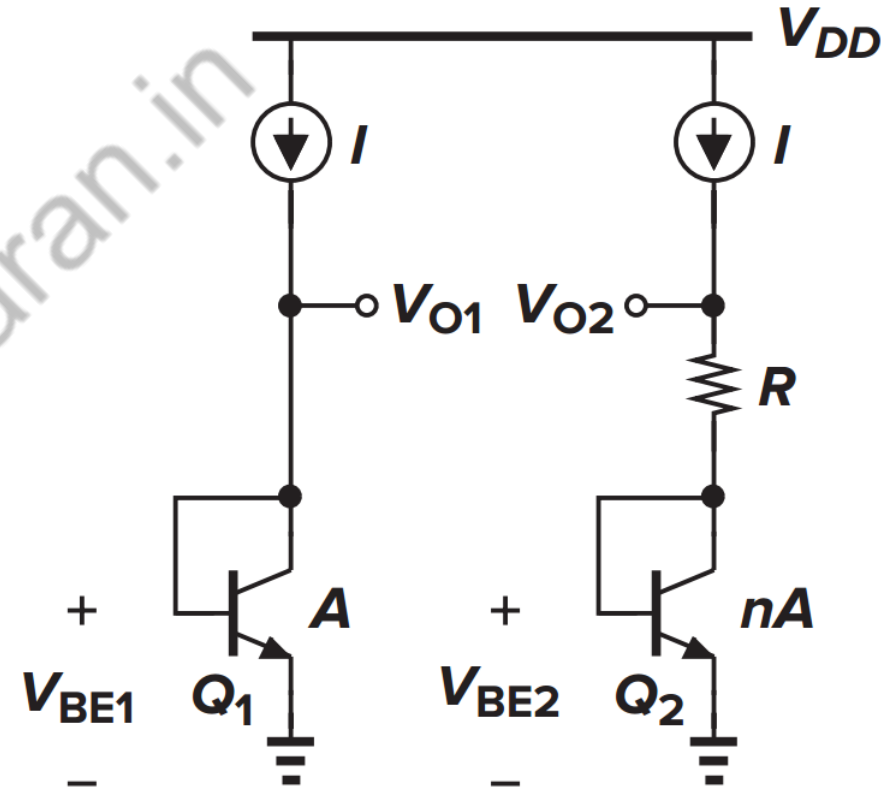1. Guarantee that  $V_{O1} = V_{O2}$
2.  $\ln n = 17.2$  translates to a prohibitively large  $n$
3.  $V_{O2} \approx V_{BE1} \approx 800 \text{ mV}$  whereas,

For temperature independence, we must have  $V_{O2} = V_{BE2} + 17.2V_T \approx 1.25 \text{ V}$



# 3. Temperature-Independent References

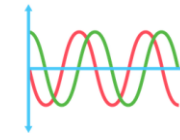

## Band gap Reference

$$V_{O1} = V_{O2}$$


$$I = \frac{V_T \ln(n)}{R_3}$$

$$V_{out} = \frac{V_T \ln(n) R_2}{R_3} + V_T \ln(n) + V_{BE2}$$

$$V_{out} = V_T \ln(n) \left(1 + \frac{R_2}{R_3}\right) + V_{BE2}$$



$$\left(1 + \frac{R_2}{R_3}\right) \ln n \approx 17.2.$$

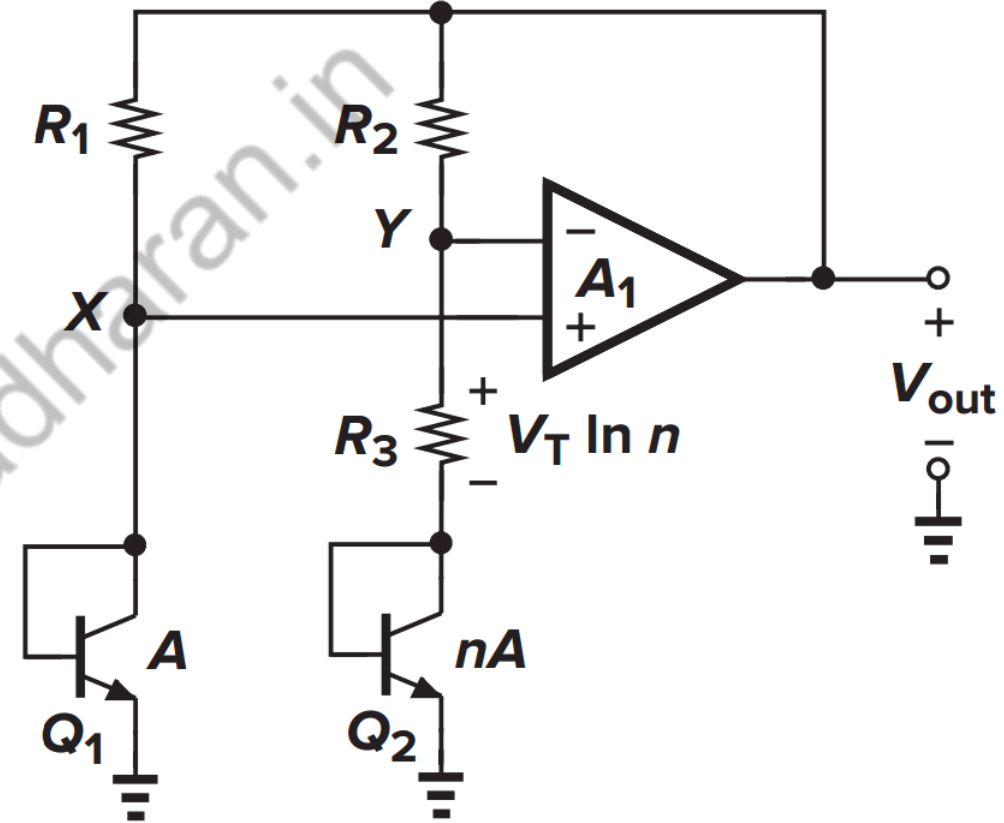we may choose  $n = 31$  and  $R_2/R_3 = 4$ .




# 3. Temperature-Independent References

## Band gap Reference

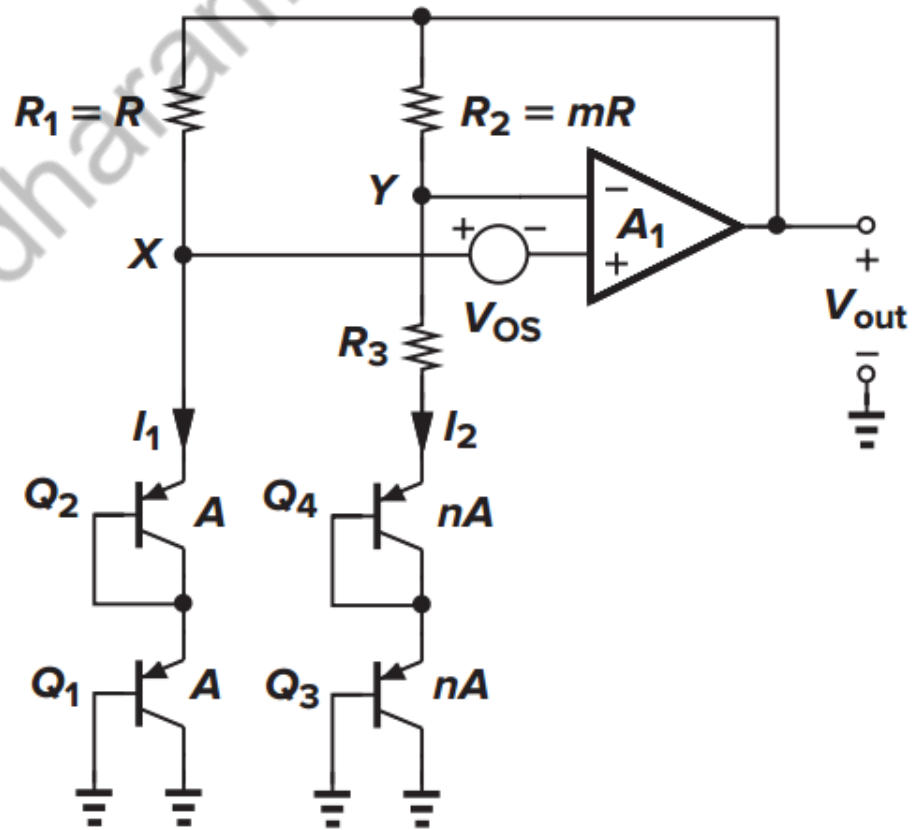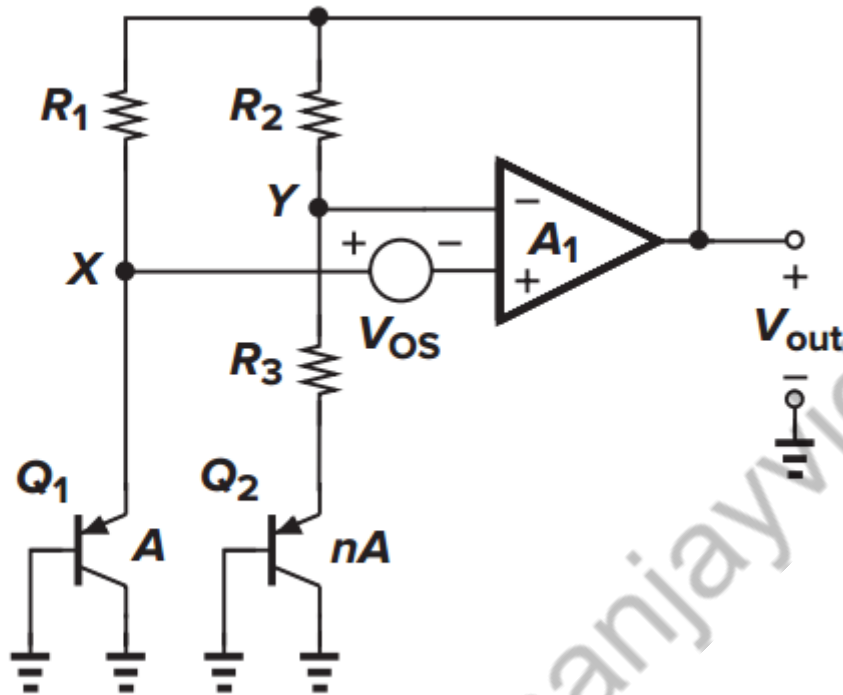


$$V_{out} \approx 2 \times 1.25 \text{ V} = 2.5 \text{ V}$$


# 3. Temperature-Independent References

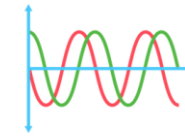

## Band gap Reference

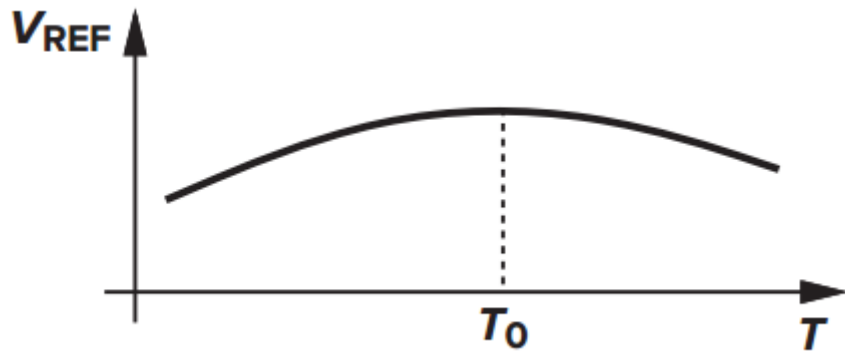

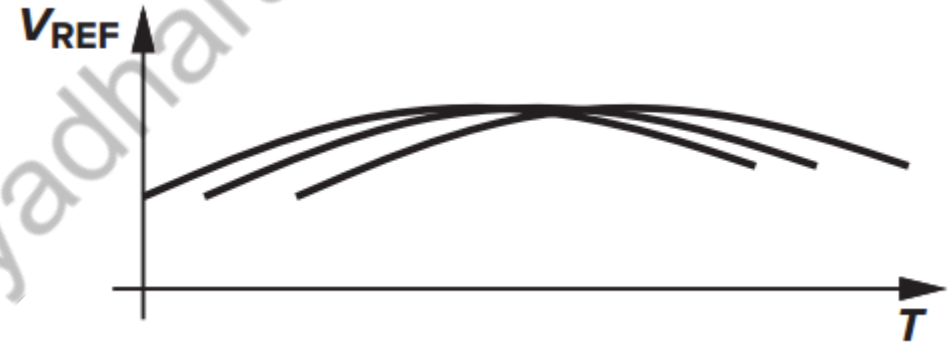
Curvature in temperature dependence of a bandgap voltage




Variation of the zero-TC temperature for different samples.

# 3. Temperature-Independent References

## Band gap Reference

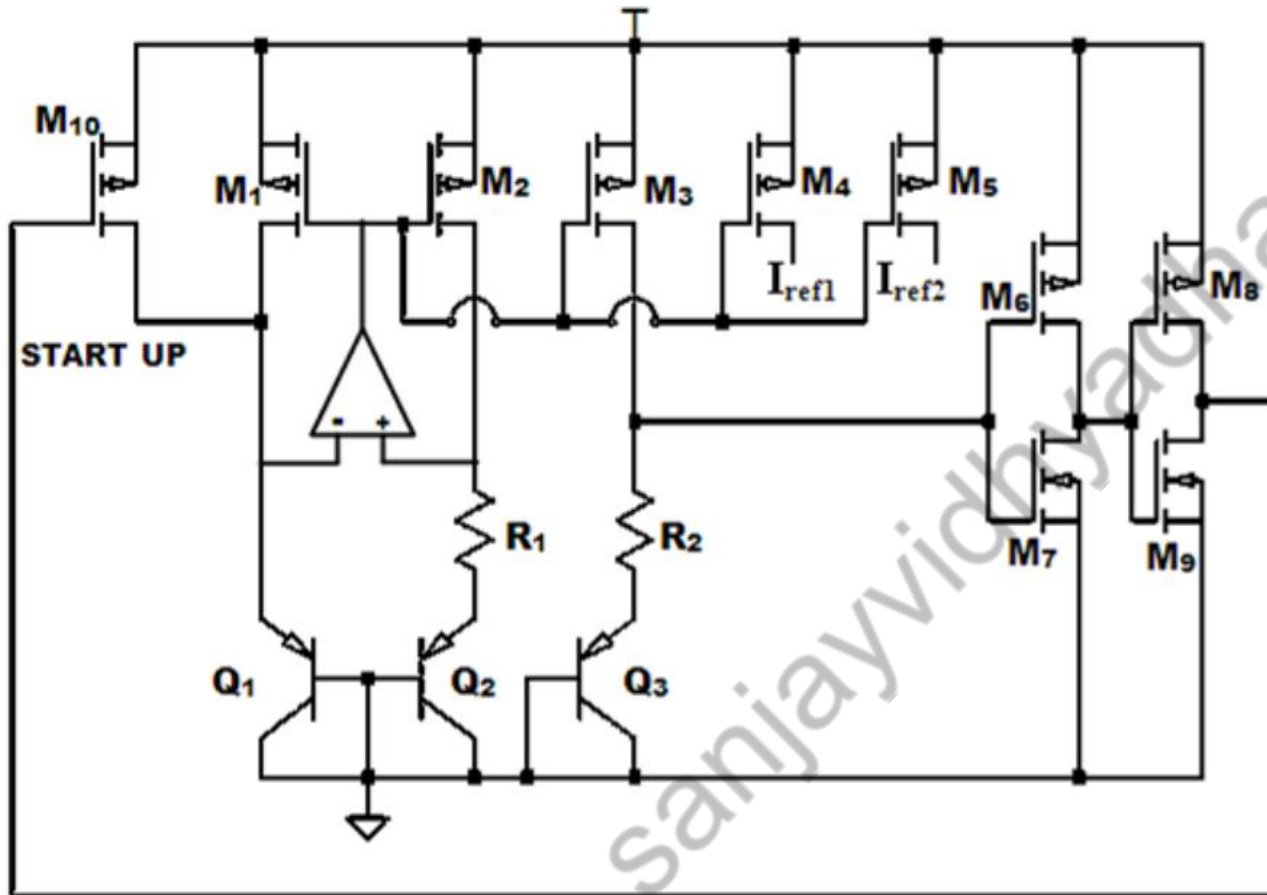


Bandgap reference circuit

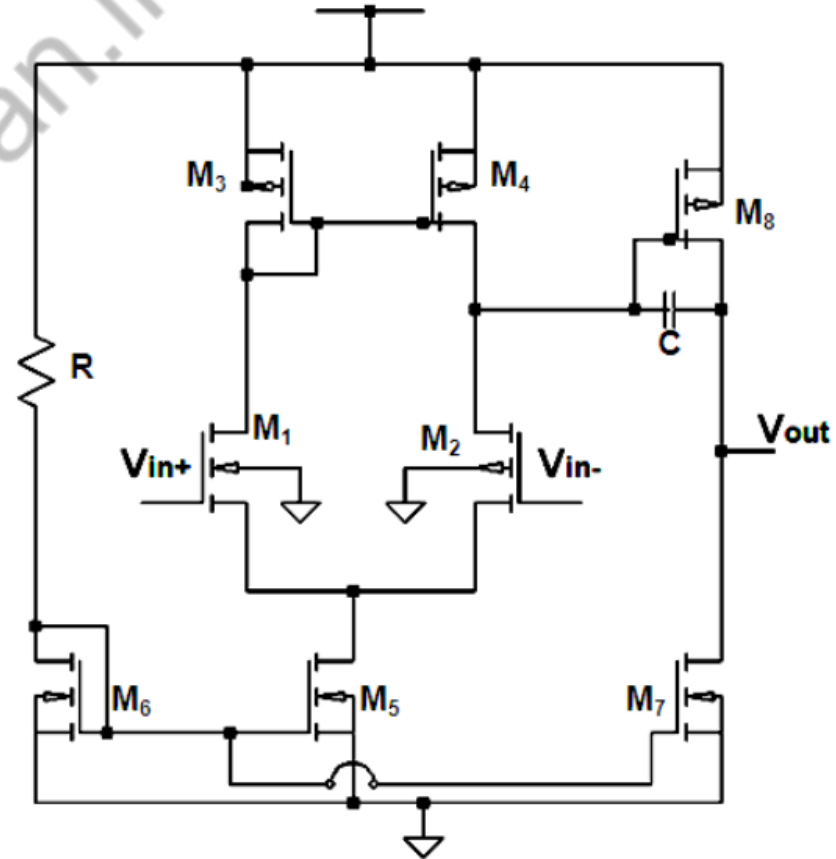


Op-amp used in bandgap reference circuit



# 3. Temperature-Independent References

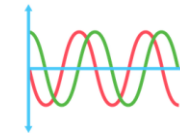


## Band gap Reference

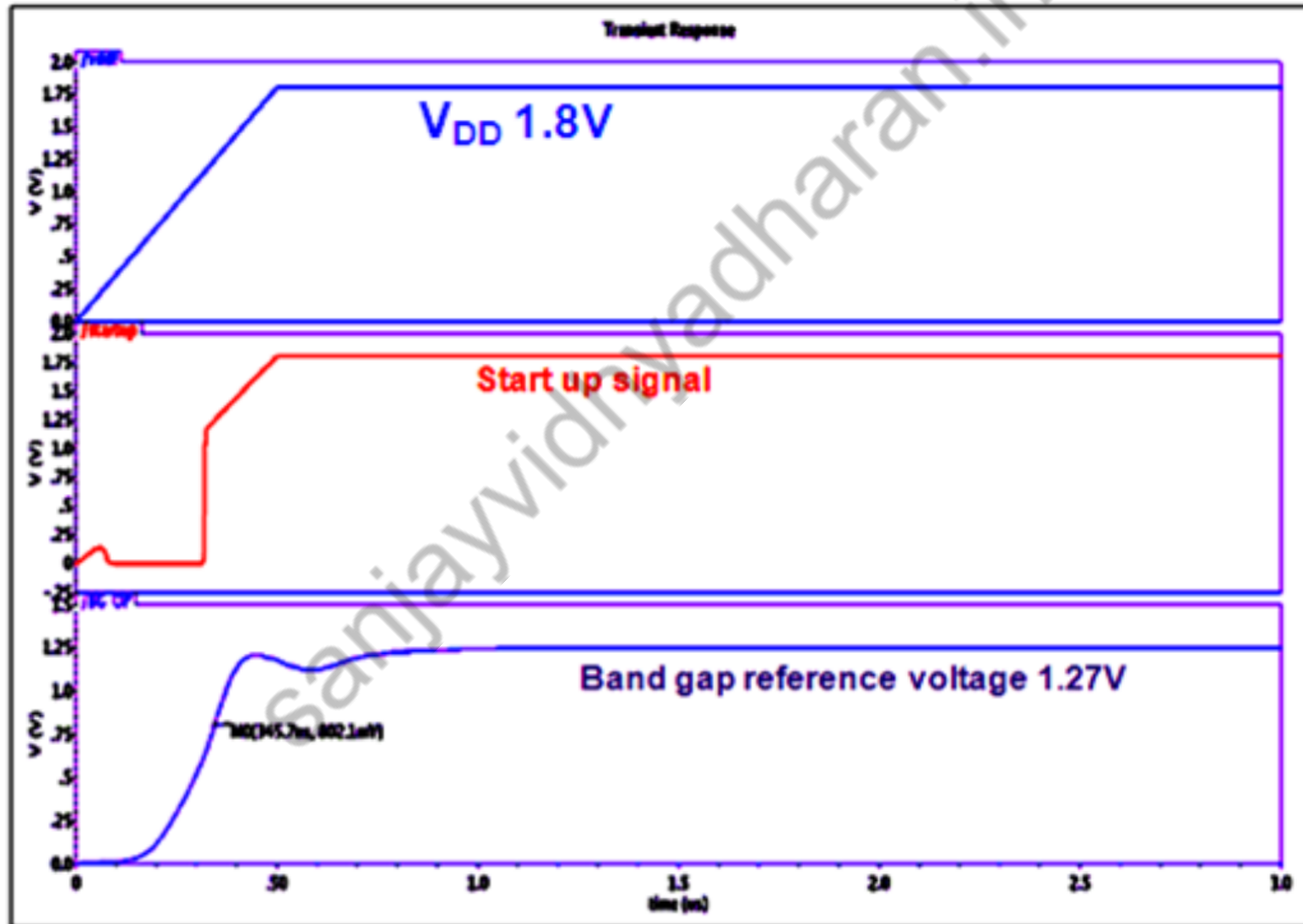


# 3. Temperature-Independent References


## Linear regulator circuit

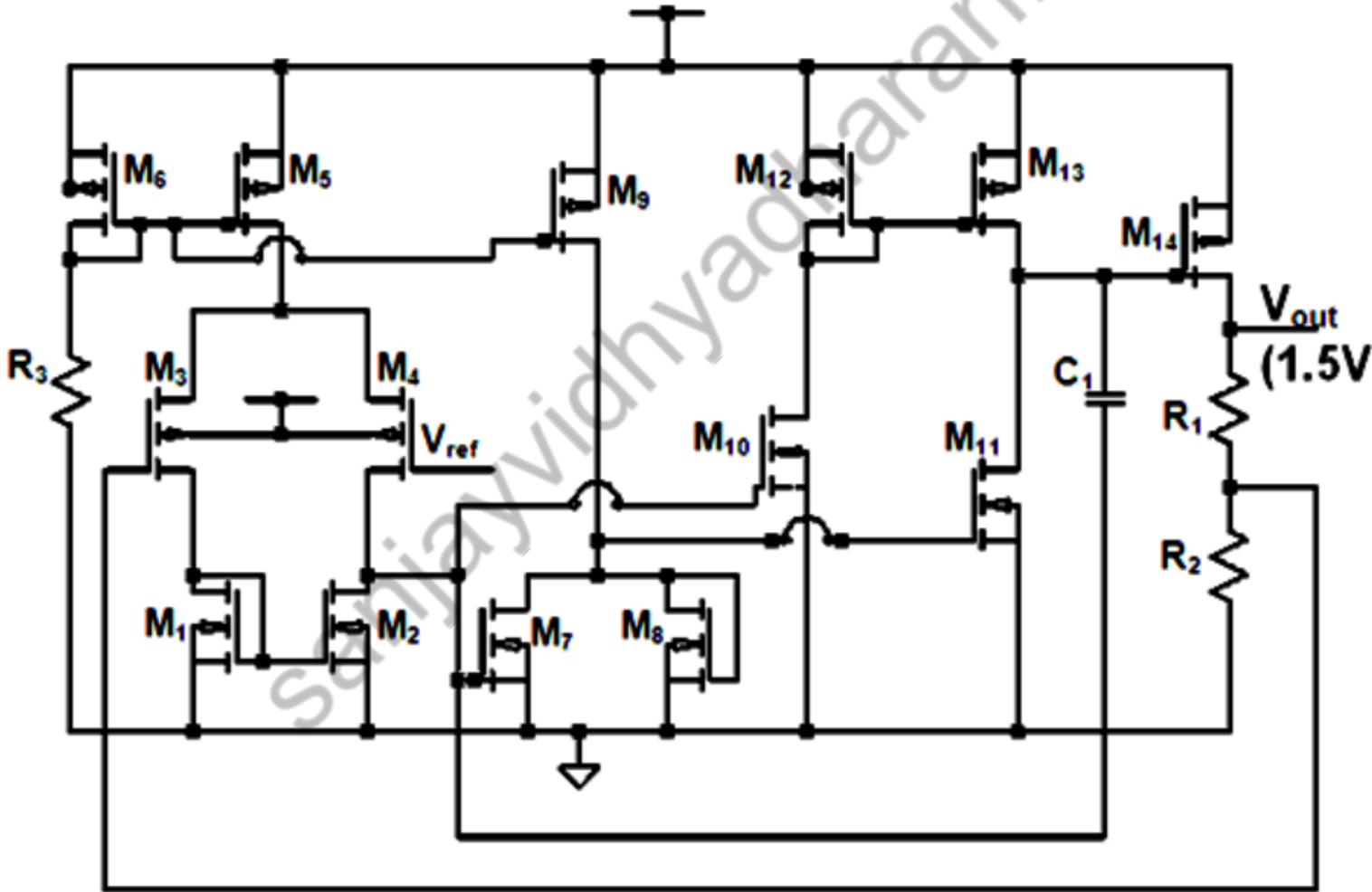



# 3. Temperature-Independent References

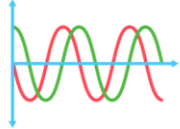

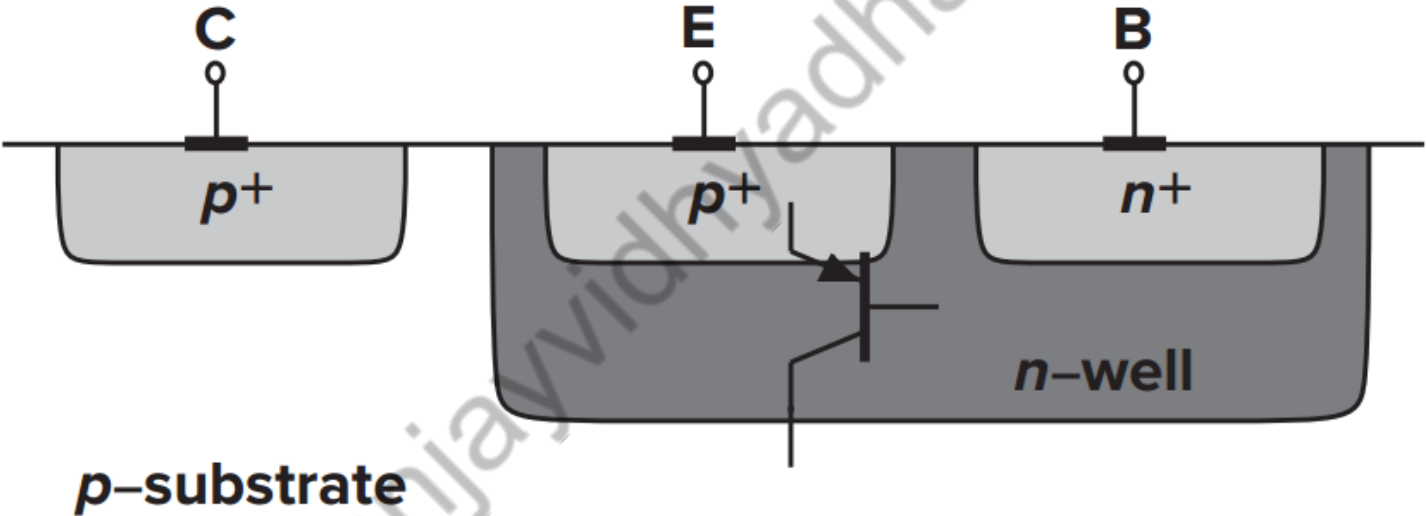
Realization of a *pn*p bipolar transistor in CMOS technology



# 4. PTAT Current Generation

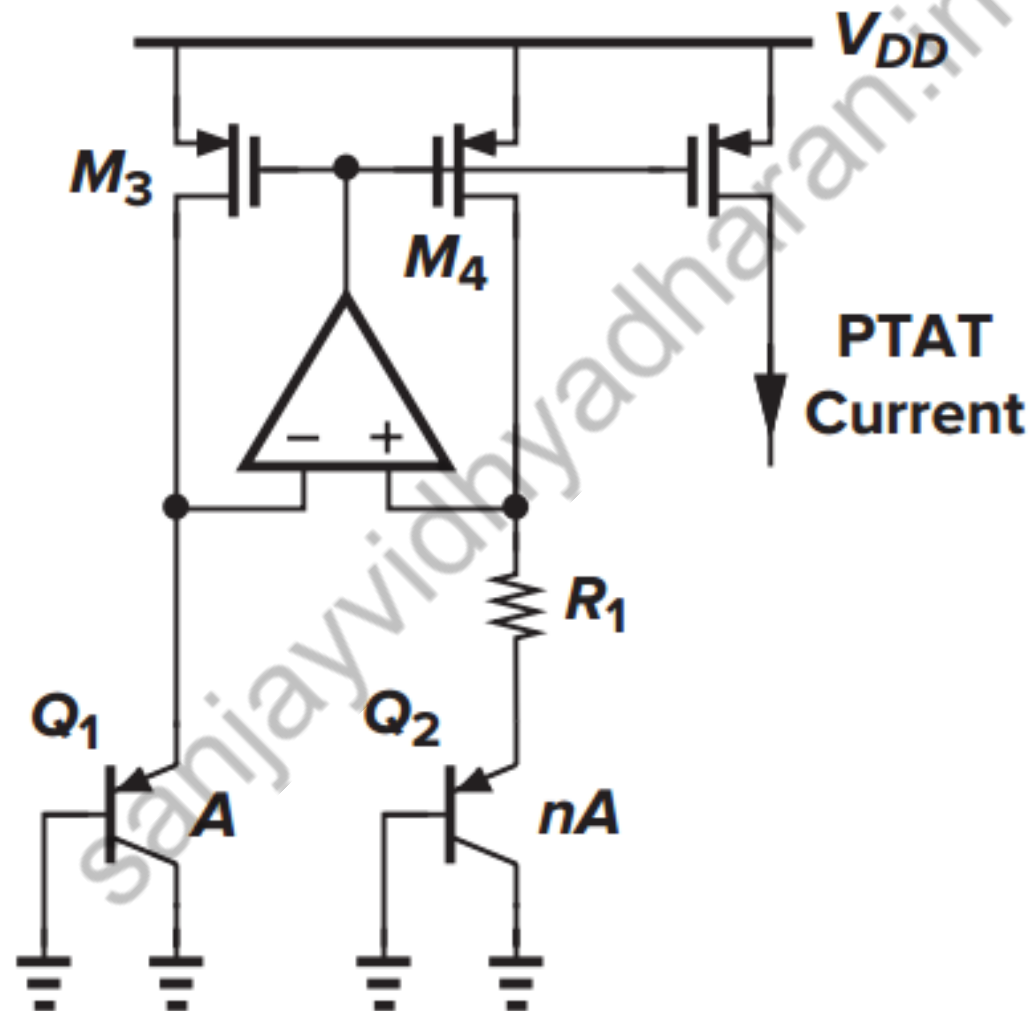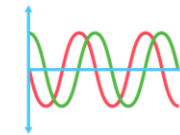


# 5. Constant-Gm Biasing

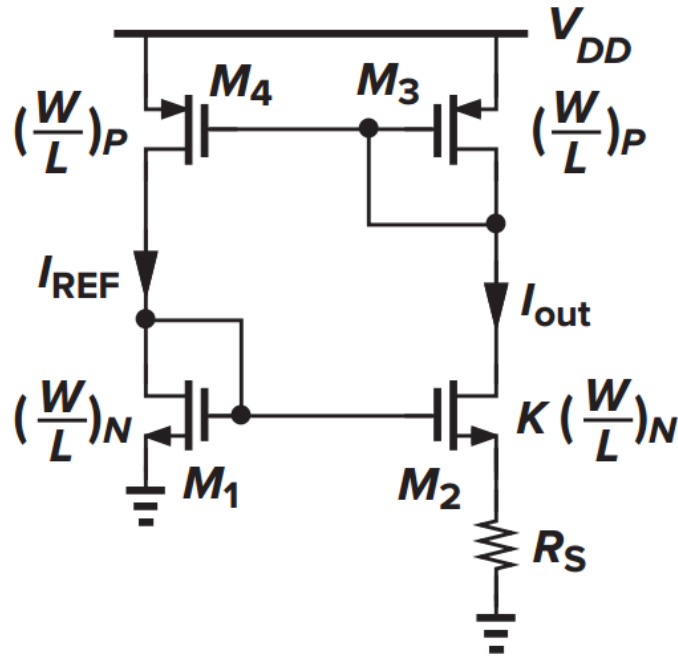


$$I_{out} = \frac{2}{\mu_n C_{ox} (W/L)_N} \cdot \frac{1}{R_S^2} \left(1 - \frac{1}{\sqrt{K}}\right)^2$$

$$g_{m1} = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_N I_{D1}}$$
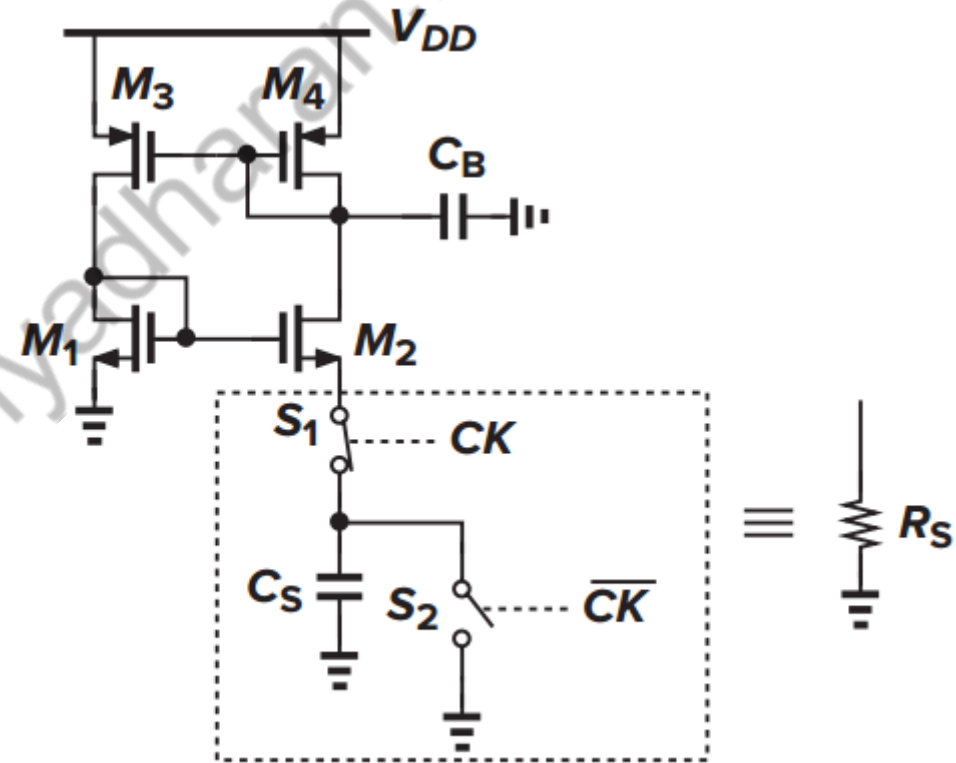
$$= \frac{2}{R_S} \left(1 - \frac{1}{\sqrt{K}}\right)$$



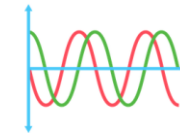

**Thankyou**

sanjayvidhyadharan.in