




Advanced VLSI Design

Lecture 14


Combinational Components

By Prof. Sanjay Vidhyadharan

Decoders

 


(a) active-high output;

 


(b) active-low output.

Decoders

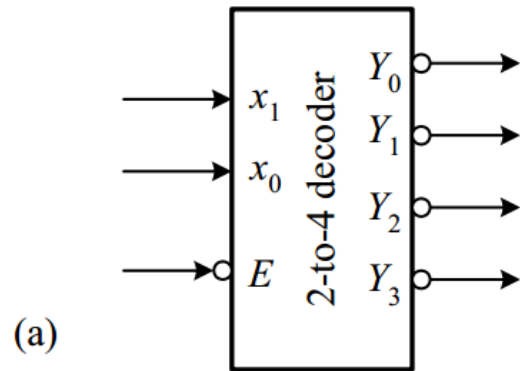

E	x_1	x_0	Y_3	Y_2	Y_1	Y_0
1	ϕ	ϕ	1	1	1	1
0	0	0	1	1	1	0
0	0	1	1	1	0	1
0	1	0	1	0	1	1
0	1	1	0	1	1	1

(b)

 

(c)


For most practical decoders, one or more enable controls may also be embedded into decoders to allow expanding capability

Decoders

Implementing a 3 to 8 decoder using two 2 to 4 decoders with enable pin


X	Y	Z
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
1	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0
0	0	1	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	0	0	1	0	0	0
0	0	0	0	0	1	0	0
0	0	0	0	0	0	1	0
0	0	0	0	0	0	0	1

 


Decoders

 Implementing a 3 to 8 decoder using two 2 to 4 decoders with enable pin



Decoders


3 to 8 decoder

 

Decoders

4 to 16 decoder


INPUTS				OUTPUTS															
A ₃	A ₂	A ₁	A ₀	Y ₁₅	Y ₁₄	Y ₁₃	Y ₁₂	Y ₁₁	Y ₁₀	Y ₉	Y ₈	Y ₇	Y ₆	Y ₅	Y ₄	Y ₃	Y ₂	Y ₁	Y ₀
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1
0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0
0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0
0	0	1	1	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0
0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0
0	1	0	1	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0
0	1	1	1	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0
1	0	1	1	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0

 

Decoders

4 to 16 decoder


INPUTS				OUTPUTS															
A ₃	A ₂	A ₁	A ₀	Y ₁₅	Y ₁₄	Y ₁₃	Y ₁₂	Y ₁₁	Y ₁₀	Y ₉	Y ₈	Y ₇	Y ₆	Y ₅	Y ₄	Y ₃	Y ₂	Y ₁	Y ₀
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1
0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0
0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0
0	0	1	1	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0
0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0
0	1	0	1	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0
0	1	1	1	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0
1	0	1	1	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0
1	1	1	1	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0

 


Decoders

Implementing function using Decoders

 
$$F = \sum (1, 2, 4, 7) = X'Y'Z + X'YZ' + XY'Z' + XYZ$$




Decoder Applications

 

Encoders

 


(a) active-high output;

 


(b) active-low output.

Priority Encoder

 


(a)

 

Input				Binary output			1-out-of-4 output			
I_3	I_2	I_1	I_0	A_1	A_0	$Valid$	EP_3	EP_2	EP_1	EP_0
0	0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	1	0	0	0	1
0	0	1	ϕ	0	1	1	0	0	1	0
0	1	ϕ	ϕ	1	0	1	0	1	0	0
1	ϕ	ϕ	ϕ	1	1	1	1	0	0	0

(b)

Priority Encoder

 

Priority Encoder

D_0	D_1	D_2	D_3
1	0	0	0
0	1	0	0
0	0	1	0
0	0	0	1

X	Y
0	0
0	1
1	0
1	1

Encoder

$$X = D_2 + D_3$$

$$Y = D_1 + D_3$$

D_0	D_1	D_2	D_3
1	0	0	0
X	1	0	0
X	X	1	0
X	X	X	1
0	0	0	0

X	Y	V
0	0	1
0	1	1
1	0	1
1	1	1
X	X	0

Priority Encoder

$$X = D_2 + D_3$$

$$Y = D_1 D_2' + D_3$$

$$V = D_0 + D_1 + D_2 + D_3$$

Priority Encoder


Priority Encoder

$$X = D_2 + D_3$$


$$Y = D_1 D_2' + D_3$$

$$V = D_0 + D_1 + D_2 + D_3$$


D_0	D_1	D_2	D_3	X	Y	V
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1
0	0	0	0	X	X	0

 

Priority Encoder

 


Binary to Gray Using Encoder-Decoder

 


4-to-16 Line Decoder Implemented with two 3-to-8 Decoders


Encoder Applications

 

Encoder Applications

 


Encoder Applications

 

Multiplexers


2-to-1 multiplexer

 


The (a) logic symbol and (b) logic circuit of a gate-based 2-to-1 multiplexer.

Multiplexers

4-to-1 multiplexer


 


S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

 


Multiplexers

Tri State Buffer

  


Switch implementation of tri-state gate.

2:1 MUX using Tri-state buffer

 


Multiplexers

 4:1 MUX using Tri-state buffers and 2 to 4 Decoder




74HCT125 Quad Tri-State Buffer

LOGIC SYMBOL

 

Multiplexers

 


Multiplexers

Boolean Function implementation

$$F(X, Y, Z) = \sum (1, 2, 6, 7)$$

X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 


Multiplexers

Boolean Function implementation

$$F(X, Y, Z) = \sum (1, 2, 6, 7)$$


X	Y	Z	F	
0	0	0	0	F = Z
0	0	1	1	
0	1	0	1	F = Z'
0	1	1	0	
1	0	0	0	F = 0
1	0	1	0	
1	1	0	1	F = 1
1	1	1	1	

4:1
Multiplexer

 


Multiplexers


Boolean Function implementation

 

Multiplexers


 


Multiplexers

 


Switch-based 2-to-1 multiplexers: (a) TG-switch circuit; (b) Nmos circuit; (c) Lean Integration with Pass-Transistors (LEAP) circuit; (d) CMOS circuit; (e) CPL circuit; (f) DPL circuit.


Demultiplexers

  

Demultiplexers

 

E	S_1	S_0	Y_0	Y_1	Y_2	Y_3
1	ϕ	ϕ	0	0	0	0
0	0	0	D	0	0	0
0	0	1	0	D	0	0
0	1	0	0	0	D	0
0	1	1	0	0	0	D

 

Magnitude Comparators

sanjayvidhyadharan.in

Magnitude Comparator

1	0	1
1	1	0

sanjayvidhyadharan.in

Magnitude Comparator

1	0	1
1	1	0

sanjayvidhyadharan.in

Magnitude Comparator

1-Bit Comparator

A_0

B_0

Let G_0 indicate greater, L_0 indicate Lesser and E_0 indicate equal

A_0	B_0	G_0	L_0	E_0
0	0	0	0	1
0	1	0	1	0
1	0	1	0	0
1	1	0	0	1

$$G_0 = A_0 B_0$$

$$L_0 = A_0' B_0$$

$$E_0 = (A_0 \oplus B_0)' = (A_0 \odot B_0) = (G_0 + L_0)'$$


Magnitude Comparator

1-Bit Comparator

A_0

B_0

0

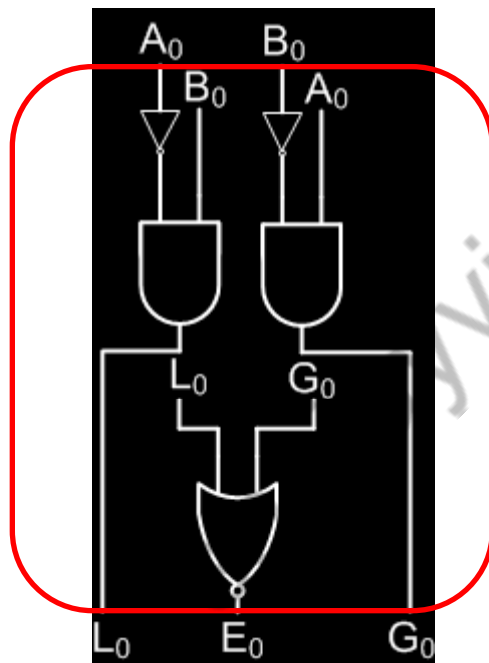

$$G_0 = A_0 B_0'$$

$$L_0 = A_0' B_0$$

$$E_0 = (G_0 + L_0)' = (A_0 \oplus B_0)'$$

$B_0 \quad A_0$

1-Bit
Comp

$L_0 \quad E_0 \quad G_0$


Magnitude Comparator

2-Bit Comparator

A $A_1 A_0$
B $B_1 B_0$

$A = B$ When $A_0 = B_0$ and $A_1 = B_1$

$$E = E_0 \cdot E_1$$

 

Magnitude Comparator



2-Bit Comparator

A A_1A_0

B B_1B_0

$A > B$ When $A_1 > B_1$ OR
When $A_1 = B_1$ and $A_0 > B_0$

$$G = G_1 + E_1 \cdot G_0$$

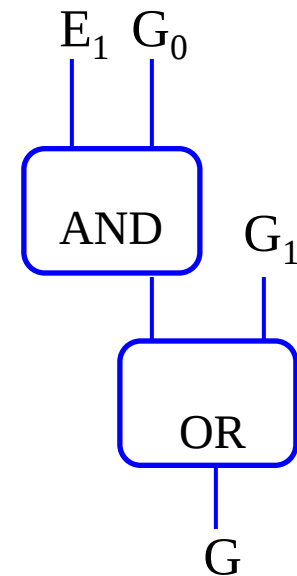 


Magnitude Comparator

2-Bit Comparator

A $A_1 A_0$
 B $B_1 B_0$
 1 0

$A < B$ When $A_1 < B_1$ OR
 When $A_1 = B_1$ and $A_0 < B_0$

$$L = L_1 + E_1 \cdot L_0$$

 

Magnitude Comparator

1-Bit Comparator

$$G = G_0 \quad L = L_0 \quad E = E_0$$

2-Bit Comparator

$$G = G_1 + E_1 \cdot G_0 \quad L = L_1 + E_1 \cdot L_0 \quad E = E_1 \cdot E_0$$

3-Bit Comparator


$$G = G_2 + E_2 \cdot G_1 + E_2 \cdot E_1 \cdot G_0$$

$$E = E_2 \cdot E_1 \cdot E_0$$

$$L = L_2 + E_2 \cdot L_1 + E_2 \cdot E_1 \cdot L_0$$

Magnitude Comparator

4-Bit Comparator

 


$$E = E_3 \cdot E_2 \cdot E_1 \cdot E_0$$


$$G = G_3 + E_3 \cdot G_2 + E_3 \cdot E_2 \cdot G_1 + E_3 \cdot E_2 \cdot E_1 \cdot G_0$$

$$L = L_3 + E_3 \cdot L_2 + E_3 \cdot E_2 \cdot L_1 + E_3 \cdot E_2 \cdot E_1 \cdot L_0$$


Magnitude Comparator

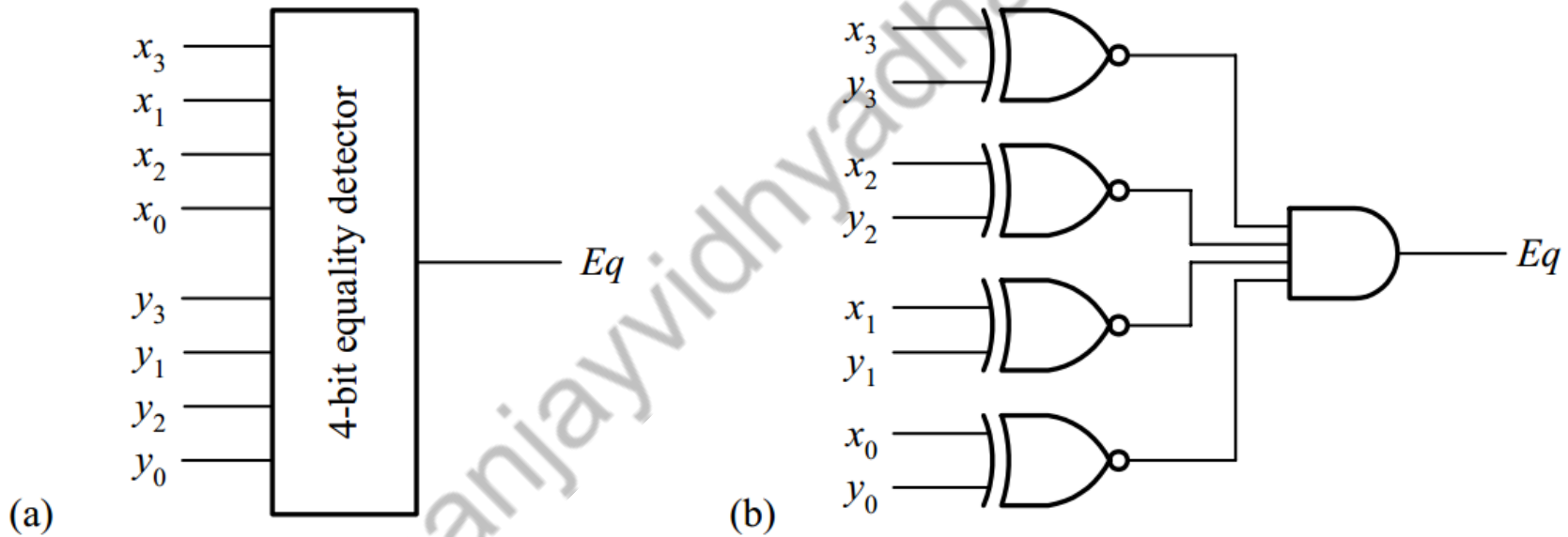


Magnitude Comparator

 


Magnitude Comparator

 

Magnitude Comparator

 

Magnitude Comparator

 



Thank you

sanjayvidhyadharan.in