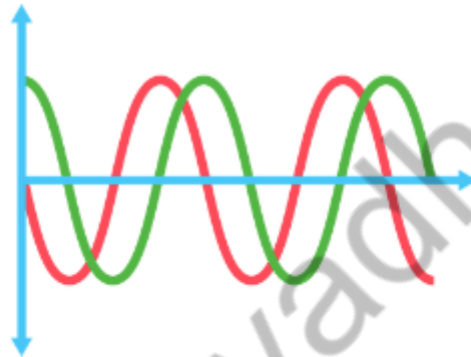


**Course : RF Microelectronics**





**Lecture 3: Low Noise Amplifiers**


**Prof. Sanjay Vidhyadharan**



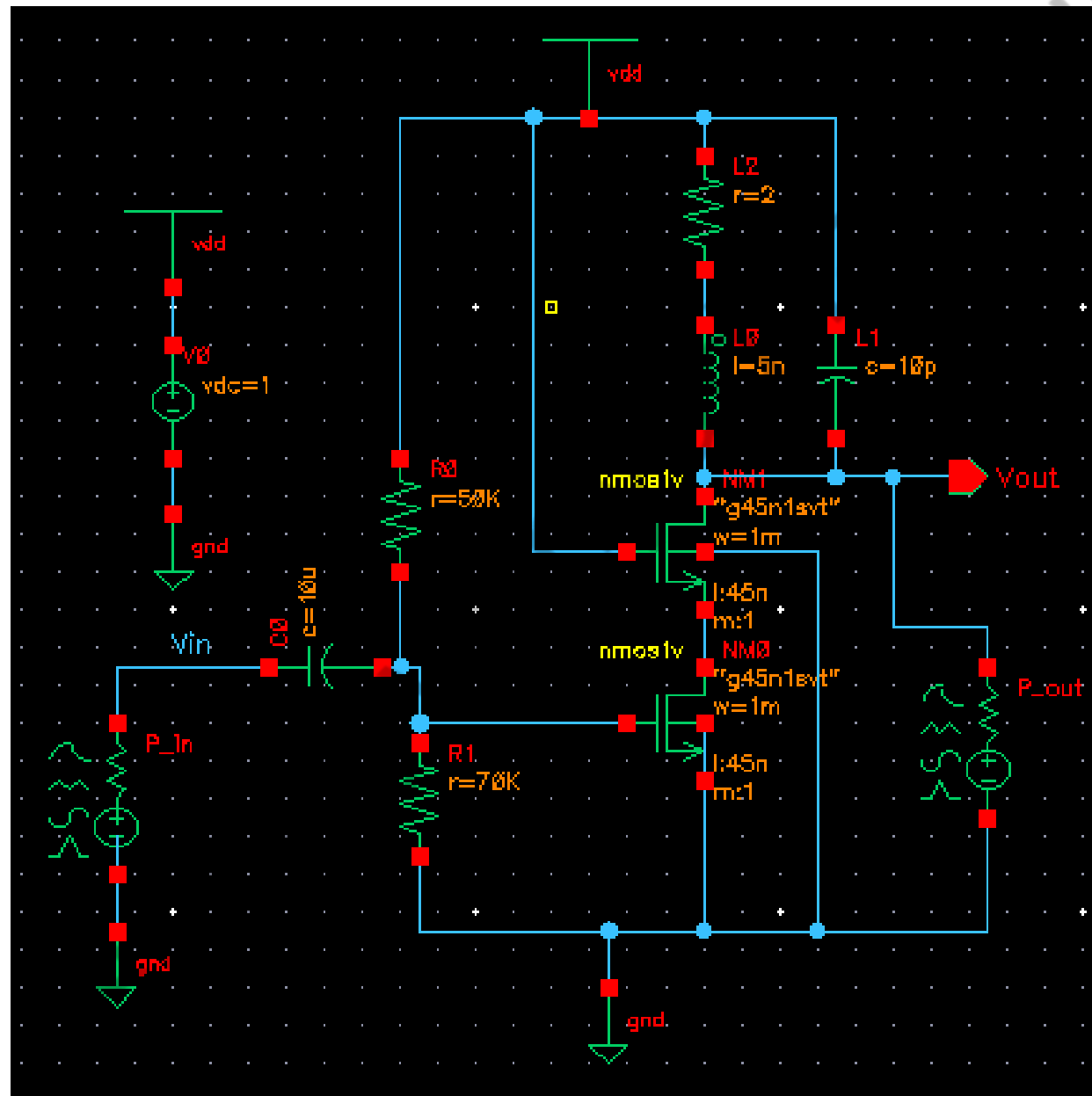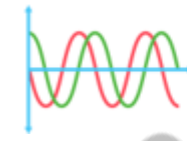
**website: [sanjayvidhyadharan.in](http://sanjayvidhyadharan.in)**




# LNA

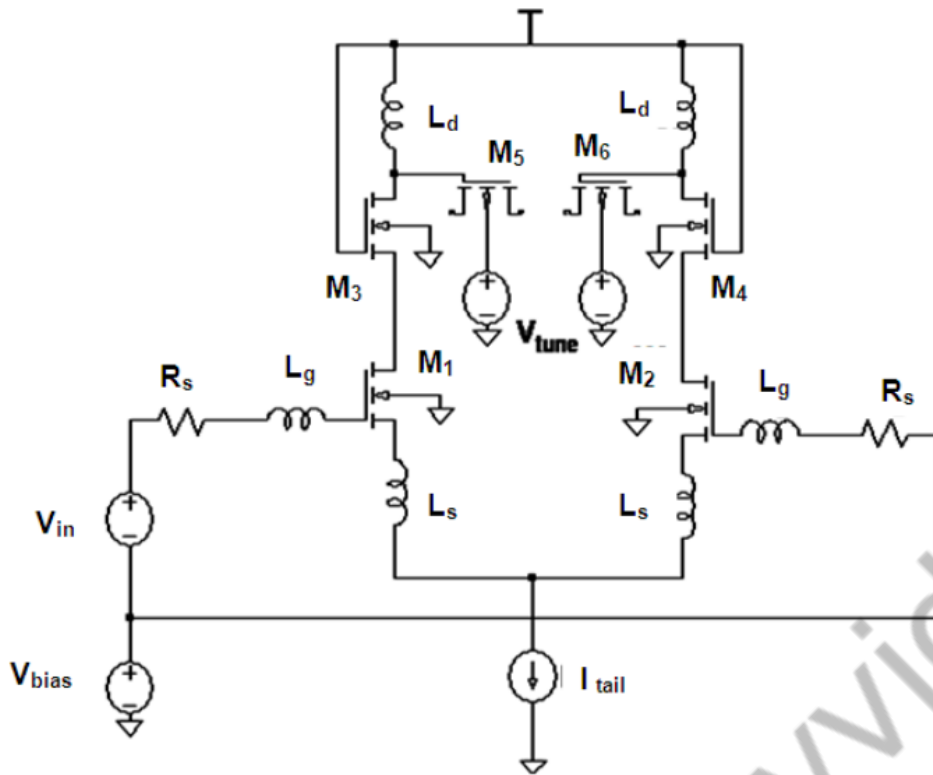


PMOS Varicap

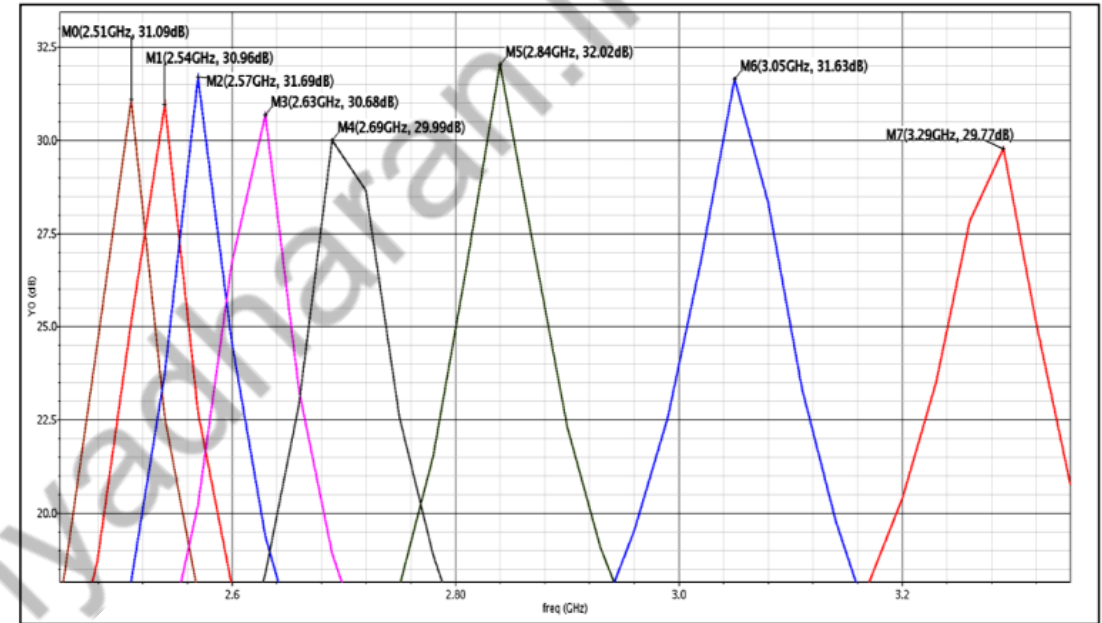

Active Inductor

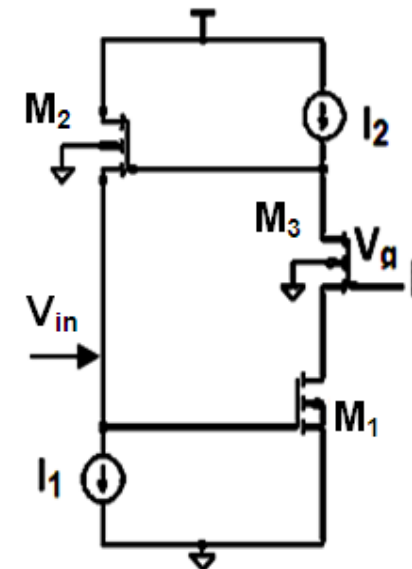

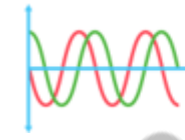

## Figure of Merits

1. AC gain , centre freq and bandwidth
2. Verification of gain with transient analysis
3. Noise Figure

<https://sanjayvidhyadharan.in/courses/analog-ic-design/>

- The amount of noise added by the network is embodied in the Noise Factor F, which is defined by


$$\text{Noise factor } F = \frac{\left(\frac{S}{N}\right)_{IN}}{\left(\frac{S}{N}\right)_{OUT}}$$

- F equals to 1 for noiseless network and in general  $F > 1$ . The noise figure in the noise factor quoted in dB  
i.e. Noise Figure F dB =  $10 \log_{10} F$   $F \geq 0 \text{ dB}$


3 dB

## Figure of Merits

### 4. S-Parameters

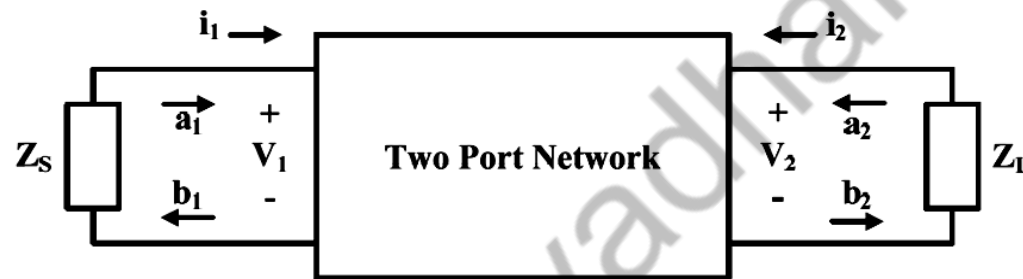

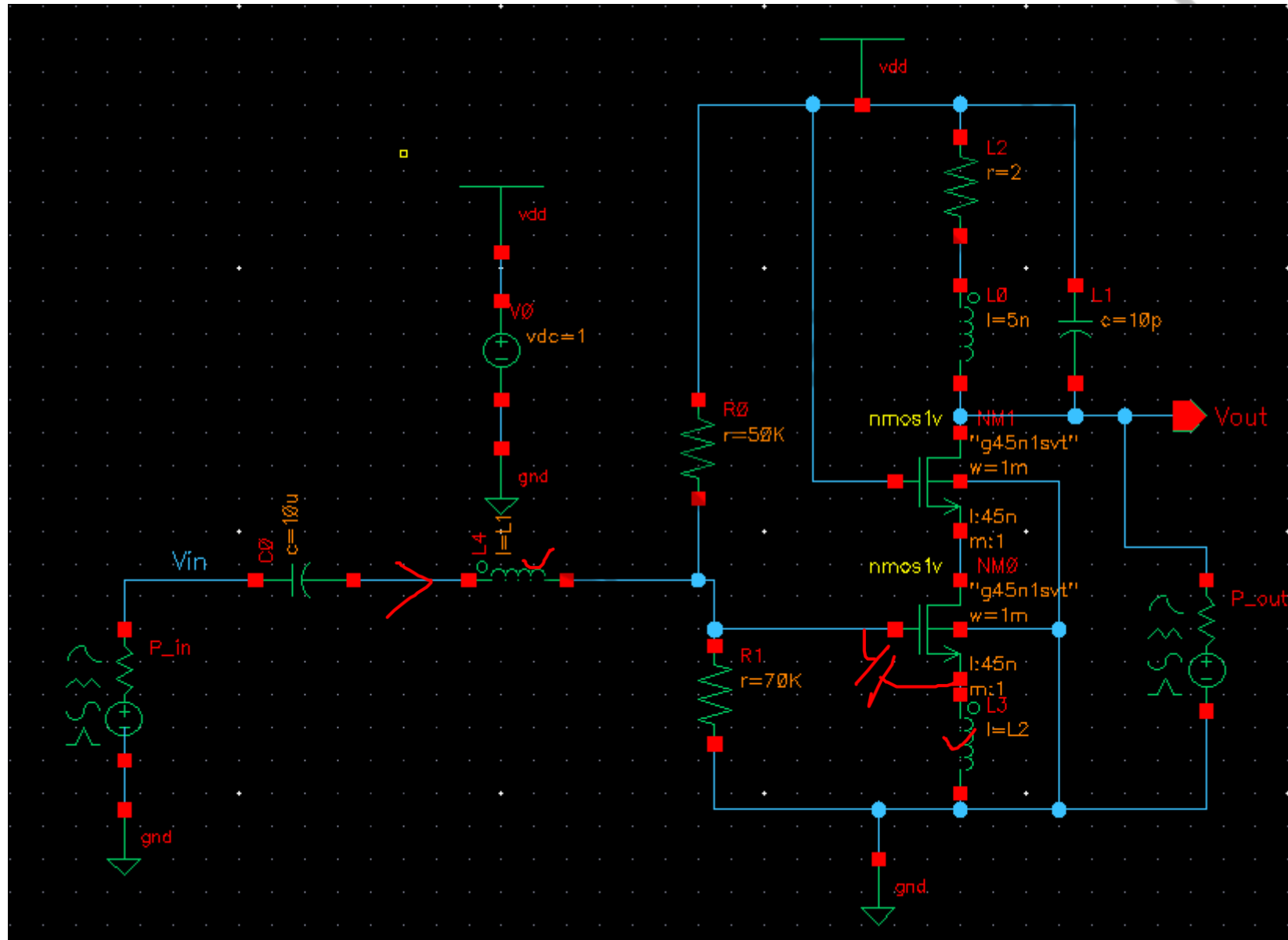- $S_{11} = b_1/a_1$  Network input reflection coefficient ✓
- $S_{21} = b_2/a_1$  Forward gain
- $S_{22} = b_2/a_2$  Output reflection
- $S_{12} = b_1/a_2$  Reverse gain



## Design Steps for Input Matching

•**Step 1:** Chose a value below 10 nH for  $L_S$  (say 1 nH). Larger size spiral inductors in CMOS technology will be lossy and will occupy large silicon area.

•**Step 2:** Calculate  $\omega_0$  as per the formula given below for input impedance matching.

$$R_S = 50 = \omega_0 L_S$$

•**Step 3:** Calculate value of  $L_G$  as per the formula given below for desired value of Q (3dB band width  $BW_{3dB}$ ).

$$Q = \frac{f_0}{BW_{3dB}} = \frac{(L_G + L_S)\omega_0}{R_S}$$


•**Step 4:** Calculate  $C_{gs}$  as per the formula given below for obtaining the desired center frequency  $f_0$ .

$$f_0 = \frac{1}{2\pi\sqrt{C_{gs}(L_G + L_S)}}$$

•**Step 5:** Calculate the width  $W$  of the input stage transistor knowing  $C_{ox}$  from technology and assigning appropriate  $L$ . (say 500 nm to avoid short channel effects)

•**Step 6:** Calculate  $g_m$  and  $I_{tail}$  using the formulae given below.
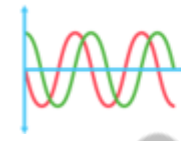
$$g_m = \omega_T C_{gs} = \sqrt{2k'_n \left(\frac{W}{L}\right)_n I_{DS}}$$



**Thankyou**