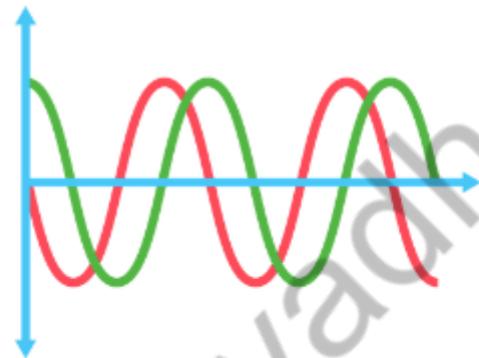


Course : RF Microelectronics





Lecture 4: Mixers

Prof. Sanjay Vidhyadharan




website: sanjayvidhyadharan.in

Mixers

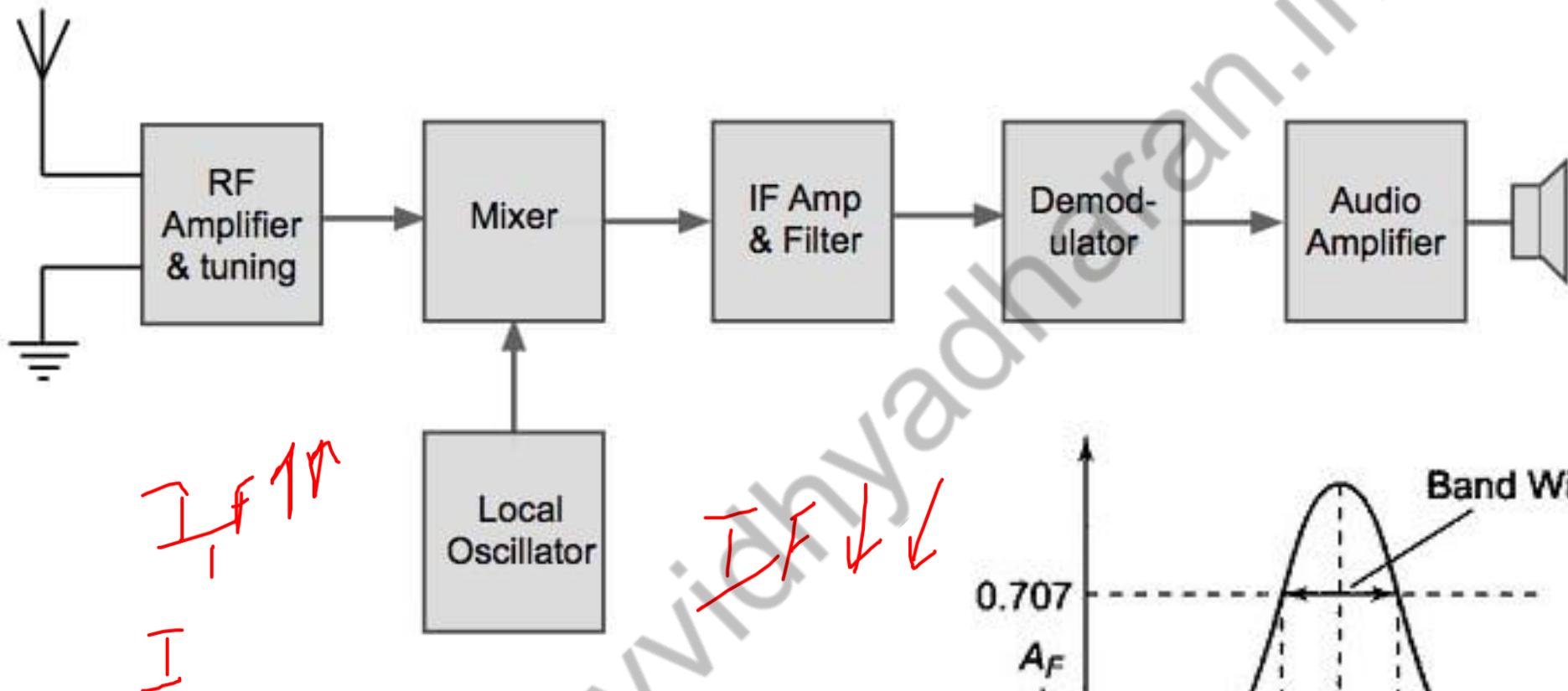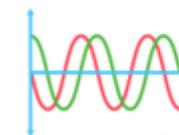


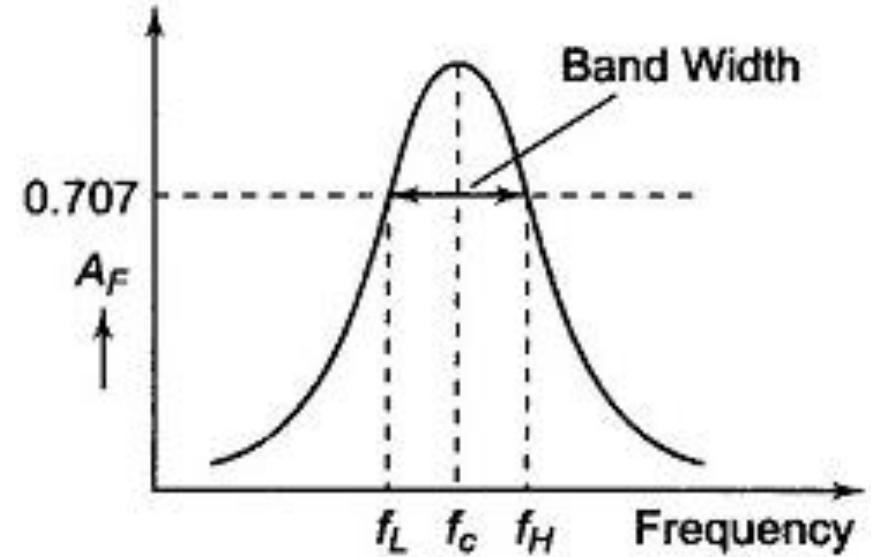
$$\cos A * \cos B = \frac{1}{2} [\cos(a+b) - \cos(a-b)]$$



100 MHz RF * 90 MHz LO = 10 MHz IF + 190 MHz (To be filtered)

80 MHz RF (image freq) * 90 MHz IF = 10 MHz + 170 MHz (To be filtered)


Mixers

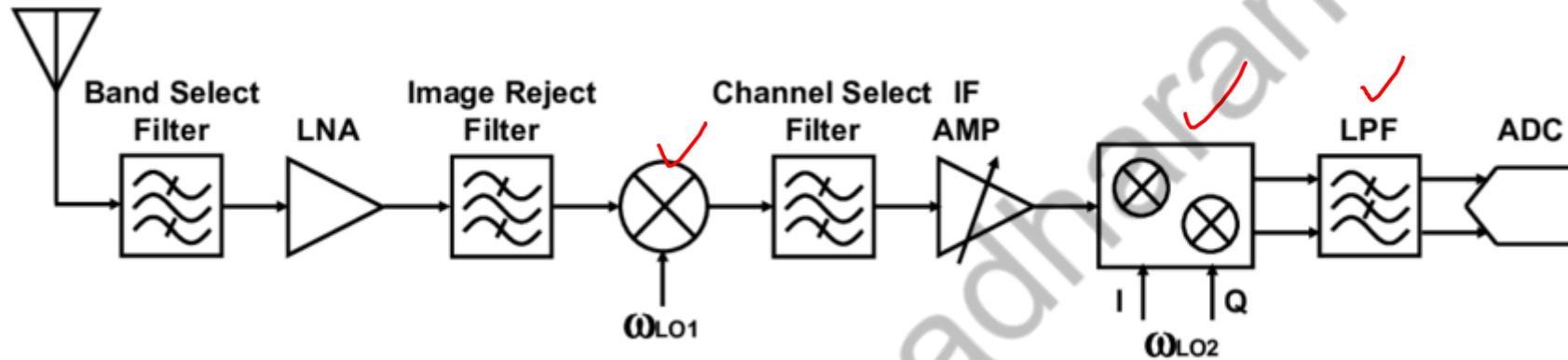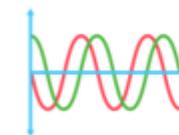



$$\cos A * \cos B = \frac{1}{2} [\cos(a + b) - \cos(a - b)]$$

$$100 \text{ MHz RF} * 90 \text{ MHz IF} = 10 \text{ MHz IF1}$$
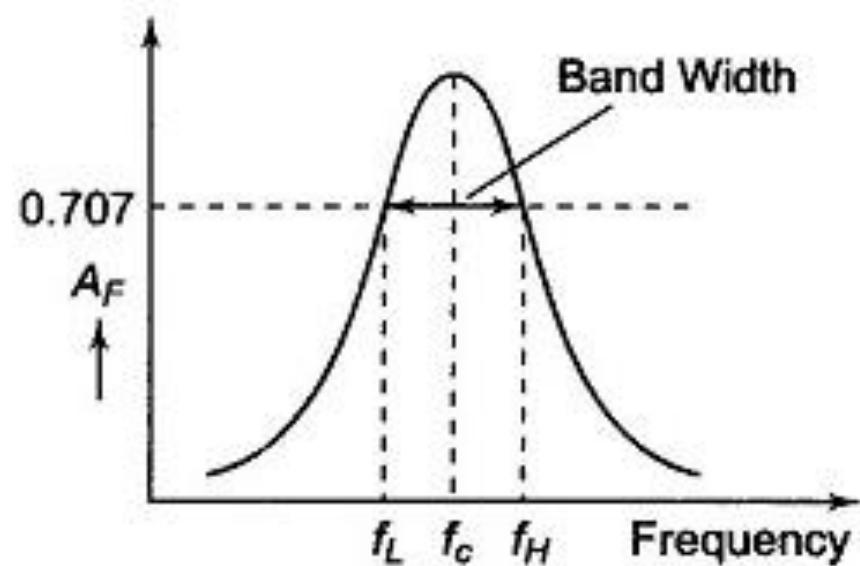
$$10 \text{ MHz RF} * 9.5 \text{ MHz IF} = 500 \text{ KHz IF2}$$



Mixers

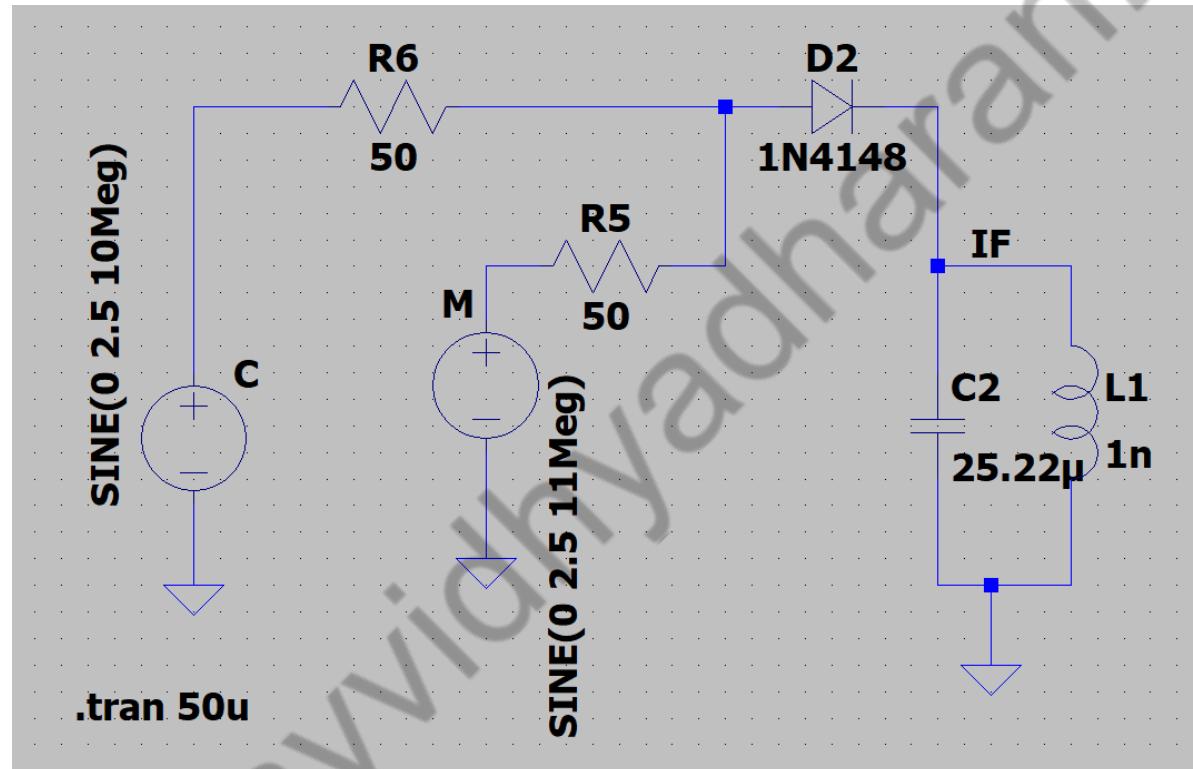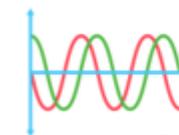


$$y(t) \approx a_0 + a_1 x(t) + a_2 x^2(t) + a_3 x^3(t) + a_4 x^4(t) + \dots$$

$$(\cos A + \cos B)^2$$

$$2 \cos A \cos B$$


$$\cos A * \cos B = \frac{1}{2} [\cos(a+b) - \cos(a-b)]$$


Mixers

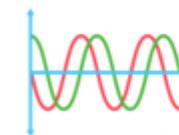

sanjayvidhyadharan.in

Gilbert Mixer

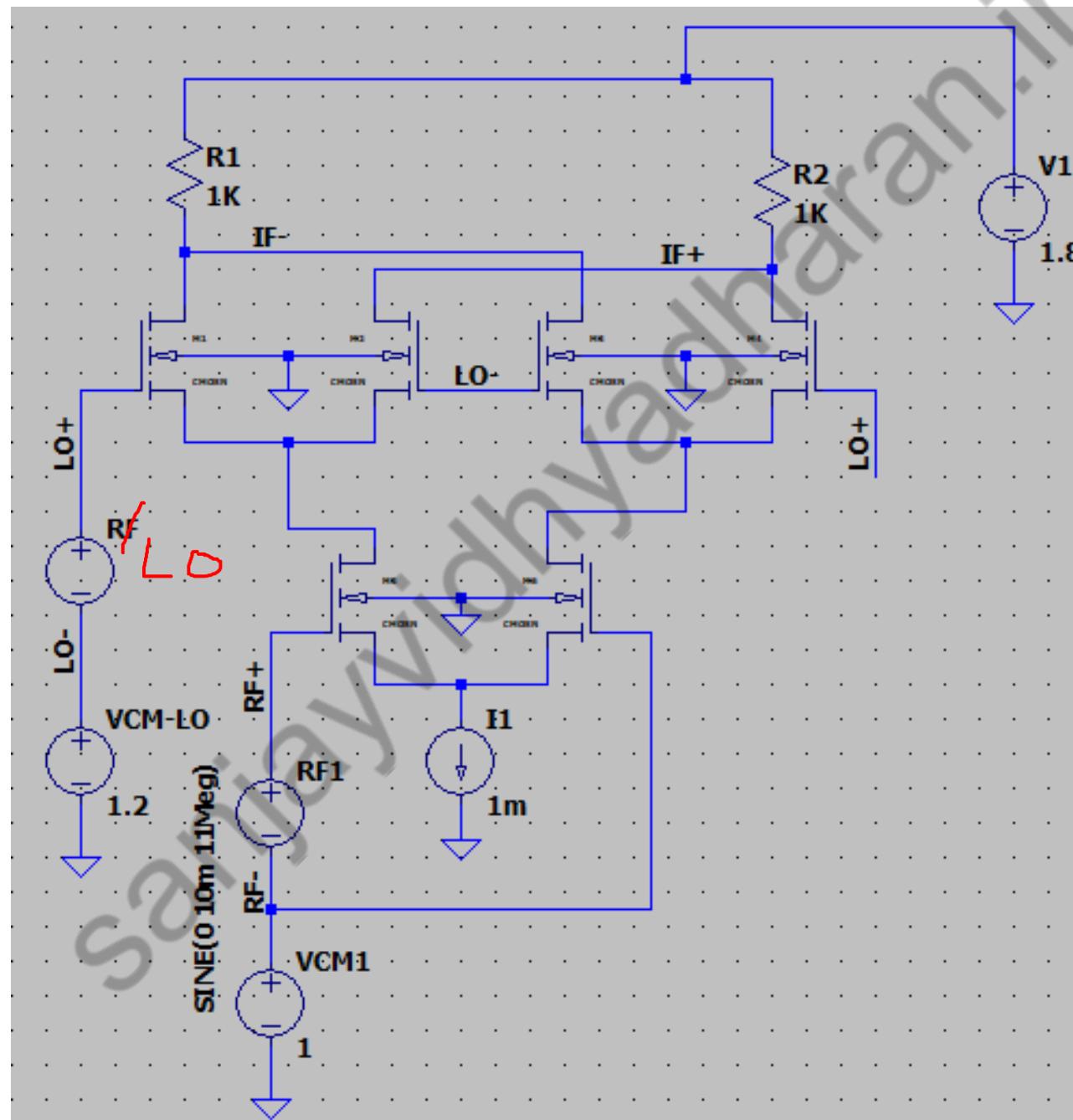

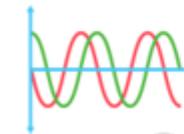

Thankyou

SanjayVidhyadharan.in