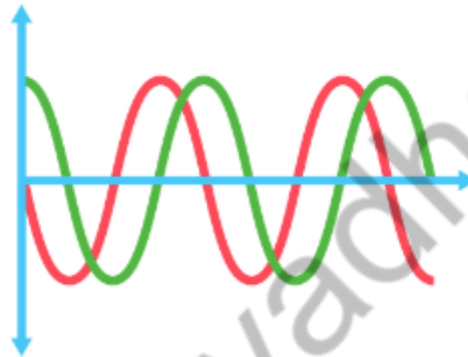


Course: Advanced Analog IC Design




Lecture 5: Linear Regulator Design and Simulation

Prof. Sanjay Vidhyadharan



website: sanjayvidhyadharan.in

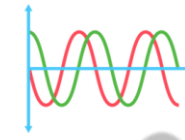


Output DC Voltage independent of:-


1. Power Supply Voltage
2. Load Current
3. Temperature

Should be stable

Linear Regulator

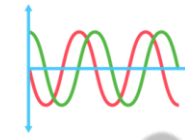

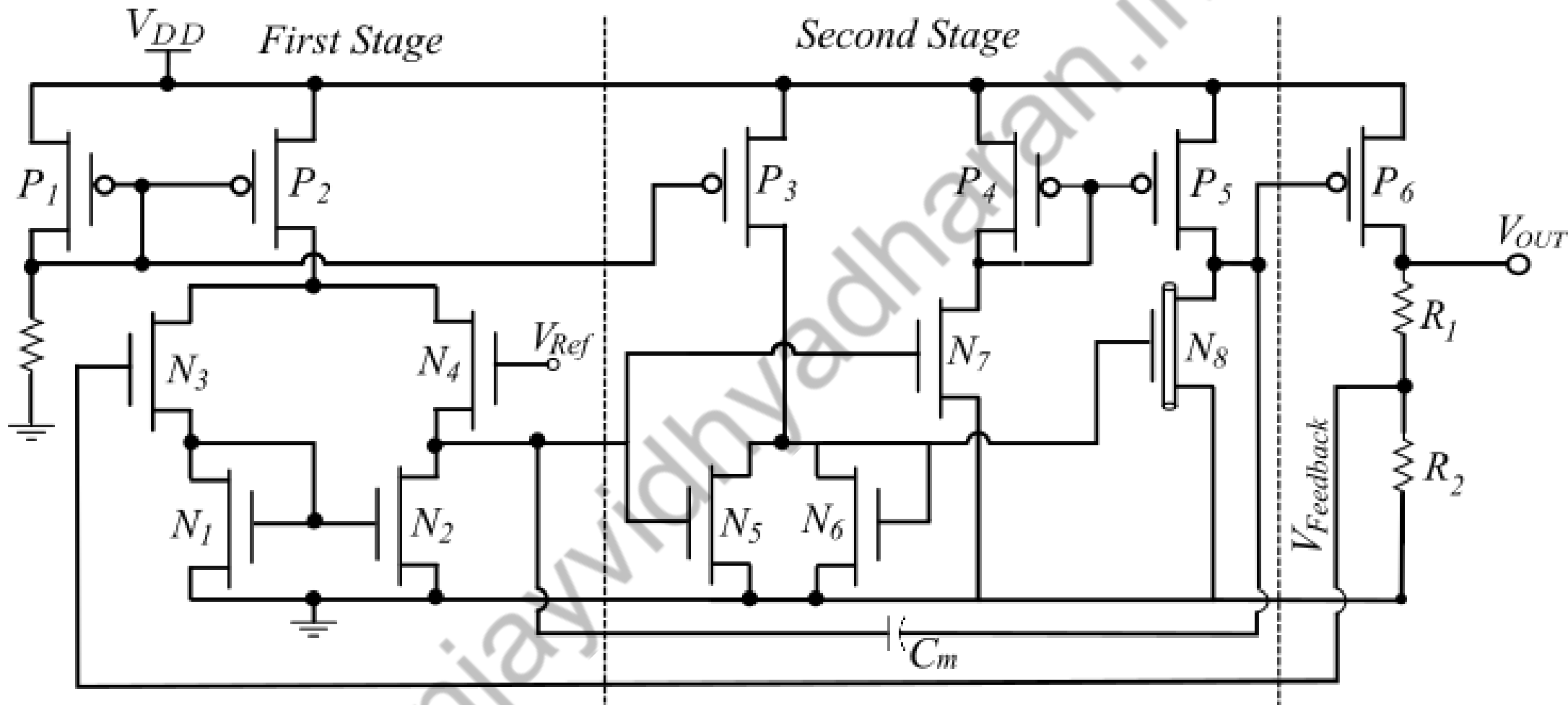sanjayvidhyadharan.in
Course: Advanced Analog IC Design



$$\frac{V_{out} * R_2}{R_1 + R_2} = V_{Ref}$$

$$V_{out} = \frac{V_{Ref} (R_1 + R_2)}{R_2}$$

Simulation done for $V_{out} = 0.7 V$ and $V_{Ref} = 0.25 V$

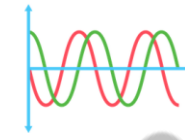



Figure of Merits:-

1. Line Regulation (%) = $(\Delta V_{out} / \Delta V_{in}) * 100$

2. Load Regulation (%)
= $[(V_{no_load} - V_{full_load}) / V_{full_load}] * 100$

3. Temperature Variation = $\Delta V_{out} / \Delta Temp$

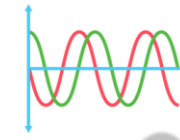4. Efficiency (%) = $(Power\ Load / Power\ Source) * 100$



Thank You