





# **VLSI Design**

## **Lecture 8**

### **Dynamic Logic**

**By Prof. Sanjay Vidhyadharan**

# Static CMOS Logic

 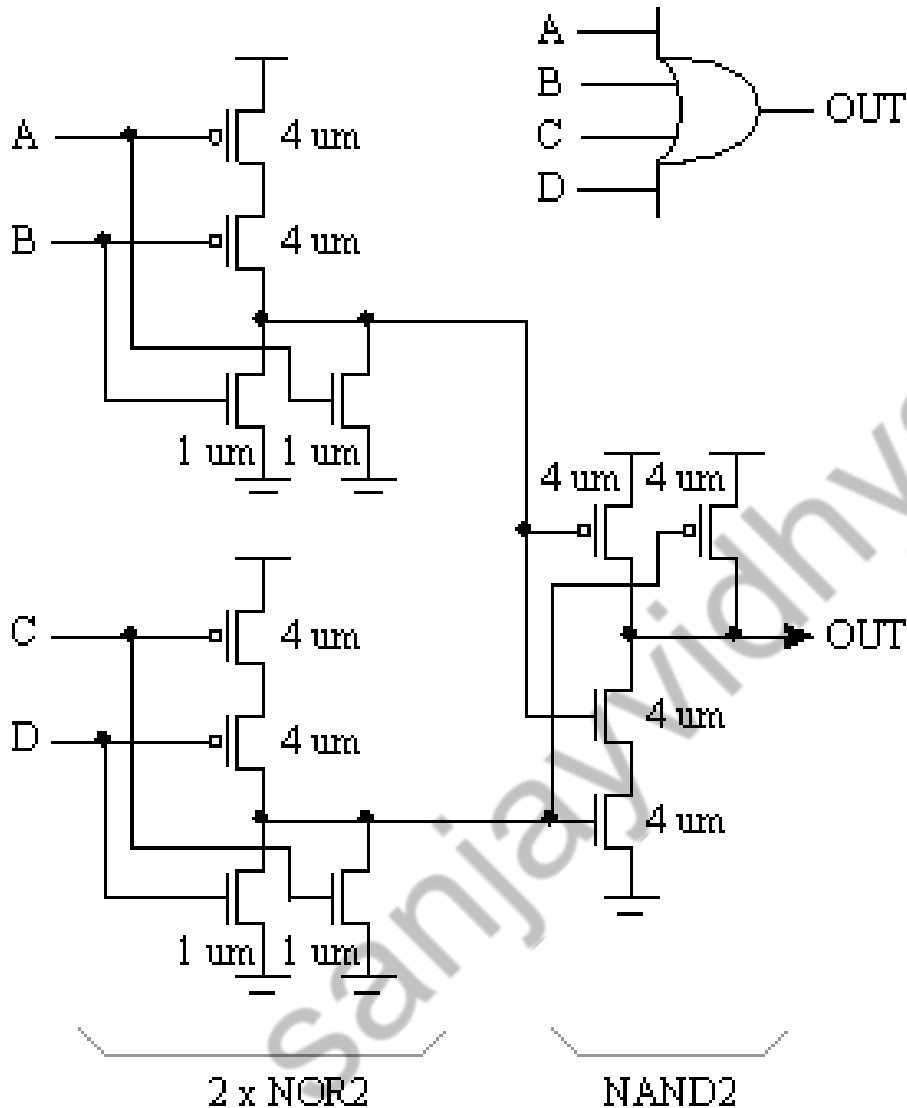

$$F = A + B + C + D$$


$$F = \{[(A+B) + (C+D)]'\}'$$

$$F = \{(A+B)' \cdot (C+D)'\}'$$

- Area Large
- Static Dissipation
- Dynamic Dissipation
  - Short Circuit
  - Switching Loss

# Static Full Adder

A	B	Carry In	Sum	Carry out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

$$\text{Carry}(CY) = AB + BC + AC$$

$$\text{Sum}(S) = \bar{A}\bar{B}C + A\bar{B}\bar{C} + \bar{A}B\bar{C} + ABC$$

$$\left. \begin{aligned} CY &= AB + C(A + B) \\ S &= \bar{C}Y(A + B + C) + ABC \end{aligned} \right\} \begin{array}{l} \text{Simplified} \\ \text{Expressions} \end{array}$$

# CMOS 28T Mirror Adder


	BC <sub>i</sub>	00	01	11	10
A	0	0	0	1	0
	1	0	1	1	1

$$\text{Carry} = AB + BC + CA = AB + C(A + B)$$

$$\text{Pull - Down Network for Carry Bar} = AB + C(A + B)$$


$$\begin{aligned} \text{Pull - UP Network for Carry Bar} &= A'B' + B'C' + C'A' \\ &= A'B' + C'(A' + B') \end{aligned}$$

# CMOS 28T Mirror Adder

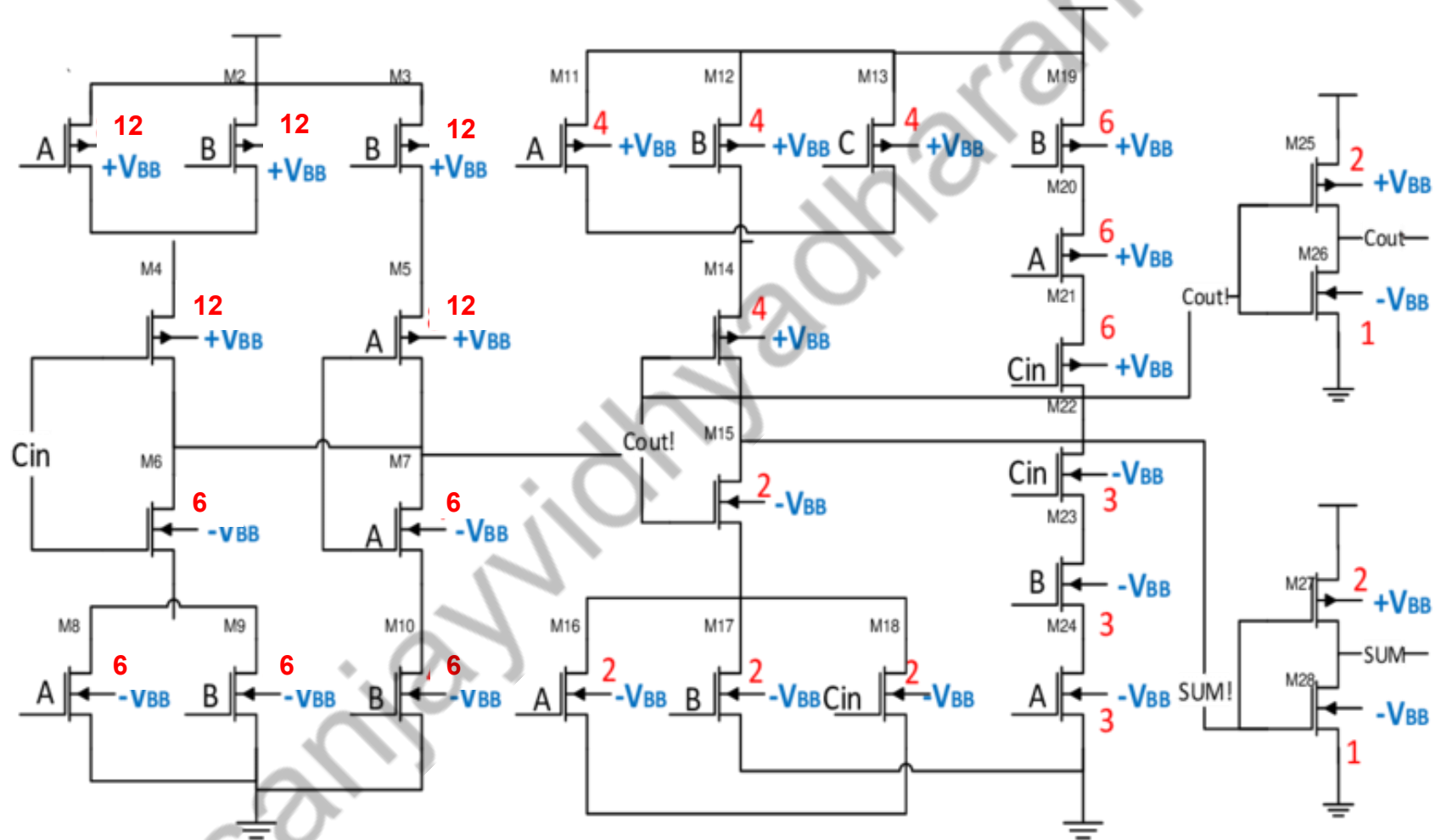

10/1/2025 Carry Delay = 2 Gate Delay and Sum = 3 Gate Delays

# Dynamic Logic

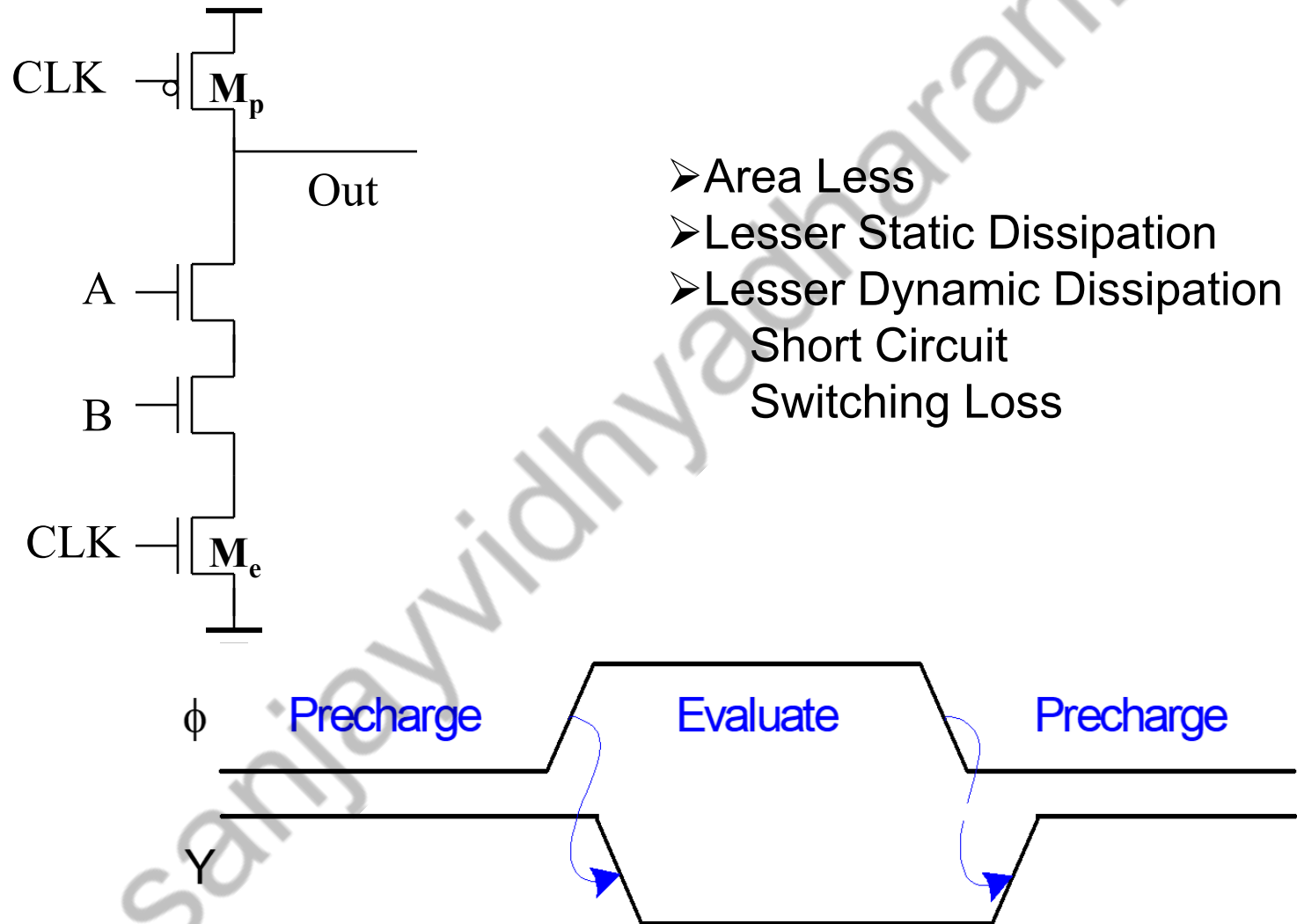

# Static vs. Dynamic


**In static circuits at every point in time (except when switching) the output is connected to either GND or VDD via a low resistance path.**

fan-in of  $n$  requires  $2n$  ( $n$  N-type +  $n$  P-type) devices

**Dynamic circuits rely on the temporary storage of signal values on the capacitance of high impedance nodes.**

requires on  $n + 2$  ( $n+1$  N-type + 1 P-type) transistors


# Dynamic Gate

 

Two phase operation

Precharge (Clk = 0)

Evaluate (Clk = 1)

 

$$OUT = \overline{CLK} + (\overline{A \cdot B + C}) \cdot CLK$$

DG needs periodic sequence of pre-charges and evaluations



# Properties of Dynamic Gate

- Once the output of a dynamic gate is discharged, it cannot be charged again until the next pre-charge operation.
- Inputs to the gate can make at most one transition during evaluation.
- Output can be in the high impedance state during and after evaluation (PDN off), state is stored on CL

# Properties of Dynamic Gate

- **Logic function is implemented by the PDN only**  
number of transistors is  $N + 2$  (versus  $2N$  for static complementary CMOS)
- **Full swing outputs ( $V_{OL} = \text{GND}$  and  $V_{OH} = V_{DD}$ )**
- **Non-ratioed - sizing of the devices does not affect the logic levels**
- **Faster switching speeds**
  - Reduced load capacitance due to lower input capacitance
  - Reduced load capacitance due to smaller output loading
  - Reduced logical effortNo  $I_{sc}$  so all the current provided by PDN goes into discharging  $C_L$

# Properties of Dynamic Gate

- **Overall power dissipation usually higher than static CMOS (for low input switching activity)**
  - No static current path ever exists between  $V_{DD}$  and GND (including  $P_{sc}$ )
  - Higher transition probabilities
  - Extra load on Clk
- **PDN starts to work as soon as the input signals exceed  $V_{Tn}$ , so  $V_M$ ,  $V_{IH}$  and  $V_{IL}$  equal to  $V_{Tn}$** 
  - Low noise margin ( $N_{ML}$ )
  - Needs a pre-charge / evaluate clock

# Speed of Dynamic Logic

Main advantages are increased speed and reduced implementation area

For low input signal no additional switching occurs  $t_{pLH} = 0!$

Pre-charge time should coincide with other system function “Dead Zone”

- o For Microprocessor instruction decode

# Transition Activity

- ❑ Switching activity,  $P_{0 \rightarrow 1}$ , has two components
  - A static component – function of the logic topology
  - A dynamic component – function of the timing behavior (glitching)

2-input NOR Gate

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

Static transition probability

$$\begin{aligned} P_{0 \rightarrow 1} &= P_{\text{out}=0} \times P_{\text{out}=1} \\ &= P_0 \times (1 - P_0) \end{aligned}$$

With input signal probabilities

$$P_{A=1} = 1/2$$

$$P_{B=1} = 1/2$$


NOR static transition probability

$$= 3/4 \times 1/4 = 3/16$$
 
# Transition Activity

- Switching activity is a strong function of the input signal statistics


- $P_A$  and  $P_B$  are the probabilities that inputs A and B are one



$$P_{0 \rightarrow 1} = P_0 \times P_1 = (1 - (1 - P_A)(1 - P_B)) (1 - P_A)(1 - P_B)$$

# Transition Activity

	$P_{0 \rightarrow 1} = P_{\text{out}=0} \times P_{\text{out}=1}$
NOR	$(1 - (1 - P_A)(1 - P_B)) \times (1 - P_A)(1 - P_B)$
OR	$(1 - P_A)(1 - P_B) \times (1 - (1 - P_A)(1 - P_B))$
NAND	$P_A P_B \times (1 - P_A P_B)$
AND	$(1 - P_A P_B) \times P_A P_B$
XOR	$(1 - (P_A + P_B - 2P_A P_B)) \times (P_A + P_B - 2P_A P_B)$

 


For X:  $P_{0 \rightarrow 1} = P_0 \times P_1 = (1 - P_A) P_A$   
 $= 0.5 \times 0.5 = 0.25$

For Z:  $P_{0 \rightarrow 1} = P_0 \times P_1 = (1 - P_X P_B) P_X P_B$   
 $= (1 - (0.5 \times 0.5)) \times (0.5 \times 0.5) = 3/16$

# Dynamic Logic

## ➤ Dynamic Logic Suffers from Charge Sharing Phenomenon

 

**Case1.**  $\Delta V_{out} > -V_{Tn}$   
 $|\Delta V_{out}| < V_{Tn}$

$$V_{DD} \cdot C_Y = V_Y C_Y + (V_{DD} - V_{Tn}) C_X$$

$$\Delta V_{out} = - \frac{(V_{DD} - V_{Tn}) C_X}{C_Y}$$


$$C_X \ll C_Y$$

$$V = Q/C$$



# Dynamic Logic

## ➤ Dynamic Logic Suffers from Charge Sharing Phenomenon

 

**Case2.**  $\Delta V_{\text{out}} < -V_{\text{Tn}}$


$$V_{\text{DD}} \cdot C_Y = V_Y C_Y + V_X C_X$$

$$V_{\text{DD}} \cdot C_Y = V_Y C_Y + V_Y C_X$$

$$V_{\text{DD}} \cdot C_Y = (V_{\text{DD}} + \Delta V_{\text{out}}) (C_Y + C_X)$$


$$\Delta V_{\text{out}} = - \frac{V_{\text{DD}} C_X}{C_Y + C_X}$$

# Dynamic Logic

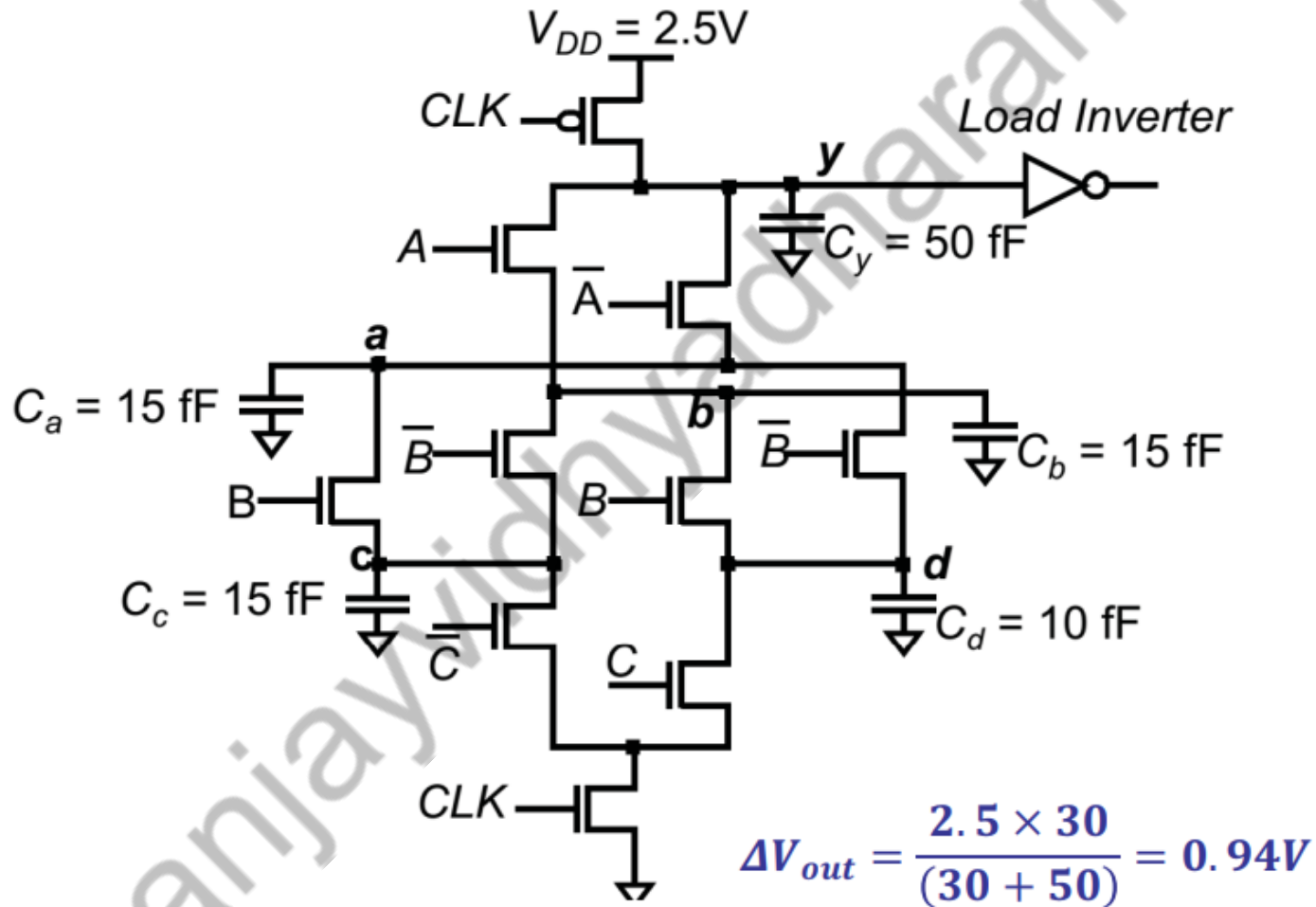

# Dynamic Logic

## Solution to Charge Redistribution

 

Pre-charge internal nodes using a clock-driven transistor (at the cost of increased area and power)

# Dynamic Logic


---

## *Capacitive Coupling*

The high impedance of the output node makes the circuit very sensitive to crosstalk effects. A wire routed over a dynamic node may couple capacitively and destroy the state of the floating node.

# Dynamic Logic


*Backgate (or output-to-input) coupling*

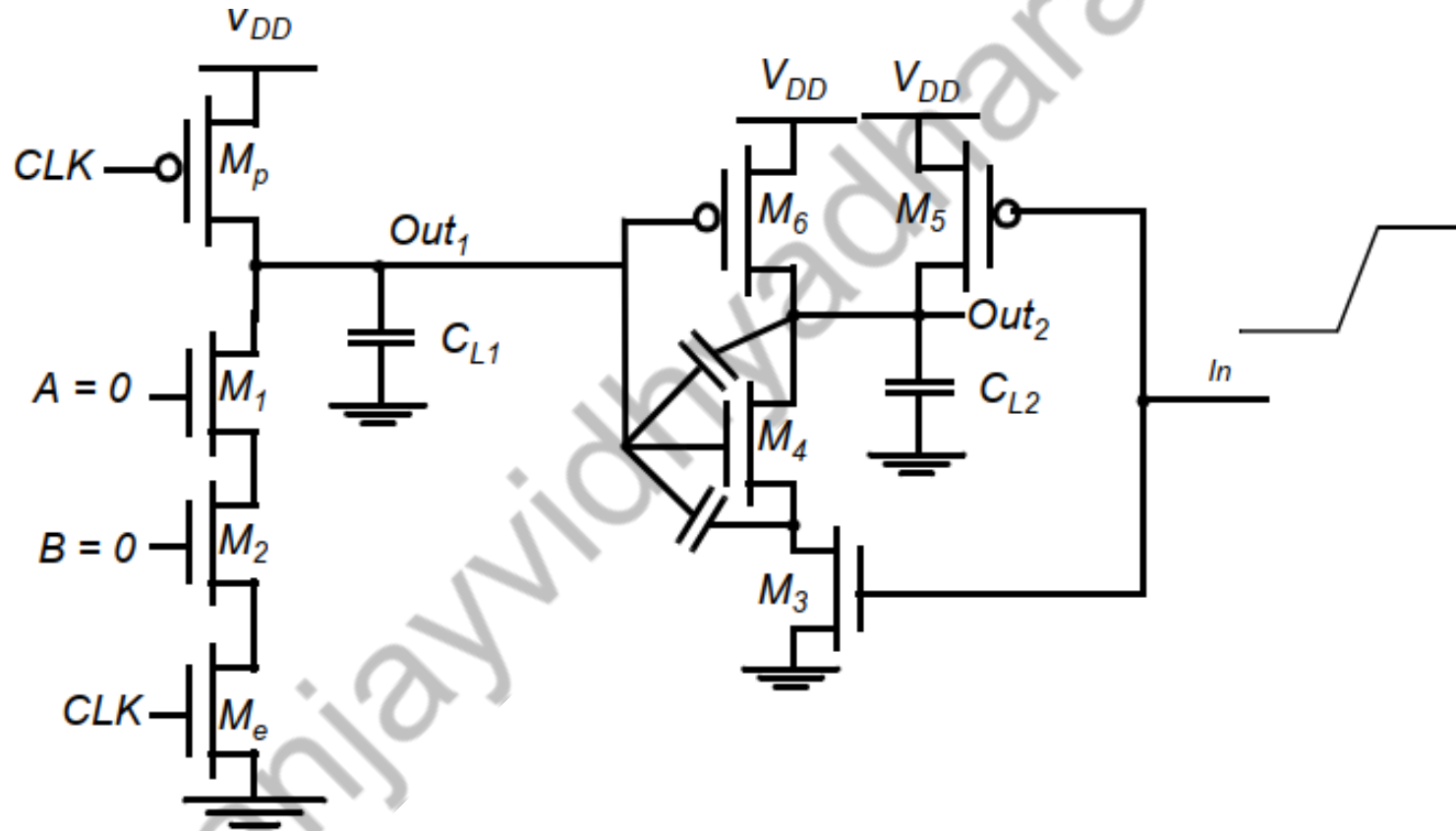

# Dynamic Logic


## Solution to Charge Redistribution

Keeper PMOS used to restore high state

 


# Dynamic Logic

## Contention

 

# Dynamic Logic


 


[7] M.E.S Elraba, M.H Anis, M.I Elmasry, "A contention-free domino logic for scaled down CMOS technologies with ultra low threshold voltages," *Proc. of IEEE International Symposium on Circuits and Systems* pp. 748 - 751, May 2000.



# Dynamic Logic


## Clock-Feedthrough

  
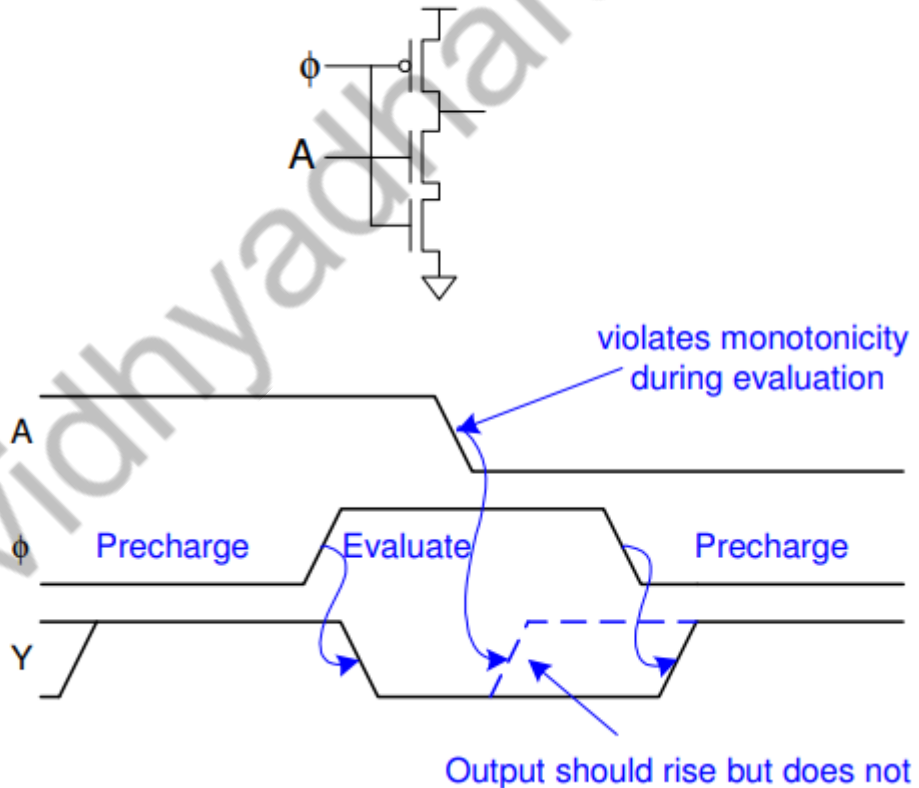
# Dynamic Logic



- Dynamic gates require *monotonically rising* inputs during evaluation

- 0  $\rightarrow$  0
- 0  $\rightarrow$  1
- 1  $\rightarrow$  1
- But not 1  $\rightarrow$  0



# Dynamic Logic

## ➤ Cascading Dynamic Gates

  



**Thank you**

sanjayvidhyadharan.in